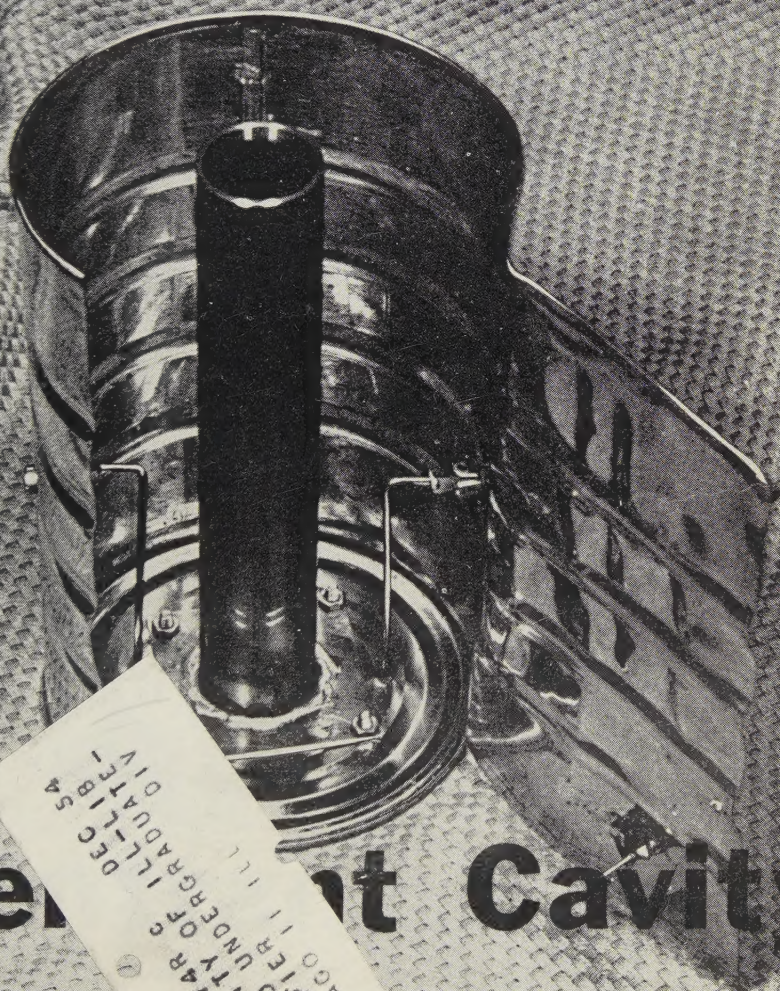


CQ

**RADIO  
AMATEURS'  
JOURNAL**

JULY  
1954  
35c




**Re-entrant Cavity  
TV Filter**

CHICAGO ILL  
UNIVERSITY OF ILL-  
CHICAGO ILL  
7748  
UNDERGRADUATE  
DIV-  
4  
DEC  
11-15  
FBS  
-



## Oscillator

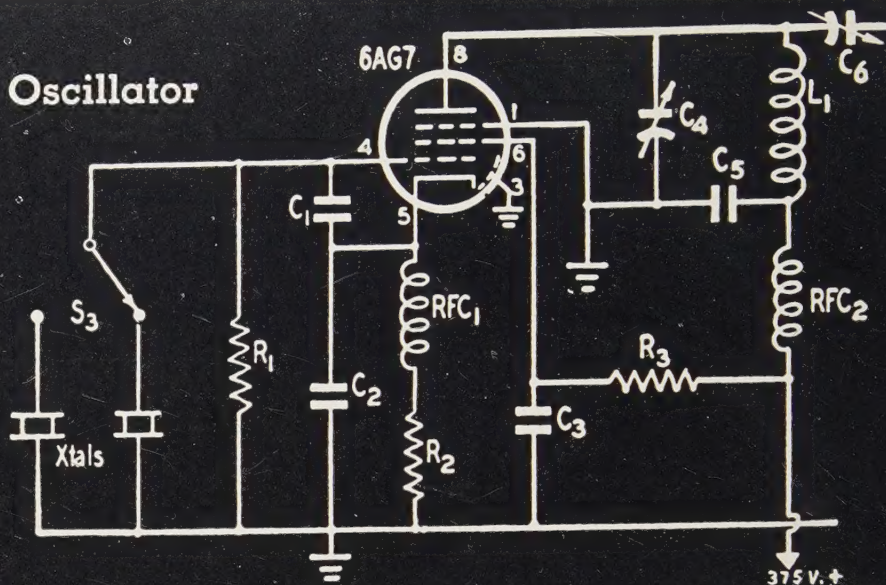

C1—15-uufd. mica

C2—50-uufd. mica

C3—0.002-uufd. mica

C4—100-uufd. variable

C5—500-uufd. mica

C6—7 to 35-uufd. variable

R1—68,000 ohms, ½ watt

R2—500 ohms, 1 watt

R3—47,000 ohms, 1 watt

RFC1, 2—2.5-mh. choke

S3—S.p.d.t. snap switch

L1—(see text below)

# FOUR BAND COVERAGE with **ONE** PR Crystal!

Never underestimate the driving power of a crystal oscillator . . . providing you have the right circuit and the right crystal. Here's one that will give ample output on 40, 20, 15 and 10 meters, utilizing a low-cost PR 7 MC. Crystal! It will drive a 2E26 or even an 807 clear down to 10 meters. The circuit is not tricky. Crystal oscillates at all times regardless of whether plate circuit is at resonance. The inductance L1 should resonate at the frequency on which output is desired. Do not substitute another tube for the 6AG7. Use a minimum of 375 volts and as high as 390 volts for best results when doubling, tripling or quadrupling. Try this oscillator. Addition-

al copies of the circuit may be obtained from your PR Jobber, or directly from the factory.

You can get high-quality, low-cost PRs for all amateur bands (exact integral frequency) at no additional cost. It's good to know where you are with a PR! They're unconditionally guaranteed!



**TYPE Z-2**

**\$2.95**

Exact integral frequency within 80 or 40 meter band without extra charge . . . from your jobber.

**PETERSEN RADIO CO., INC.** 2800 WEST BROADWAY  
COUNCIL BLUFFS, IOWA


EXPORT SALES: Royal National Company, Inc., 75 West Street, New York 6, N. Y., U. S. A.



Ask for the extra that costs you no more . . .
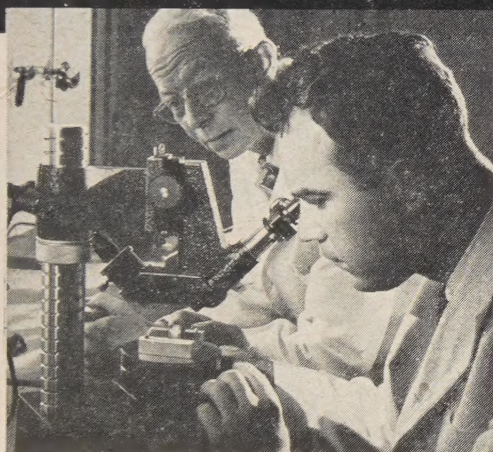
# G-E INSURED TUBE QUALITY! \*


\* Quality insured by G.E.'s multi-million-dollar investment in the world's most advanced tube manufacturing and test facilities.



← **MATERIALS CHECKING.** Special optical instruments are used to check surfaces of G-E tube parts. In addition, metallurgical and chemical tests analyze content, to determine whether materials meet specifications. G-E tube components must bear laboratory okays for quality.



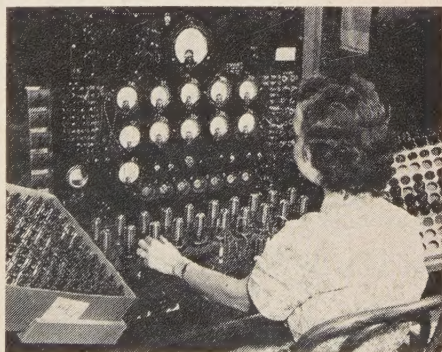**MANUFACTURING INSPECTION.** The comparator shown here magnifies a G-E tube grid some 50 times, so that the wire winding—finer than a human hair—can be accurately checked. Similar highly-developed optical equipment at all stages, makes inspection of tube parts easy and virtually mistake-proof.



**TUBE TESTING.** Before tubes are shipped, a comprehensive final test! Instrument dials tell a scientific story of electrical performance. Tubes that don't "make good" are scrapped. When you take a G-E tube from its carton, you know it will serve you long and well.

● G-E tube facilities include seven large factories in different cities, totaling more square feet of production space than used by any other manufacturer. Facilities include hundreds of intricate machines for high-precision quantity output, many of them G-E-designed . . . also advanced equipment like that shown on this page, for raw-materials analysis, manufacturing inspection, and final tube testing.

Insist on G-E Insured tube quality\*! See your G-E tube distributor for amateur tubes that are better-built because unequaled G-E resources stand behind them! *Tube Department, General Electric Company, Schenectady 5, New York.*

**COMING in September, on this page: terms of the 1954 Edison Radio Amateur Award. Get ready now to nominate an amateur you believe to be qualified, by reason of some outstanding public service!**

**GENERAL**  **ELECTRIC**

166-1B4



**choose with  
confidence...**

**use with  
satisfaction**

# BUD


**ELECTRONIC  
COMPONENTS  
and Sheet Metal  
PRODUCTS**

Get acquainted with the new and improved products in the extensive Bud line of Electronic Components and Sheet Metal Products. They will improve the performance of your rig and add to its appearance. Now there are over 1500 different types and sizes to meet your requirements.

Bud combines the latest technical data, engineering skill and manufacturing "know-how" to provide outstanding performance and still gives you the best value at prices no higher than ordinary products. Illustrated below are three products from the large Bud line, widely used by "Hams" for many years.

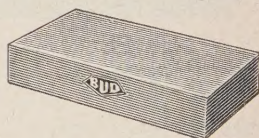
## BUD ALUMINUM CHASSIS

These outstanding chassis are made from one piece of best grade sheet aluminum. All corners are reinforced and welded on Government approved spot welders that are the same as those used in the welding of aluminum aircraft parts. The four sides are folded at right angles at the bottom to provide additional strength and rigidity. This also permits the attachment of a bottom plate if desired.



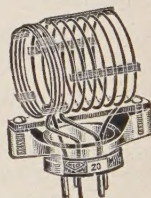
## BUD-75 WATT COIL with Polystyrene Base

Polystyrene has proven superior to porcelain for many reasons, including far greater resistance to breaking or cracking—the Q of the coil is exceptionally high due to the low power factor—pins are molded in place and always remain perfectly aligned—sharp corners are eliminated. Coils are furnished with fixed or adjustable center links or fixed or adjustable end links. They can be used on bands from 6 meter to 160 meter or in circuits using Pentode tubes.


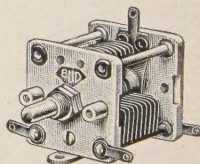
## BUD "CE" MIDGET CONDENSERS

Designed to meet the most rigid requirements in design of efficient ultra-high frequency electronic devices and precision laboratory equipment. Brass rotor and stator plate stacks are assembled into permanent units by means of electro-soldering which assures long life and accurate plate spacing. Sleeves and ball bearings assure smooth rotation. Fully insulated. Available in single or dual section in 25 sizes and capacities.



*See the Complete Bud Line at Your Local Distributor*



## BUD RADIO, INC.

2120 East 55th St.

Dept. Q

Cleveland 3, Ohio



# CQ RADIO AMATEURS' JOURNAL

Vol. 10, No. 7  
JULY, 1954

## EDITORIAL STAFF

MANAGING EDITOR  
OLIVER P. FERRELL

TECHNICAL EDITOR  
E. M. BROWN, W2PAU

## DEPARTMENT EDITORS

Herb Brier, W9EGQ	Novice
Wayne Green, W2NSD	Teletype
George Jacobs, W2PAJ	Propagation
Louisa B. Sando, W0SCF	YL
R. C. Spenceley, KV4AA	DX

## CONTRIBUTING EDITORS

Jack N. Brown,	W3SHY
G. F. Montgomery,	W3FQB
William I. Orr,	W6SAI
W. M. Scherer,	W2AEF

## DRAFTSMAN

Thomas Smith, W2MCJ

## BUSINESS STAFF

S. R. COWAN,	Publisher
S. L. CAHN,	Adv. Director
H. N. REIZES,	Adv. Mgr.
L. STEINER,	Adv. Rep.
D. SALTMAN,	Prod. Mgr.
R. CAMPBELL,	Edit. Prod.
H. WEISNER,	Circ. Mgr.
E. HARMAN	Ass't. Circ. Mgr.

## BRANCH OFFICES

California: Ted E. Schell, 2700 West 3rd Street, Los Angeles 5, Calif. Dunkirk 2-4889.  
Cleveland: Richard E. Cleary, Commercial Bank Bldg., Berea, Ohio. Telephone BE 4-7719.  
Foreign Subscription Representative: Radio Society of Great Britain, New Ruskin House, Little Russel St., London, WC 1, England.  
Technical Book & Magazine Co., 297 Swanston St., Melbourne C1, Victoria, Australia.  
Scandinavian Representative: Intrapress, 17 Nordre Paradisvej, Holte, Denmark.

CQ—(title Reg. U.S. Post Office)—is published monthly by Cowan Publishing Corp. Executive and Editorial offices, 67 West 44th Street, New York 36, N.Y. Phone MUrray Hill 7-2080. Reentered as Second Class Matter February 6, 1951 at the Post Office, New York, N.Y. under the Act of March 3, 1879. Subscription rates in U.S.A. Possessions, APO & FPO, 1 year \$3.00; 2 years \$5.00; 3 years \$7.00. Elsewhere add \$1.00 per year for postage. Single copies 35 cents. Printed in U.S.A. Entire contents copyright 1954 by Cowan Publishing Corp. CQ does not assume responsibility for unsolicited manuscripts.

POSTMASTER: SEND FORM 3579 to CQ.  
57 WEST 44th ST., NEW YORK 36, N. Y.

## FEATURE ARTICLES

Cavity TVI Filter	
Robert Schlesinger, K2CWO .....	14
Antennascope-54 (Part II)	
Wilfred M. Scherer, W2AEF .....	17
Test Equipment in the Ham Shack	
Howard Burgess, W5WGF .....	21
W2JIO—Achievement in Darkness	
Robert Hertzberg, W2DJJ .....	24
10/6 Packset	
Clifford C. Johnson W0URQ .....	26

## Departments

DX and Overseas News (KV4AA) .....	29
The YL's Frequency (W0SCF) .....	32
Ionospheric Propagation Conditions (W2PAJ) .....	34
The Novice Shack (W9EGQ) .....	36
What's New in Ham Radio .....	40
The VHF News .....	42

## Miscellaneous

Scratchi .....	6
Servos Available .....	8
Zero Bias .....	11
FEARL Notice .....	33
Classified Ads .....	62
Advertising Index .....	64





# Clipperts


Chicago Daily Tribune F\*\* Fri., March 19, 1954

## 5 IOWANS HEAD FOR PACIFIC IN RADIO HAM TEST

Newton, Ia., March 18 [Special]—Five radio hams left Newton today for an uninhabited coral atoll in the Pacific from which they will try to contact as many as possible of the world's 230,000 licensed radio amateurs.

The unique expedition was financed by contributions from radio hams all over the country, by the five participants, and by the Hallicrafters company of Chicago, which is lending the necessary equipment.

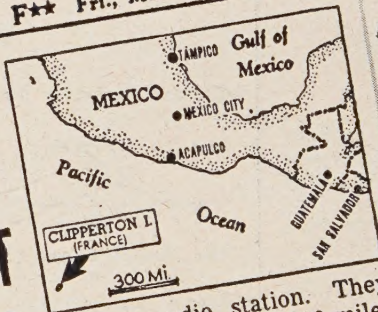The island on which they will be located will qualify as "a new country" in the rivalry among hams who try to excel each other in establishing contact with the most foreign



amateur radio station. They expect to drive the 2,200 miles to Acapulco in three or four days, where they will load their equipment aboard a chartered 83 foot motor vessel for the trip to the atoll.

### Use All Wave Bands

The group is comprised of Robert Denniston, a Newton building supply dealer; two employees at his lumber yard, Tom Partridge and Vern Hedman; Gene O'Leary, who operates a radio and television shop here, and Leo Olney, who has a television service in Des Moines.

At the end of the experiment all radio hams who contacted the "new country" will receive confirmation cards mailed by the Hallicrafters company.

Chicago Daily Tribune  
 Saturday, April 3, 1954  
 Part 1—Page 4 F\*\*

## SEXTANT LOCATES SO 'HAMS' CAN FIND THEIR

Five radio amateurs from Newton, Ia., March 18, set up a powerful radio transmitter on Clipperton Island, 65 miles off Acapulco, Mexico, today reported to have been unable to reach the land.

On their sea voyage the navigator plotted their bearing as the craft rolled, and the sextant was used to find the ocean.

The party was brought to a halt by a fog, and the communications commission was unable to reach them.



# F08AJ

## Adventure


Chicago Daily Tribune  
Saturday, April 24, 1954

### VIA RADIO 'HAMS' REACHED DESTINATION, UNINHABITED ISLE

Five radio amateurs who left Newton, Ia., March 18, reached the uninhabited island of Clipperton in the Pacific Ocean yesterday, and reported their arrival to radio "hams" of the Chicago area.


The group reached Clipperton island, 600 miles southwest of Acapulco, Mexico, after a hazardous voyage in which they lost their sextant, then had their schooner virtually disabled thru loss of sails in a squall and mechanical troubles, and finally got caught in the Humboldt current and drifted 90 miles from the island.

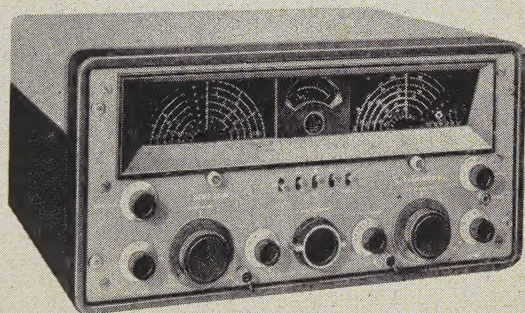The Hallicrafters company in Chicago said the group reached the is-



THIS RECEIVER WENT TO CLIPPERTON. Hallicrafters SX-88, the most wanted piece of ham equipment in years. Exclusive sensitivity from 10 Kc to 250 cycles in 6 steps. 1108 contacts on Clipperton from 28 countries—5 continents.

ONLY \$595.00.

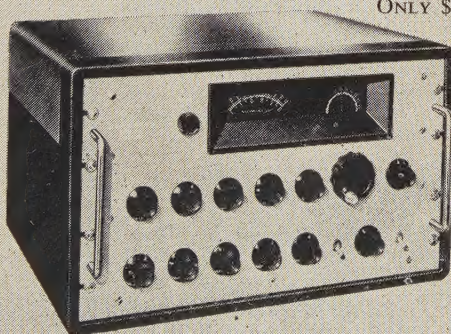

HERE'S THE TRANSMITTER THAT WENT TO CLIPPERTON. TVI Suppressed 100 Watter. Hallicrafters HT20. Continuous coverage from 1.7 Mc to 30 Mc—full band switching. Choice of 10 crystals. Shielded, filtered r-f compartment plus low-pass 52 ohm coaxial line output filter cuts anything over 30 Mc.


ONLY \$449.50.



Designed for



Application

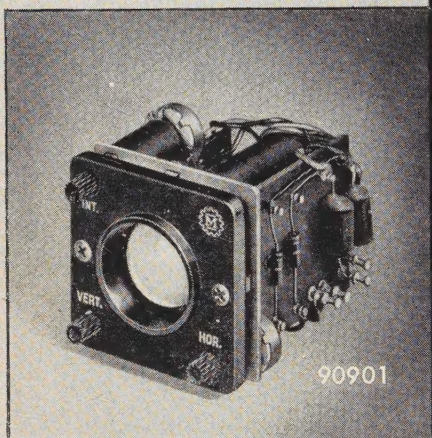

The No. 90901

One Inch

Instrumentation Oscilloscope

Miniaturized, packaged panel mounting cathode ray oscilloscope designed for use in instrumentation in place of the conventional "pointer type" moving coil meters uses the 1" 1CP1 tube. Panel bezel matches in size and type the standard 2" square meters. Magnitude, phase displacement, wave shape, etc. are constantly visible on scope screen.

**JAMES MILLEN  
MFG. CO., INC.**

MAIN OFFICE AND FACTORY  
**MALDEN  
MASSACHUSETTS**



Feenix, Ar

Deer Hon. Ed:

Ever are finding sum days that are just perfect aren't Hon. Sumthing? Boy oh boys. Like take a day. Hon. Brother Itchi and I going into town for all day like shopping trip. We getting into car, and sun are shining like million bux. We stepping on starter, and motor turning rite overs, instead grinding round like most same always. We zoomin' along hiways, motor sounding like pooring cat like king cream.

Scratchi turning on mobile rigs in car, toonin' across band, and heering fellows calling QRZ? grabbing mike and giving quick call, and back I coming! Having nice QSO, sineing off, and fellows from Sirraques New York calling me. What you thinking? He giving me S-9 plussedeyplus report. Wowie!! Sum DX on 160 meter mobiles, ne you thinking?

When hitting town, not running into any red lites. No sirree, all lites seeming to be green. We cuming to place to shopping, and what are we finding but place to parking rite in front of store. We going in store and finding big sale goings on. We savin' monies hand over fist. Leeving store and going down block and finding new store opening. Itel and I going in, buying few things, and as leeving man are telling us we win door prize. Free lunch for Brother Itchi and Scratchi and all groceries can possibly using for hole weeks.


Itchi and I staggering back to car, loded down with ham, turkey, sugar, flour and all sorts stuff, and when getting to car—Hon. Ed, you not bulleeving it. There are car, sitting there so pretty and shiny looking like new car. It are polished so looking like microwave antenna. What happening? Sum company are putting out new car polish, and they using Scratchi's car for showing how fine can looking with there compliments.

Well, Hon. Ed, it are likesame way all day. We can doing no rong. Fineally Itchi and I are done shopping, getting in car, and starting home. We are both smiling so much Hon. Jaws are akeing. In fact, Itchi are saying how lucky we are. Not only having 1/c day, but are even having free housekeeper. Yes indeedy. For past week having ree top-notch free housekeeper. You see, my Hon. Auntie Watanabe are cuming over from Sandy Ayege to visiting for awhile, and she deciding we needing helping hand around house. She are being as handy to having around house as VFO in DX contest. I

(Continued on page 8)



Your  
FREE copy  
is ready!

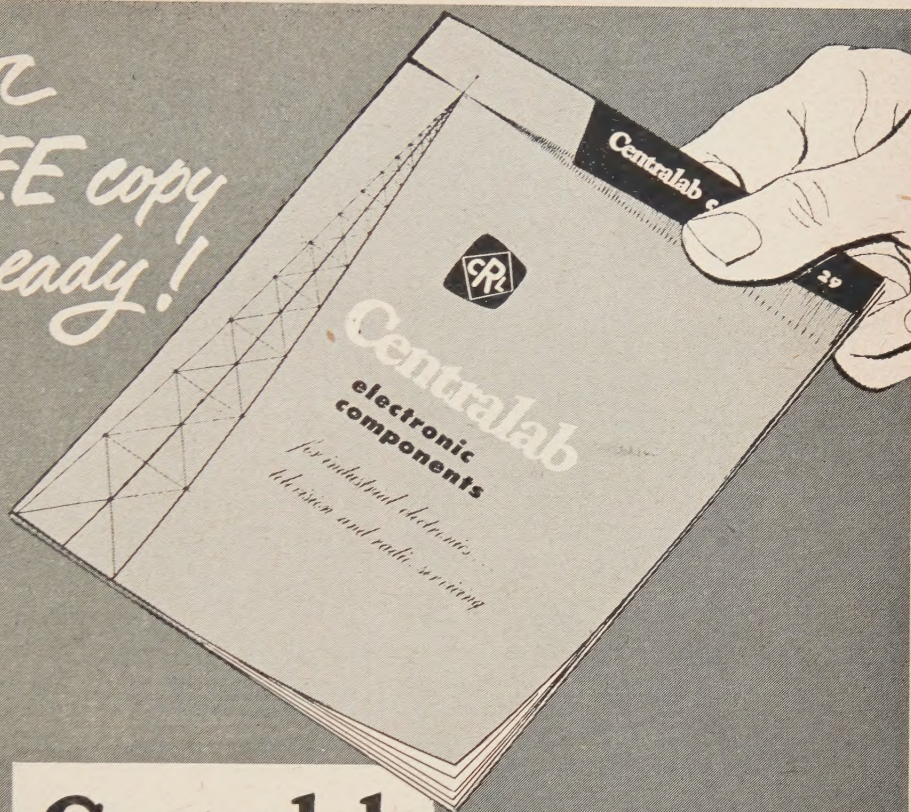

## New Centralab Catalog No. 29

**Keeps you up to date  
on Centralab's latest developments**

- New** values in Adashaft\* Radiohms
- New** Adashaft shafts
- New** Snap-Tite Controls
- New** Fastatch\* Dual Concentric Controls
- New** Senior Compentrol\*
- New** miniature rotary phenolic switches
- New** Phenolic Switch Kit
- New** complete line of standard DD disc capacitors
- New** miniature disc capacitors
- New** 3000-VDCW and 6000-VDCW Hi-Vo-Disc\* Capacitors
- New** arrangement of capacitor kits
- New** Precision Attachable Terminal Hi-Vo-Kaps®
- New** Negative 330 and Negative 1500 TC Tubular Capacitors
- New** easier-to-read listings on CRL Printed Electronic Circuits
- New** P. E. C.\* Kits

\*Trademark

**Revised 48-page reference book on  
America's most complete line of:**

**Volume controls      Switches  
Printed Electronic Circuits\*  
Capacitors      Steatite insulators**

Centralab Catalog No. 29 pictures and describes hundreds of CRL components, with exact specifications and details.

Ask your Centralab distributor for your free copy. Or send the coupon to us today.

# Centralab

\*Trademark

*Tear out coupon and mail today!*

CENTRALAB, A Division of Globe-Union Inc.  
911G E. Keefe Avenue, Milwaukee 1, Wisconsin

Send me free copy of Centralab Catalog No. 29.

Name.....

Address.....

City.....Zone.....State.....

G-3254B




# PRECISION COMPONENTS tuned to tomorrow


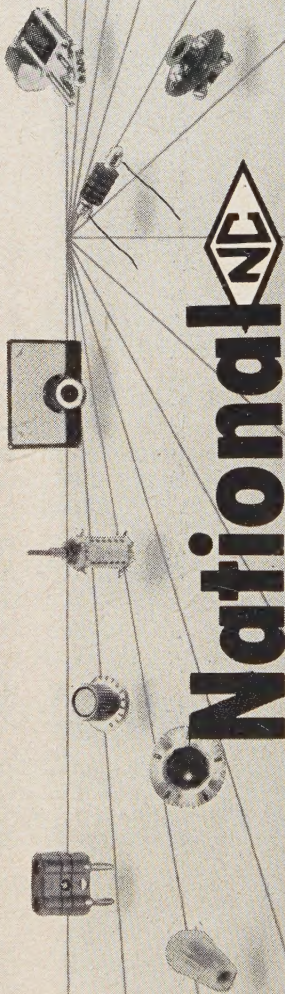
## NEW CATALOGS

Write on your business letterhead, (or give your amateur call sign) for your free copy of National's new catalogs of quality knobs, dials, drives, chokes, terminals, plugs, bindings, insulators, spreaders, couplings, tube caps, grips and sockets, coils, coil forms, condensers and multi-band tank assemblies. Specify items in which you are interested. Write to Dept. C-7.



# National

NATIONAL COMPANY, INC., 61 SHERMAN ST., MALDEN 48, MASS.

(from page 6)

she leeving we not knowing how to getting alon without her.

We arriving home at Itchi's ranch about dusk, ar as driving in driveway and alongside rubbish ca are seeing sumthing looking like my 6-Meter Bod legger Club Certifikat sticking out from rubbish ca. Are not humerus how eyes can deseiving ones Still, Scratchi are curryus, so going to see wh are sticking out of ashey can.

Sacramento Bullevard!! It are my 6-Meter Bod legger Club Certifikat. But how . . . it can't . . . last time this mornings it are hanging on wall i Hon. Shack. Shurely Hon. Ant Fuie are knoeing who committing such outrage. Are rushing lik madly into house and running up to Ant Fuie. B fore can getting word into sideways she telling m she happy I home, an acct. she wanting to show m how nice my shack are looking since she Sprin Homecleaning it. Are asking her howcomes wha persons are throwing away Hon. Certifikat. Sh saying sumthing about that old things and explai ing she using picshure frame for other purpose. Just then we cuming into shack.

Hon. Ed., you never seeing so many pickshures i life. All over wall are pickshures. Ant Fuie poin ing out pickshure of Hon. Grate-Grandfather Sak Hon. Grate-Uncle Messysuki, Hon. Grate-Grate Ar Tukisoy, and just then my eyes are looking over res of shack. Hon. Horror of Horrors!!! My shack! My nice dirty, messy, lived-in shack! What a catastrofe!

Furnitshure are moved all whichways. Operating table on rong-side room, with control wires danglin on floor. Antenna connecckshuns no longer going thr window, on acct. window are having pretty curtain over same. All a-c wiring I having run aroun room on thumbtacks are down and neatly coiled i corner. All nobbs of xmitter are neatly tied with ribbons, and all nobbs detooned and pointing sam way. All scrap-paper cleened off desk—my log for past to years—all gone! New reseever sitting o stand near window, drying. Are just evidently get ting fresh cote of lavender paint, to matching cur tains.

And, the wall where keeping QSL cards. Hol wall, inklooding cards, all freshly scrubbed. Al scrubbed so cleen that are no ink on QSL cards. Only printing left. Hon. Ed., what can saying? Wha can doing?

Respectively yours  
Hashafisti Scratchi


P.S. By chance, Hon. Ed., are not big inflewenshu man likesame you needing 1/c housekeeper. Are knoeing one who can cleening like furies are neet, hard worker. What you saying? Writ ing posthasty if needing. Money no object.

Hashafisti Scratch
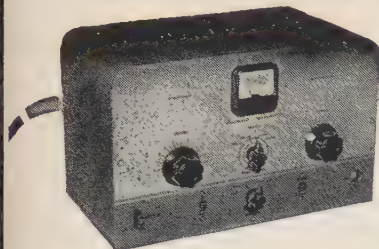
### Servo Controller Available

In response to several requests, the Editors have ascertained that the Harold H. Powell Co., 2102 Market St., Philadelphia 3, Pa. has a stock of the surplus Barber-Colman aYLC-5091 aircraft controllers. The most recently announced price was \$5.95. These units were utilized in the article by W2JKH (Nov., 1953, CQ, page 13) entitled, "Antenna Rotation with a Servo-Mechanism."





# Heathkit AMATEUR TRANSMITTER KIT

MODEL AT-1


**\$29<sup>50</sup>**

SHIPPING  
WT. 16 LBS.

Single knob  
band switching

Pre-wound coils —  
metered operation

52 ohm  
coaxial output

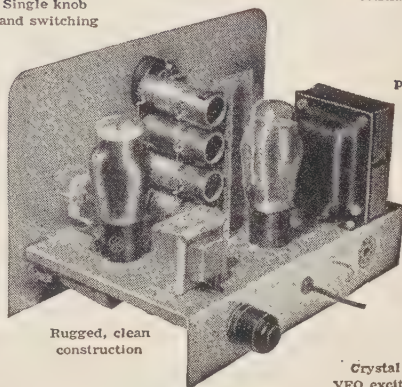

Built-in  
power supply

Rugged, clean  
construction

Crystal or  
VFO excitation

Range ..... 80-40-20-15-11-10 meters  
6AG7 ..... Oscillator - Multiplier  
6L6 ..... Amplifier - Doubler  
5U4G ..... Rectifier  
105-125 volts AC 50/60 cycles 100  
watts  
Size — 8 1/4" high x 13 1/4" wide x  
7" deep

Here is the latest Heathkit addition to the Ham Radio field, the AT-1 Transmitter Kit incorporating many desirable design features at the lowest possible dollar-per-watts price. Panel mounted crystal socket, standby switch, key click filter, AC line filtering, good shielding, etc. VFO or crystal excitation-up to 35 watts input. Built-in power supply provides 425V @ 100MA. Amazingly low kit price includes all circuit components, tubes, cabinet, punched chassis and detailed construction manual. (Crystal not supplied.)


## New HEATHKIT COMMUNICATIONS RECEIVER KIT

Four band operation  
535KC to 35MC

Electrical band  
spread and scale

RF gain control  
with AVC or MVC

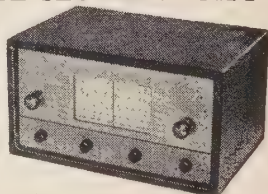Range.....535KC to 35MC  
12BE6.....Mixer oscillator  
12BA6.....IF amplifier  
12AV6.....Detector - AVC - Audio  
12BA6.....BFO oscillator  
12A6.....Beam power output  
5Y3GT.....Rectifier  
105-125 volts AC 50/60 cycles  
45 watts



MODEL AR-2


**\$25<sup>50</sup>**

SHIP. WT. 12 LBS.

CABINET

Proxylon impreg-  
nated fabric cov-  
ered plywood cabi-  
net. Ship. wt. 5 lbs.  
No. 91-10. **\$4.50**

Six tube trans-  
former operation

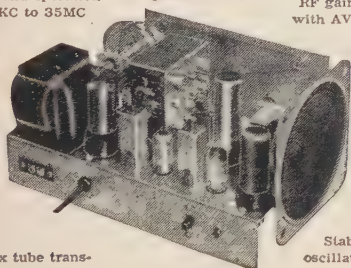

Stable BFO  
oscillator circuit

Noise limiter —  
standby switch


5 1/2" PM speaker —  
headphone jack

A new Heathkit AR-2 Communications Receiver. The ideal companion piece for the AT-1 Transmitter. Electrical band spread scale for tuning and logging convenience. High gain miniature tubes and IF transformers for high sensitivity and good signal to noise ratio. Construct your own Communications Receiver at a very substantial saving. Supplied with all tubes, punched and formed sheet metal parts, speaker, circuit components, and detailed step-by-step construction manual.

## THE IMPROVED Heathkit GRID DIP METER KIT

- Pre-wound coil kit
- Compact one hand operation
- Range — 2MC to 250MC
- Headphone monitoring jack
- Meter sensitivity control
- Transformer operated

The invaluable instrument for all Hams. Numerous applications such as pre-tuning, neutralization, locating parasitics, correcting TVI, etc. Receiver applications include measuring C, L, and Q of components, determining RF circuit resonant frequencies, etc. Thumbwheel drive for convenient one hand operation. All plug-in coils are wound and calibrated (rack included). Headphone panel jack further extends usefulness to operation as an oscillating detector.

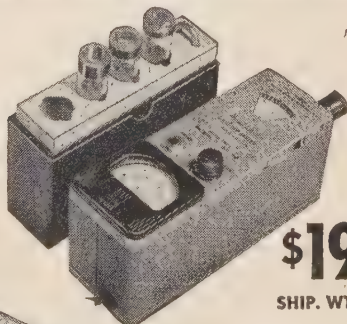MODEL  
GD-1A


**\$19<sup>50</sup>**

SHIP. WT. 4 LBS.

**HEATH COMPANY**  
BENTON HARBOR 6, MICHIGAN

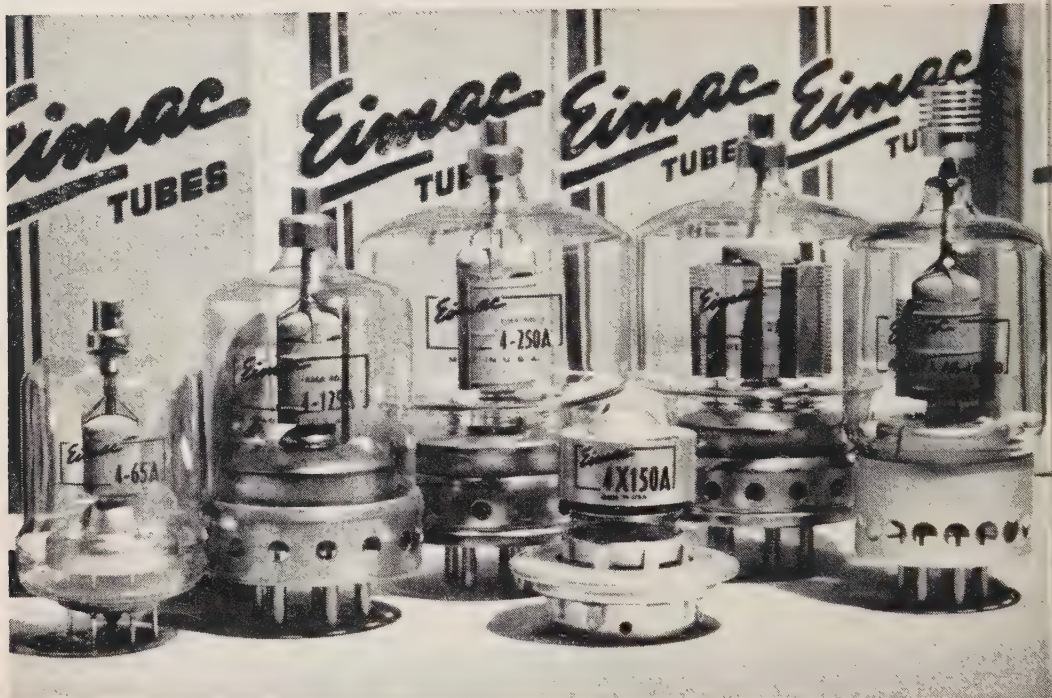Two additional plug-in coils are available and provide continuous extension of low frequency coverage down to 355KC. Dial correlation curves included. Shipping Wt. 1 lb. **\$3.00**  
Kit 841.





## For The CUSTOM Rig Take Your Pick From The Eimac Big Six

Eimac Big Six tubes incorporate the features famous in all Eimac multi-grid tubes and the experience of proven performance in all types of commercial, military and amateur application. Whether phone or CW, DSB or SSB, 160 meters or two meters, mobile or shack, there's an Eimac Big Six tube to do the job with a wallop. In planning a new rig or rebuilding, think of the six incomparable features of Eimac Big Six tubes: 1) Low driving power and high power gain 2) Low grid-plate capacitances and low inductance leads 3) Simple circuit needs 4) Easy TVI suppression 5) Pyrovac plate and non-emitting grid wire and 6) Unmatched reliability and performance. To be sure of Eimac quality ask your distributor for Eimac—the mark of excellence in electron power tubes for twenty years.

### EIMAC BIG SIX Radial-Beam Power Tubes TYPICAL OPERATION

	Class-C Telephony or FM Phone		AM Phone	
	Driving Power	Power Input	Driving Power	Power Input
4-65A	1.7w	345w	1.9w	270w
4-125A	2.5w	500w	3.3w	380w
4-250A	2.6w	1000w	3.2w	675w
4-400A	6.1w	1000w	3.5w	1000w
4X150A	1.0w	200w	2.0w	200w
4E27A	1.6w	500w	2.0w	380w

For additional information write  
our Amateurs' Service Bureau.



EITEL-McCULLOUGH, INC.  
SAN BRUNO, CALIFORNIA

Export Agents: Frazar & Hansen, 301 Clay St., San Francisco, California



# Zero Bias...

## Read This Before Going Any Further In CQ

This may be the most important Docket issued by the FCC on the regulation of Amateur Radio

This is a notice of proposed rule making Docket 11060 in the matter of amendment of Part 12 of the Commissions rules concerning eligibility to hold amateur radio operator licenses.

1. Notice is hereby given of proposed rule making in the above entitled matter.

2. In accordance with the Commission's statutory authority to prescribe the qualifications of amateur radio operators, the Commission proposes to amend *Section 12.21* of its rules so as to make ineligible to hold an amateur radio operator's license any person who is a member of the Communist Party, of any organization which has been required to register as Communist-action or Communist-front organization under the provisions of the *Internal Security Act of 1950 (50 USC786)*, or any organization which advocates or teaches the overthrow of the United States Government or the Government of any sub-division thereof by force or violence.

3. It is also proposed to amend *Section 12.21* so as to provide that only a person of good moral character will be eligible to hold an amateur radio operators license. Factors which the Commission proposes to consider in determining the character qualifications of applicants for amateur radio operators license include:

(1) Whether or not the person has been a member of the Communist Party or any organization which has been required to register as Communist-action or Communist-front organizations under the provisions of the Internal Security Act of 1950, or any organization which advocates the overthrow of the Government by force or violence;

(2) Whether or not the person has been convicted of any crime which is a felony under the laws of the jurisdiction in which the conviction was secured.

4. In addition, it is proposed to amend the forms for applying for amateur radio operators licenses to include questions with respect to membership in organizations which teach or advocate the overthrow of the Government by force or violence, to provide that all applicants

must submit finger prints with their applications and to provide that holders of amateur radio operators licenses shall be required to answer questions from the Commission during the terms of their licenses concerning any of the eligibility sections set forth in the Commission rules.

5. (This section omitted by editor as it deals with authority of the FCC to make this rule—o.p.f.)

6. Any interested party may file with the Commission on or before July 19, 1954 a written statement or brief setting forth comment in favor or opposed to the proposed amendment. The Commission will consider all such comments, briefs, or statements before taking final action. If any comments are received which appear to warrant the Commission in holding Oral Argument before the final action is taken, notice of the date and place of such oral argument will be given.

7. In accordance with the provision of Section 1.764 of the Commission Rules, an original and 14 copies of all statements, briefs, or comments shall be furnished the Commission.

Adopted June 10, 1954

Released June 11, 1954

(Applies to all class of licenses)

Signed:

Federal Communications Commission  
Mary Jane Morris, Secy.

This material was received via telephone on 14 June 1954 and is not a complete verbatim copy of Docket 11060. This material is, however, a full account of the important sections. Note particularly that all Amateur Radio Operators would be finger printed and that they must be ready to answer questions (unidentified, but assumed to be related to this Docket), at any time during the term of their license. No quarrel or objection can be raised with the provisions that would preclude the granting of a license to a known Communist. However, it is the reaction of this editor that the Docket does not sufficiently spell out the extent to which this authority would be carried. It is my hope that by the time you read this the ARRL will have taken action to set the closing date for filing comments further away, or will have appealed for an oral hearing. This Docket provides too many sweeping powers through its loose wording.

o.p.f.



# Sooner or later you'll want COLLINS amateur radio equipment



... so why not see  
your authorized  
COLLINS distributor  
right away

## ALABAMA

BIRMINGHAM  
Ack Radio Supply Co.  
3101 Fourth Ave. S.

## ARIZONA

PHOENIX  
Radio Parts of Arizona  
214 S. 11th St.

## ARKANSAS

LITTLE ROCK  
David White Radio Co.  
1222 Main St.

## ARKANSAS-TEXAS

TEXARKANA  
Lavender Radio Supply  
Co., Inc.  
520 E. Fourth St.  
P. O. Box 596

## CALIFORNIA

BURBANK  
Valley Electronic Supply  
1302 W. Magnolia Blvd.

LONG BEACH  
Scott Radio Supply  
266 Alamitos Ave.  
Larry Lynde Electronics  
1526 E. 4th St.

LOS ANGELES  
Henry Radio  
11240 W. Olympic Blvd.  
Kierulff & Co.  
820-830 W. Olympic Blvd.

OAKLAND  
Elmar Electronics  
140 — 11th St. at Madison

SAN DIEGO  
Western Radio & TV  
Supply Co.  
1415 India St.

SAN FRANCISCO  
San Francisco Radio &  
Supply Co.  
1282-1284 Market St.

## COLORADO

DENVER  
Radio Products Sales Co.  
1237 Sixteenth St.

## CONNECTICUT

NEW HAVEN  
Dale Electronic Dist.  
150 James St.

## DELAWARE

WILMINGTON  
Radio Electric Service Co.  
of Pa., Inc.  
S.E. Corner Third &  
Tatnall Sts.  
Wilmington Electrical  
Spec. Co., Inc.  
405 Delaware Ave.

## DISTRICT OF COLUMBIA

WASHINGTON  
Electronic Wholesalers, Inc.  
2345 Sherman Ave., N.W.

## FLORIDA

JACKSONVILLE  
Kinkade Radio Supply  
1402 Laura St.

MIAMI  
Electronic Supply Co.  
61 N.E. 9th St.  
Walder Radio &  
Appliance Co.  
1809 N.E. 2nd Ave.

TAMPA  
Kinkade Radio Supply  
1707 Grand Central

WEST PALM BEACH  
Goddard Distributors, Inc.  
1309-11 N. Dixie

## GEORGIA

ATLANTA  
Specialty Distributing Co.  
425 Peachtree St., N.E.

AUGUSTA  
Specialty Distributing Co.  
644 Reynolds St.

SAVANNAH  
Specialty Dist. Co.  
411 E. Broughton St.

## ILLINOIS

CHICAGO  
Allied Radio Corp.  
100 N. Western Ave.  
Newark Electric Co.  
223 W. Madison St.

PEORIA  
Klaus Radio & Electric Co.  
707 Main St.

ROCK ISLAND  
Tri-City Radio Supply Co.  
1919 Fourth Ave.

## INDIANA

FT. WAYNE  
Ft. Wayne Electronics  
Supply, Inc.  
223 E. Main St.

INDIANAPOLIS  
Graham Electronic  
Supply, Inc.  
102 S. Pennsylvania St.

LAFAYETTE  
Lafayette Radio Supply, Inc.  
627 Main St.

MUNCIE  
Muncie Electronics  
Supply, Inc.

SOUTH BEND  
Radio Distributing Co.  
432 Carroll St.

## IOWA

COUNCIL BLUFFS  
World Radio Laboratories,  
Inc.

3415-27 W. Broadway  
DES MOINES  
Radio Trade Supply Co.  
1224 Grand Ave.

## KANSAS

TOPEKA  
The Overton Electric Co.,  
Inc.  
522 Jackson St.

## KENTUCKY

LEXINGTON  
Radio Equipment Co.  
480 Skain Ave.

## LOUISIANA

NEW ORLEANS  
Radio Parts, Inc.  
807 Howard Ave.

## MARYLAND

BALTIMORE  
Kann-Ellert Electronics, Inc.  
9 South Howard St.

## MASSACHUSETTS

BOSTON  
DeMambro Radio Supply,  
Inc.  
1095 Commonwealth Ave.  
Radio Shack Corp.  
167 Washington St.



# DISTRIBUTORS NATIONWIDE . . .

## MICHIGAN

DETROIT  
M. N. Duffy & Co.  
2040 Grand River Ave., W.  
KALAMAZOO  
Warren Radio Co.  
1002 Adams St.

## MISSOURI

BUTLER  
Henry Radio Co.  
211 North Main  
KANSAS CITY  
Radiolab  
1612 Grand Ave  
ST. LOUIS  
Walter Ashe Radio Co  
1125 Pine St

## MINNESOTA

DULUTH  
Lew Bonn Co.  
228 E. Superior St.  
Northwest Radio  
123 E. First St.  
MINNEAPOLIS  
Lew Bonn Co.  
1211 La Salle Ave.  
ST. PAUL  
Lew Bonn Co.  
141-147 W. Seventh St.  
Hall Electric Co.  
566 N. Robert St.

## MONTANA

BILLINGS  
Electronic Supply Co.  
214 11th Street W

## NEW HAMPSHIRE

CONCORD  
Evans Radio  
10 Hills Ave.

## NEW JERSEY

ATLANTIC CITY  
Radio Electric Service Co.  
of Pa., Inc.  
452 N. Albany Ave.  
CAMDEN  
Radio Electric Service Co.  
of Pa., Inc.  
513-15 Cooper St

## NEW MEXICO

ALBUQUERQUE  
L. B. Walker Radio Co.  
114 W Granite Ave.

## NEW YORK

ALBANY  
Ft. Orange Radio Dis-  
tributing Co., Inc.  
642-644 Broadway  
AMSTERDAM  
Adirondack Radio Supply  
185-191 W. Main St.  
BUFFALO  
Genesee Radio & Parts Co.  
205 Genesee St.  
JAMAICA  
Harrison Radio Corp.  
144-24 Hillside Ave.  
NEW YORK  
Harrison Radio Corp.  
225 Greenwich St.  
Harvey Radio Co., Inc.  
103 W. 43rd St.

## NORTH CAROLINA

GREENSBORO  
Johannesen Electric Co., Inc  
312-14 N. Eugene St.

## OHIO

CINCINNATI  
Steinberg's Inc.  
633 Walnut St  
CLEVELAND  
Radio & Electronic Parts Co.  
3235 Prospect Ave.  
COLUMBUS  
Universal Service  
114 N. 3rd St  
DAYTON  
SREPCO, Inc.  
314 East Leo St.  
SPRINGFIELD  
SREPCO, Inc.  
119 W Main St.  
TOLEDO  
Selectronic Supplies, Inc.  
1320 Madison Ave.

## OKLAHOMA

TULSA  
Radio, Inc.  
1000 S. Main St

## OREGON

PORTLAND  
Pacific Stationery  
Wholesale Radio Dept.  
414 S.W. Second Ave

## PENNSYLVANIA

ALLENTOWN  
Radio Electric Service Co  
of Pa., Inc.  
1042 Hamilton St.  
EASTON  
Radio Electric Service Co  
of Pa., Inc.  
916 Northampton St  
JOHNSTOWN  
Cambria Equipment Co  
17 Johns St.  
PHILADELPHIA  
Radio Electric Service Co  
of Pa., Inc.  
3412 Germantown Ave.  
Radio Electric Service Co.  
of Pa., Inc.  
5930 Market St.  
Radio Electric Service Co  
of Pa., Inc.  
N.W. Corner 7th & Arch Sts.  
PITTSBURGH  
Cameradio Co  
1211 Penn. Ave.  
Keps Electric Co  
5800 Baum Blvd.  
READING  
George D. Barbey Co., Inc.  
155-157 Penn St.

## RHODE ISLAND

PROVIDENCE  
W. H. Edwards Co.  
94 Broadway

## SOUTH DAKOTA

ABERDEEN  
Burghardt Radio Supply  
P. O. Box 342

## WATERTOWN

Burghardt Radio Supply  
P. O. Box 41

## TENNESSEE

CHATTANOOGA  
Curle Radio Supply  
439 Broad St.  
Specialty Distributing Co  
709 Chestnut St.  
JACKSON  
L. K. Rush Co.  
P. O. Box 1418  
MEMPHIS  
Lavender Radio Supply Co.  
Inc.  
1014-16 Union Ave.  
W & W Distributing Co  
639 Madison Ave.

## TEXAS

AUSTIN  
The Hargis Co  
P. O. Box 716  
706 W. 6th St.  
CORPUS CHRISTI  
Electronic Equipment &  
Engineering Co  
805 S. Staples St  
DALLAS  
Crabtree's Wholesale Radio  
2608 Ross Ave  
EL PASO  
C. C. McNicols  
811 Estrella  
HOUSTON  
Busacker Electronic  
Equip. Co.  
1721 Waugh Drive  
SAN ANTONIO  
Amateur Headquarters &  
Supply  
P. O. Box 5086  
Beacon Hill Station  
TYLER  
Lavender Radio Supply Co  
Inc.  
503 E. Oakwood

## UTAH

OGDEN  
Iverson Radio Co  
265 — 25th St.  
SALT LAKE CITY  
Standard Supply Co.  
531 S. State St.

## VIRGINIA

NORFOLK  
Radio Equipment Co.  
821 W 21st St.

## WASHINGTON

SEATTLE  
Western Electronic Supply  
Co.  
717 Dexter  
TACOMA  
C & G Radio Supply Co.  
2502-6 Jefferson Ave.

## WISCONSIN

MADISON  
Satterfield Radio Supply, Inc.  
326 W. Gorham St.  
MILWAUKEE  
Central Radio Parts Co.  
1723 W. Fond du Lac Ave.

# COLLINS RADIO COMPANY

Cedar Rapids, Iowa

11 W. 42nd Street  
NEW YORK 36

1930 Hi-Line Drive  
DALLAS 2

2700 W. Olive Avenue  
BURBANK

COLLINS RADIO COMPANY OF CANADA, LTD.  
74 Sparks Street, OTTAWA, ONTARIO





# Cavity TVI Filter

ROBERT SCHLESINGER, K2CWO

1009 Madison St., Syracuse, N.Y.

**A Radical Departure in the Field of TVI Suppression. This Easily Constructed Filter Passes Only the 144-Mc. Band, Attenuating Those Frequencies Above and Below**

The use of filters in the output of 2-meter transmitters has been generally limited to the low-pass type. The low-pass filter, of course, does nothing to suppress the 48 or 72 Mc. signals that invariably appear in the output, in varying degrees, as the result of the transmitter multipliers. These signals can be the source of v-h-f TVI in the sets of neighbors by mixing in the front end and ending up on a channel frequency. For example, the 4th harmonic of 48 Mc. is 192 Mc. or Channel 10. The harmonics resulting from multiples of the fundamental 144-Mc. signal can cause interference both in the VHF and UHF TV bands. It therefore becomes apparent that a band-pass filter would be far more desirable to use than a filter of the low-pass type.

One form of a band-pass filter in common use at ultra-high frequencies is the re-entrant cavity. These cavities are generally not employed below 500 Mc. due to the large physical size needed at the lower frequencies. The design and use of these cavities is little known to the 2-meter enthusiast. Many of those who are familiar with this technique have discarded it on the grounds that the construction problem is too cumbersome. In reality, however, the design of these cavities is quite simple.

The two major considerations of such a filter are:

1. Its band-pass characteristics.
2. Its insertion loss.

If the cavity must be electrically foreshortened with a large loading capacity, it was felt that the first of the above points might be adversely affected. Also since the material used in the construction of tin cans is not recommended for r-f work it was felt that perhaps the second point, the insertion loss, might be too great. However, we designed, built and tested one of these cavities using an ordinary large size (1.44 qt.) orange juice can, with very encouraging results.

## Theory of the Re-entrant Cavity

We will outline the theory of the design procedure so that the builder will have the background necessary to use any available type of

cylindrical can and will not be confined to the exact type used in this article. As a matter of fact there may be some advantage in using so large paint cans if space permits.

An optimum  $Q$  is equal to the ratio of  $b$  of 3.6 (see Fig. 1). For any can of given diameter we may determine the inner conductor by letting  $a = b/3.6$ . Notice that  $a$  and  $b$  radii and must be multiplied by 2 to give correct diameter. Remember that we deal with the outside diameter of the inner conductor and inside diameter of the outer conductor.

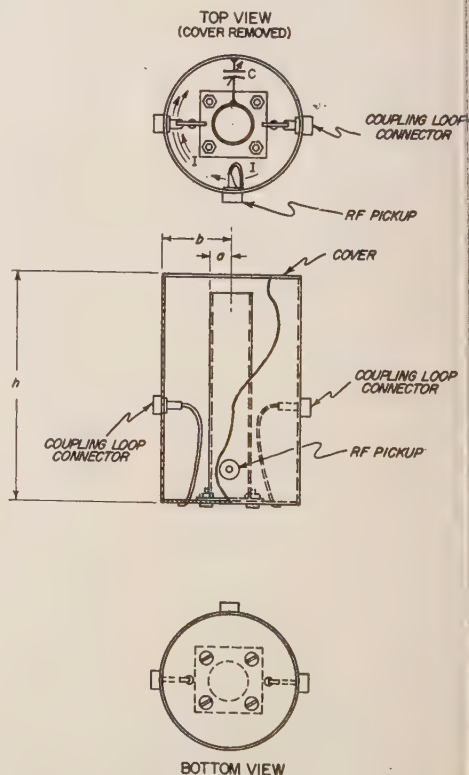


Fig. 1. The re-entrant cavity filter makes use of distributed constants rather than lumped circuit constants to tune to the 144-Mc. band.



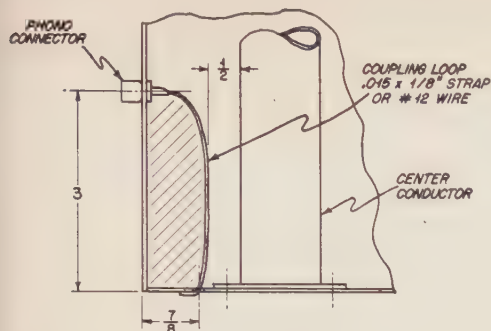


Fig. 2. The coupling loops are rigidly mounted inside the cavity. The proximity of the loop to the center conductor and the pickup area (shaded) determine the amount of coupling. See text for details.

The can we chose had an O.D. of 4.25 inches therefore,  $2a = 4.25/3.6 = 1.18$  inches. Since a piece of brass pipe 1.25 inches in diameter was on hand this was used for the center conductor.

The surge impedance of a cylindrical concentric line cavity with air dielectric is  $Z_o = 138 \log 10 \times b/a$ , where  $b$  and  $a$  are the respective radii just referred to. For a ratio of  $b/a = 3.6$ ,  $Z_o = 77$  ohms. This will give an unloaded  $Q$  in the order of 5000,\* depending on the exact material from which the can is made. Although it was not found necessary, silver plating will increase the  $Q$  considerably.

The next step is to determine the necessary loading capacity to make the cavity look like an electrical quarter wave at the middle of the band. This is only necessary if the can is less than  $1/4$  wave length to begin with. A wave length being 81.5 inches, a quarter wave length is therefore 20.4 inches. The can we used was only 7 inches long. The capacitive reactance is given by:

$$X_o = Z_o \tan \beta \eta \text{ where:}$$

$$\beta = 360^\circ$$

$$\eta = h/\lambda = 7/81.5$$

$$Z_o = 77 \text{ ohms}$$

$$\text{Hence } X_o = 77 \tan 360 (7/81.5) = 46 \text{ ohms}$$

The capacity needed is therefore:

$$C = \frac{1}{2} \pi f X_o$$

$$= \frac{1}{2} \pi \times 146 \times 10^6 \times 46$$

$$= 23.5 \mu\text{fd.}$$

This capacity electrically appears as  $C$  in Fig. 1 and physically is connected from the non-grounded end of the center conductor to the can wall. In theory it would be desirable to have this multi-path return. This, however, is not physically possible, so that the best that can be done is to use good r-f connections at each side of the condenser. Actually, we used a small Johnson type 20M11 miniature condenser rated at 19.7  $\mu\text{fd.}$  maximum, and a little cera-


mic tuner of 1.5-7  $\mu\text{fd.}$  diagonally opposite to give some vernier tuning to the cavity. These condensers were used successfully with a transmitter rated at 62 watts input to the final. With transmitters running higher power inputs, heavier condensers might be needed. This is due to the fact that a high voltage is developed across the cavity at this point, just as high voltage is developed across a parallel resonant circuit.

### Coupling Loop Details

The concentric current lines are shown in the top view of Fig. 1. The size of the shaded area in Fig. 2 will determine the degree of coupling. Maximum coupling would result if the dimension marked  $1/2$ " in Fig. 2 were reduced to zero since this would permit all the current circulating in the cavity to pass through the coupling loop.

The area of the coupling loop is not too critical and a close approximation of the dimensions shown on Fig. 2 for any can about the size of the one we used will give good results for 50-ohm or 75-ohm terminations. Do not try to make the coupling too tight since this will result in capacitive coupling rather than inductive coupling. Both coupling loops are identical in construction. Electrically the cavity is a bilateral network when loaded into 50 ohms. It makes no difference which side is connected to the transmitter or to the load.

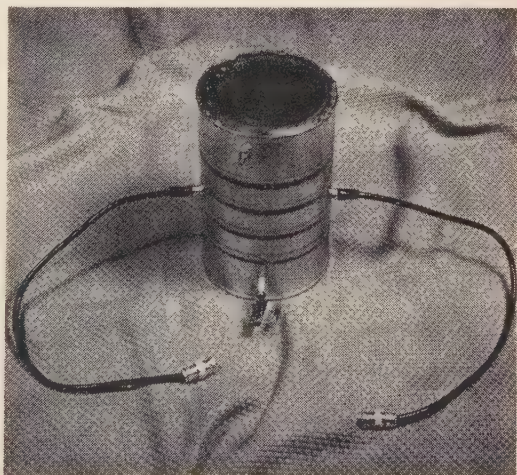With the coupling loop shown in Fig. 2 the insertion loss of the cavity is 0.4 db. If the builder desires to make a cavity whose dimensions are greatly different from the ones we used, the insertion loss is one criterion by which he can adjust to the proper degree of coupling. A figure between 0.3 and 0.6 db. insertion loss is desirable since an insertion loss of less than



This is the complete cavity with the top resoldered in place. The cavity is bilateral and either side may be used as the input or output. The r-f probe assembly is shown in the foreground. This is a useful indication device when the cavity is installed in the feedline.

\* Terman, "Radio Engineer's Handbook," p. 192.



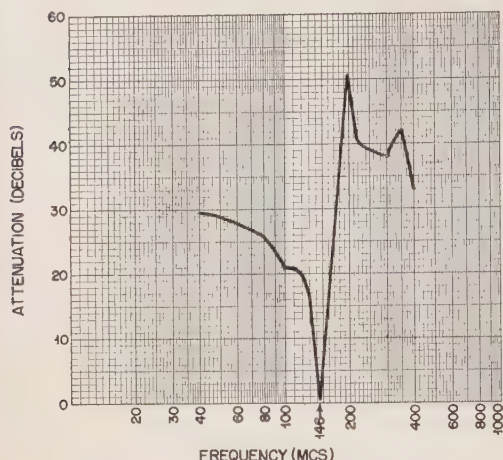


Fig. 4. This graph shows the attenuation above and below the 2-meter band. Note the absorption in the range of TV channels 7 through 13.

0.3 db. will result in the over-coupling difficulties mentioned above.

The exact method of measuring the insertion loss, although quite simple, requires some means of measuring antenna power. We had available a *Bird Termaline* wattmeter which is a good 50-ohm resistive load at this frequency.

To determine the insertion loss when power is the measured quantity proceed as follows:

$$\text{Insertion loss in db.} = 10 \log_{10} P_1/P_2$$

where  $P_1$  = power with no filter

$P_2$  = power with filter

in our case for final adjustment  $P_1 = 40$  watts  
 $P_2 = 36$  watts

$$\text{db.} = 10 \log_{10} 40/36 = 4 \text{ db.}$$

It is therefore obvious that the losses within the cavity is 4 watts. In terms of S-units this is  $4/6 = .666$  S-units.

This same procedure could be followed using voltage, if one has available a pure 50-ohm load resistor at 146 Mc. and an r-f voltmeter capable of accurate measurement at this frequency. In this case,  $\text{db.} = 20 \log_{10} V_1/V_2$ . Here  $V_1$  is the voltage across the resistor without the filter and  $V_2$  is the voltage with the filter inserted.

### Tuning the Cavity

The problem of knowing when the cavity is tuned to resonance once it is connected to the transmitter and antenna is solved by the inser-


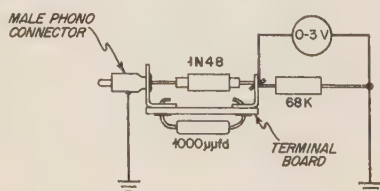


Fig. 3. Some of the r-f in the cavity may be sampled to enable tuning and later to monitor your "on-the-air" transmissions.

tion of a small r-f pick-up loop and crystal detector. The circuit is shown in Fig. 3. A female phono-connector was used to mount the pick-up loop in the side of the cavity. It should be placed one inch from the bottom of the cavity and mid-way between the axis passing through the two coupling loops. The size of the pick-up loop should be kept as small as possible so as not to absorb any power. We were able to solder a wire from the center conductor of the female phono-connector back to its outside case and get a 1-volt reading on the 3-volt scale of a 20,000 ohms-per-volt voltmeter at 40 watts to the antenna when the cavity was tuned correctly. The reading of the meter may be increased or decreased as needed, depending on the transmitter power, by changing the size of the loop, changing the 68K. resistor or changing the orientation of the loop with respect to the

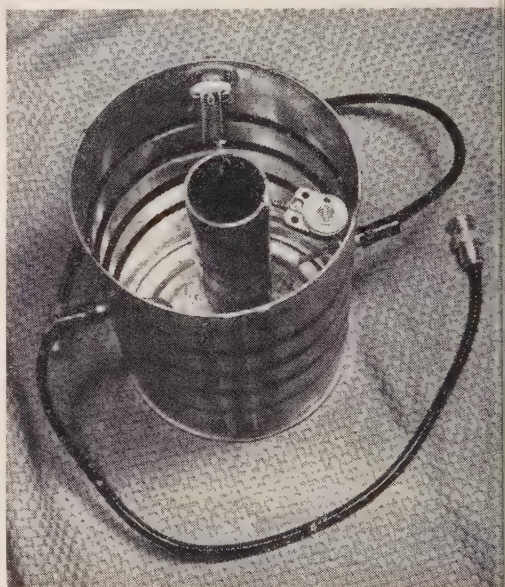

Looking down into the cavity the two variable capacitors are visible. The air padder is used to approximately set the band and the ceramic is used as a vernier adjustment.

current passing through it. Be careful not to exceed rated crystal current for the type of crystal used. The detector unit may be left in at all times or removed after the cavity is tuned. If left in and metered it makes a good indicator of transmitter output to the antenna.


All connectors are inexpensive little phono plugs and seem to have a very low VSWR when used with RG-58/U up to 500 Mc. In fact they are very much better than some u-h-f connectors at frequencies above 200 Mc.

### Assembling the Cavity

The mechanical work requires that the center conductor be fastened to the bottom of the can. This we did by soldering it to a little flange

(Continued on page 52)



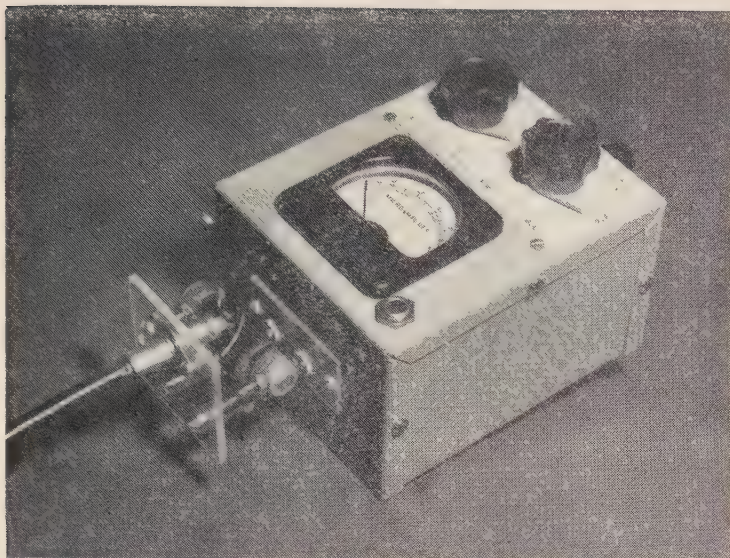

# Antennascope-54

WILFRED M. SCHERER, W2AEF

Contributing Editor

## Part Two of a Two Part Article


In the first part of this article, which started on page 23 of the June, 1954, issue of *CQ*, I described the construction of the *Antennascope-54*. In this part, I shall describe the simplified *Antennascope Jr.* and some of the many uses of both instruments.

The *Antennascope Jr.* performs essentially the same functions as the *Antennascope-54*. However, it incorporates only one impedance range, and it is designed to be used with an external indicating meter.

Referring to Fig. 1, when *R1* has a maximum resistance of 500 ohms, the impedance range of the *Antennascope Jr.* is 10 to 500 ohms, but the scale becomes quite crowded at the low-resistance end. *R1* may be made 100 ohms in an instrument which will be used exclusively with low-impedance loads. The more sensitive the meter used with the *Antennascope Jr.*, the better. A 20,000 ohms-per-volt multimeter set on its lowest d-c voltage range works excellently.

### Constructional Details

Figure 2 makes step-by-step building instructions unnecessary. Follow this layout closely, and you will have no trouble. Note carefully the mounting of *R1*. It is mounted upon a block of polystyrene (part *B*), which is supported 1/4-inch away from the top of the metal box by means of two 6-32 screws through the

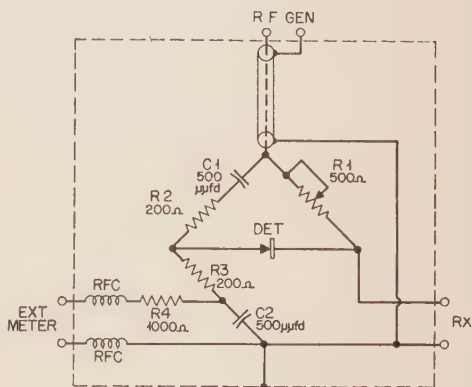

NOTE:  
R1 MAY BE 100, 250 OR 500 OHMS. (SEE TEXT)  
RFC IS 2.5 MH CHOKE, OTHER CONSTANTS ARE SAME  
AS IN STANDARD MODEL.

Fig. 1. Wiring schematic and parts list of the *Antennascope Jr.* This unit is designed for use with an external meter.

- C1, C2—500 to 1000  $\mu$ fd. "buttons." Exact capacity unimportant, but must be matched. Centralab ZA-751.
- R1—100-ohm or 500-ohm potentiometer. Allen Bradley J or Ohmite AB. See June text for choice of resistance.
- R2, R3—200 ohms, 1/2 w. non-inductive. Exact resistance is not

- critical, but resistors must be matched.
- R4—1,000 ohms, 1/2 w.
- RFC1, RFC2—2.5 mh., 50 ma. r-f chokes.
- Det—G.E. G7A or Sylvaria 1N23B crystal diode.
- External meter—50 to 200  $\mu$ a. range. (See text).
- Built in 2 1/4 x 2 1/4 x 4-inch Minibox.



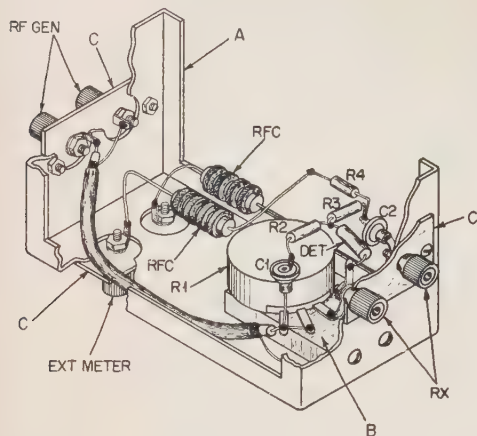


Fig. 2. Internal wiring view of the Antennascope Jr. described in this text.

end of the box into tapped holes in the end of the polystyrene. It is hardly necessary to stress the importance of short leads, which Fig. 2 makes obvious.

Upon completion of the instrument, test and calibrate it as described last month.

### Using Either Model Antennascope

The *Antennascope-54* and the *Antennascope Jr.* may be used for every purpose for which a fixed-ratio, r-f resistance bridge may be used. It can also be used for determining the resonant frequencies of antennas and feed lines, antenna radiation resistance, the *Velocity-of-Propagation* factor of feed lines, standing-wave ratios, and the input impedances of receivers, to name but a few.

The *Antennascope* is conveniently used in conjunction with a grid dipper by virtue of the latter's wide frequency coverage and portability, although it may be used with any r-f generator covering the desired frequency range at a power level not exceeding one watt.

Couple the *Antennascope* inductively to the r-f generator, which will be called the "Dipper" in the following discussion. Coupling should be sufficient to develop a full-scale meter reading with the *Rx* terminals open and *R1* set approximately to the expected impedance of the device being tested. One turn around the




*Dipper* coil should be sufficient above 15 Mc; Two or three turns may be required on lower frequencies.

Sometimes, when varying the coupling between the *Dipper* and the *Antennascope*, an apparent variation in the measured impedance occur. This is an indication of excessive capacity coupling. One cure is to use an electrostatically shielded coupling loop.<sup>1</sup> Another is a coupling transformer with an electrostatic shield between the windings. See Figs. 3 and 4.

Transformer coupling is especially helpful when working with balanced lines. In addition, the *Antennascope* and the line should be isolated from ground and large masses of metal to reduce capacity unbalance. It is also helpful to put a loose twist in the line about every two feet. Always connect the shield of coaxial line to the grounded *Rx* terminal.

For maximum accuracy, always check the actual frequency of the *Dipper* by monitoring it on a calibrated receiver. Also, in adjusting the *Antennascope* to produce a null, it may be necessary to retune the *Dipper* a trifle, to compensate for slight frequency shifts resulting from varying load. Incidentally, variations of the meter on the *Dipper* have no significance in this application. However, when a null has been achieved on the *Antennascope*, glance at the *Dipper* meter to be sure that overcoupling has not pulled the current down to zero. If it has, slightly loosen the coupling.

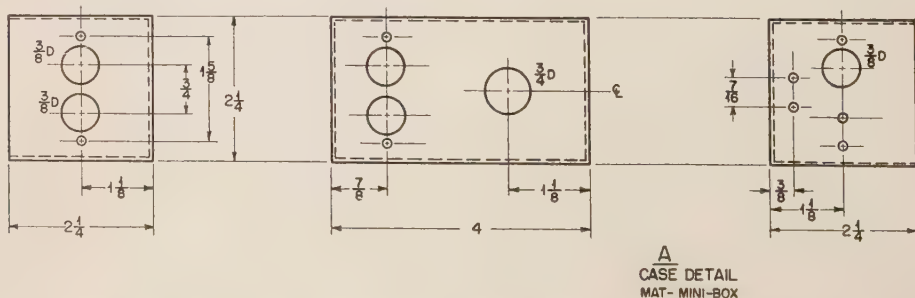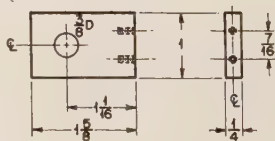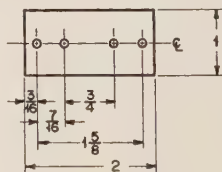1. Robberson, "Faraday Shield for the Antennascope," CQ, Feb., 1954, p. 50.



Layout drawings of the Antennascope Jr. chassis box and mounting strips of polystyrene.



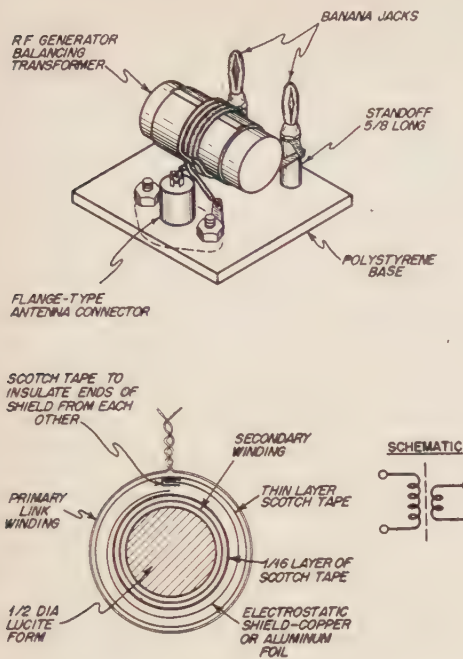


Fig. 3. Detail of the electrostatic coupler. Use 3 or 4 turns on the primary and 25 turns on the secondary depending on frequency.

### Determining Feed Line Characteristics

**QUARTER-WAVE LINES:** Set  $R1$  to "0" and with the  $Rx$  terminals open, adjust coupling to the *Dipper* for full-scale meter deflection. Connect the line to the  $Rx$  terminals. Leave the opposite end of the line open. Tune the *Dipper* to the lowest frequency which produces a complete null on the meter.

At this frequency, the line is electrically  $\frac{1}{4}$ -wavelength long. Its dimensions will satisfy the formula:

$$F_{Mo} = 246 / L_{ft} \times V.P. \quad (1)$$

when  $F_{Mo}$  is the frequency,  $L_{ft}$  is the line length, and  $V.P.$  is the line Velocity-of-Propagation factor.

Any fittings to be used on a line being resonated for a specific purpose should be in place, because they may affect the electrical length on the higher frequencies.

Nulls will also be found at odd integral multiples of the frequency just determined, because any resonant line "repeats" itself every electrical half wave. The same effect will occur if the frequency is held constant and the line length is multiplied.

**IMPEDANCE TRANSFORMATION IN QUARTER-WAVE LINES:** Leave the *Dipper* set at the null frequency and connect a non-inductive resistor across the output end of the line. Rotate  $R1$  for a new null, retuning the *Dipper* very slightly, if necessary.

The resistance shown on  $R1$  will be related to the test resistance in the following manner:

$$Z_s = (Z_o)^2 / Z_r \quad (2)$$

Where  $Z_s$  is the input resistance ( $R1$ ),  $Z_o$  is the line impedance, and  $Z_r$  is the terminating impedance (test resistance).

This formula reveals that a  $\frac{1}{4}$ -wave line always reflects to its input terminals a geometrical inversion, based upon the line impedance, of what is connected across its output terminals. This property is the basis of the operation of  $\frac{1}{4}$ -wave, linear matching transformers.

Formula (2) may be rewritten to solve for line impedance, thus:

$$Z_o = \sqrt{Z_s \times Z_r} \quad (3)$$

with the symbols having the same meanings as above.

Should it be impossible to obtain a null by rotating  $R1$ , the inverted impedance is probably beyond its range. Try a different value of test resistance. Suitable values when the approximate line impedance is suspected, are either half or double the estimated line impedance.

**HALF-WAVE LINES:** Duplicate the setup for finding the resonant frequency of a  $\frac{1}{4}$ -wave line, except that the output terminals are now shorted together. The lowest frequency at which a null can be obtained, with  $R1$  at "0" is the frequency at which the line is electrically  $\frac{1}{2}$ -wave long. Similar nulls will be found at integral multiples of this frequency.

The applicable formulas for calculating  $\frac{1}{2}$ -wave lines are:

$$L_{ft} = 492 / F_{Mo} \times V.P., \text{ or } F_{Mo} = 492 / L_{ft} \times V.P. \quad (4)$$

Substituting a non-inductive resistor for the short will require setting  $R1$  to its resistance value to produce a null. This proves that the load connected across the output terminals of a resonant line is repeated every  $\frac{1}{2}$  wave along the line.

**VELOCITY OF PROPAGATION:** The  $V.P.$  constant of a line can be determined by substituting the line length and the frequency in formulas (1) and (4) and solving for  $V.P.$  Rewritten, the

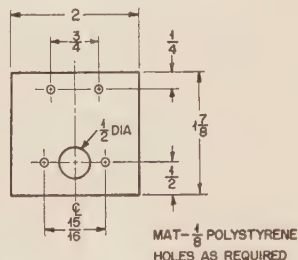


Fig. 4. Mounting for the electrostatic coupler. See the detail drawing above for further information.



become:

$$V.P. = F_{Mc} \times L_{ft}/246 \text{ (}\frac{1}{4}\text{-wave lines)} \quad (5)$$

$$V.P. = F_{Mc} \times L_{ft}/492 \text{ (}\frac{1}{2}\text{-wave lines)} \quad (6)$$

V.P. varies from about 0.95 for open-wire lines to about 0.68 for polyethylene-insulated coaxial line.

### Antenna Measurements

Although a *Dipper* may be used alone to determine antenna resonance, when combined with the *Antennascope* it will reveal the antenna radiation resistance at the same time.

**HALF-WAVE DIPOLES:** When the center of the antenna can be reached it may be checked as shown in Fig. 5. (June issue). Open the antenna in the center and connect in the *Antennascope* with very short leads. Support the instrument

tion, the length of a  $\frac{1}{2}$ -wave antenna reasonably in the clear is equal to:

$$L_{ft} = 492 \times 0.95 / F_{Mc} \quad (7)$$

When the center of the antenna cannot be reached, the scheme shown in Fig. 4b should be used. It is also recommended for use on frequencies above 75 Mc., where the presence of the equipment in the field of the antenna degrades the accuracy of the measurements. Use the *Antennascope* to cut a feed line to a length of a  $\frac{1}{2}$ -wave (or integral multiple thereof) at the desired frequency. Connect it between the antenna and the *Antennascope* and proceed as above.

If the antenna is too long, the *Antennascope* will null below the desired frequency. Conversely if the antenna is too short, the *Antennascope* will null above the desired frequency. Make appropriate adjustments in the antenna length to obtain a null on the desired frequency. Do not vary the line length for this purpose.

A line of any impedance may be used for this test, as long as it is an integral multiple of  $\frac{1}{2}$ -wave. Your regular feed line may be used if cut to the proper length. After the antenna is properly resonated, the line length can be increased or decreased as required to reach the transmitter.

Run the line at right angles to the antenna for at least  $\frac{1}{4}$ -wave before bending it. This will prevent the field of the antenna unbalancing the line and introducing errors. Line unbalance can be checked by reversing the connections to the Rx terminals. Little difference in readings should be observed.

**FOLDED DIPOLES:** Folded dipoles are adjusted in the same manner as other dipoles. Impedance to be expected will be between 100 and 400 ohms. Also, you may find a second null at a resistance of about 500 ohms and at a slightly different frequency. Referring to Fig. 4b, the length A determines the natural frequency of the antenna. But electrically the sections B and C resonate to a lower frequency, determined largely by the insulating material in the antenna.

This effect is unimportant in air-insulated folded dipoles. However, in 300-ohm ribbon dipoles the difference between the two null frequencies becomes quite pronounced. The result is that some of the broad-band characteristic of the antenna is lost.

One cure is to put the high-frequency null on the desired frequency and connect shorts across the antenna wires equally distant from each end to make the null frequencies coincide. The shorts are usually placed about 7 per cent of the antenna length from each end in 300-ohm folded dipoles.

**HARMONICALLY OPERATED ANTENNAS:** The current and impedance distribution of a harmonically-operated antenna changes from har-

(Continued on page ??)

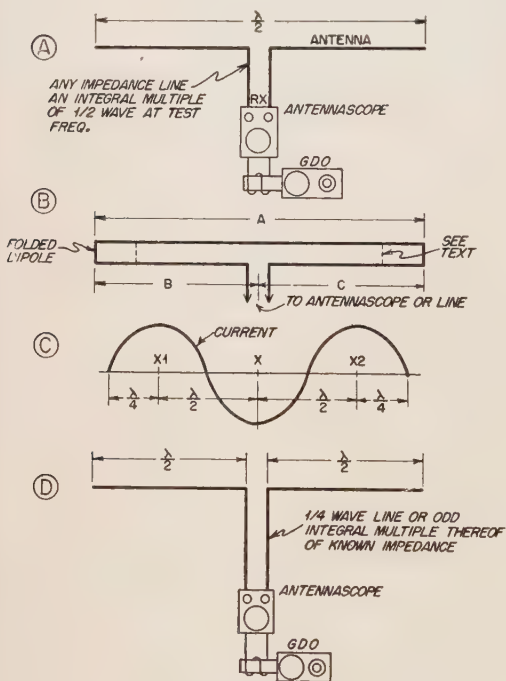


Fig. 4. These methods of using the Antennascope are explained in detail in this text.

by the connections, or tie it in place with stout cord. Do not hold it in your hand, as a serious unbalance will result.

Set *R1* to approximately 50 ohms and vary the *Dipper* frequency until the best null is obtained. Then adjust *R1*. Repeat the procedure until a complete null is obtained. The resonant frequency of the antenna is the frequency to which the *Dipper* is tuned, and its radiation resistance is read on *R1*.

The radiation resistance of a  $\frac{1}{2}$ -wave antenna runs between 10 and 100 ohms, depending upon its height above ground and its proximity to other objects. The same factors affect the resonant frequency. For a close approxima-



# Test Equipment.....

## ...in the Ham Shack

HOWARD BURGESS, W5WGF

925 Adams Street, S.E., Albuquerque, New Mexico

### Condenser Checkers

#### Part VI of This Series

Once upon a time, long, long ago, when radio was young, tubes were soft and Zepps hung high, condenser testing was a simple matter. With a pair of headphones and dry battery it was practiced somewhat like the lost art of watermelon thumping. One loud "click" meant it was good and the capacity was large. One weak "click" and the capacity was low. But a "plop" every time it was touched indicated a shorted capacitor.

In those days condensers were simple, too. There were the "big ones" and the "little ones." The big ones were hung across the B supply and the small ones were used to hold up the grid leak.

It seems that progress has its price, though, and today one instrument may have over a hundred capacitors ranging from the small ceramics of less than one micro-microfarad to electrolytics of more than 1000 microfarads. To add to the confusion, proper operation depends upon holding many of these components to close tolerance.


All of this adds up to the fact that although a condenser tester may not be as interesting as some pieces of test equipment, it is one of the more important pieces. Fortunately they are one of the simpler units to construct.

### How To Check a Capacitor

A number of methods have been devised for checking capacitors which include measuring the amount of alternating current of a known frequency which flows through the condenser at a given voltage. Another approach is to resonate the condenser with a known value of inductance. When the resonant frequency is found the capacity can easily be determined. A third method is the well-known bridge circuit. Because of the simplicity of the circuits involved, the wide range of values which it will measure, and the precision which can be obtained, this is the most widely used method of measurement.

Before going into the use of the bridge a few words regarding its operation may be of value to the beginning Ham. As shown in *Fig. 1* the bridge is essentially a pair of voltage dividers across a voltage source. When the resistors in one divider bear the same ratio to each other ( $R1$  to  $R2$ ) as the resistors in the other divider do to each other ( $R3$  to  $R4$ ) the voltage division will be the same in either divider regardless of the ohmic values used. The bridge is balanced, as shown in the diagram, because there is no voltage difference between  $A$  and  $B$  points.

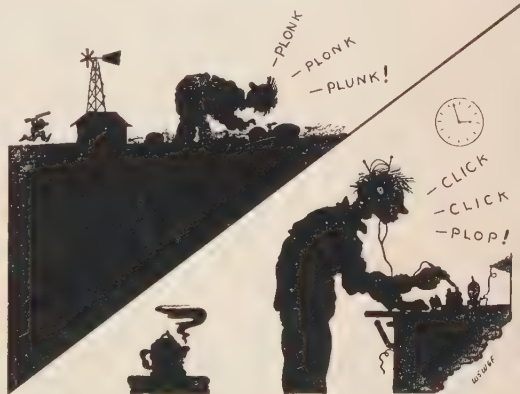In *Fig. 2* the circuit remains the same but a potentiometer has been substituted for  $R1$  and  $R2$ . In this way the ratio may be changed at will. If the value of  $R3$  is known then the value of any unknown inserted at  $R4$  is easily found.



"...condenser testing... was practiced somewhat like the lost art of watermelon thumping..."

If the pot is adjusted until there is no reading on  $V$  the bridge is balanced and  $R4$  bears the same relationship to  $R3$  as the corresponding sections of the potentiometer do to each other.

When condensers are connected in series in an a-c circuit the voltage drop across each condenser will be in proportion to its reactance. In *Fig. 3*, the resistors  $R3$  and  $R4$  have been replaced by  $Cs$ , which is a condenser of known value, and  $Cx$  which is an unknown. The voltage applied must now be a.c. The potentiometer can now be adjusted for a balance just as



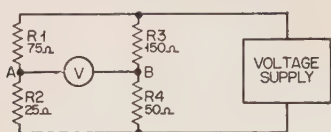


Fig. 1. The simple bridge is just a pair of voltage dividers.

in Fig. 2. This gives us a ratio between the unknown and a known value and our problem is solved.

This, then, is a condenser bridge in its simplest form. A pair of headsets can be substituted for the a-c voltmeter and the a-c supply may be a filament transformer. To make a more usable instrument several features should be added. As shown in Fig. 3 extremely small and very large values of capacity will be read so close to the ends of the potentiometer that the readings will be unusable for all practical purposes. To avoid this, several values of  $C_s$  are

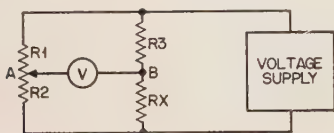


Fig. 2. A variable divider is substituted for one of the fixed dividers.

switched in for various ranges. This keeps the desired reading in the less cramped portion of the scale.

As shown in Fig. 4, another feature which should be added in  $R_3$ . In theory our condensers should contain only capacity and very little resistance. However, in practice many condensers, especially those of the electrolytic variety, contain considerable resistance in addition to capacity. This will reduce the efficiency of a condenser and make a true null impossible in the simple circuit. To get a good sharp null the same amount of resistance must be added at  $R_3$  as contained in the unknown  $C_x$ . This variable resistance is usually labeled "power factor" and will seldom be required except for electrolytics.

With the features we have added, the circuit of Fig. 4 will give a very good idea of the size

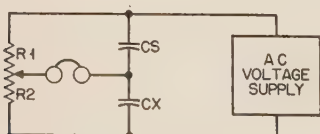


Fig. 3. Capacitors may be used as voltage dividers in alternating current circuits.

and worth of a condenser. Although nearly all of the common checkers use 60-cycle line voltage as the a-c source, a much better indication can be obtained on the smaller capacities if a higher audio frequency is used.

### Calibration

When a circuit such as this is constructed by the average Ham the problem of calibration rears its ugly head. In this case the calibration of the potentiometer will be non-linear. With several capacities of known value, an ohmmeter, and patience, the ratios can be worked

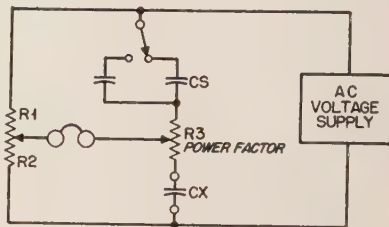


Fig. 4. This is the modification of Fig. 2 suitable for checking capacitors.

out and the scale plotted. If one is willing to add several more components to accomplish greater ease of calibration and a linear scale, the circuit may be altered to one such as that in Fig. 5. Electrically the circuit is the same but balance is accomplished in the  $R_1$  leg.

With this type of circuit the calibration scale is linear and the coverage of each range is determined by the ratio of the fixed resistor to the full range value of the variable. To illustrate, as shown the  $1K$  resistor is in the circuit. The variable  $R_1$  can be adjusted up to 10 times this value. Moving across to the capacity side, when

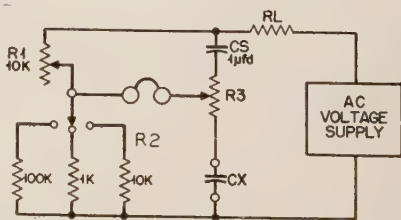


Fig. 5. These circuit revisions provide a linear calibration characteristic.

$R_1$  is 10 times  $R_2$ , the reactance of  $C_s$  will be 10 times that of  $C_x$  (assuming the bridge is balanced). Because capacity is inversely proportional to reactance, the largest condenser which can be measured with the taps shown will be  $10 \mu\text{fd}$ .

The resistor  $R_L$  is a limiting resistor. Without it, if the leads to  $C_x$  were to become shorted while  $R_L$  was in the position of minimum resistance, full a-c voltage would be applied to the indicating instrument or phones.



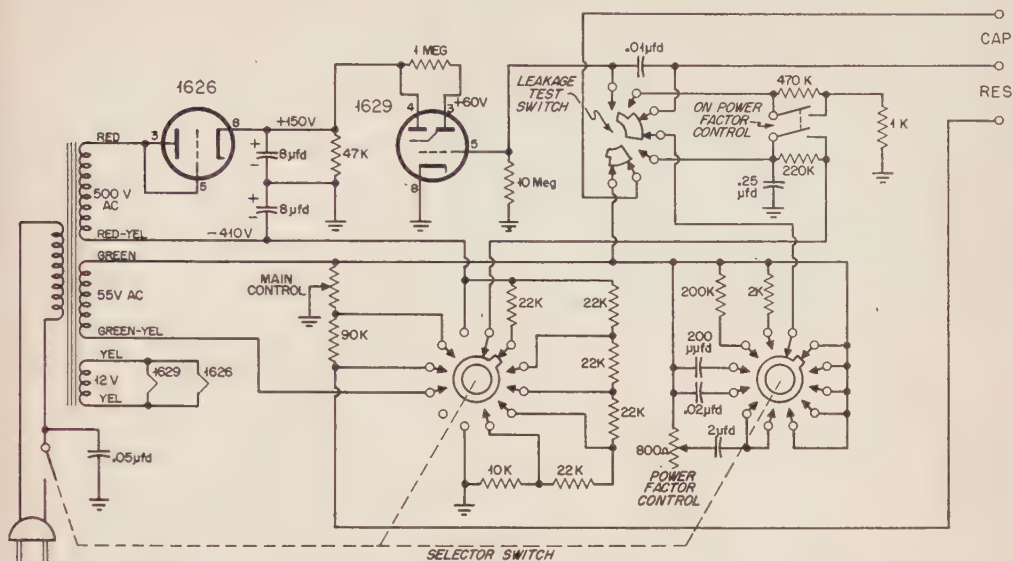


Fig. 6. Schematic of the Heathkit Model C-3 checker.

Of course there is the possibility that by now the reader has become discouraged by thoughts of calibration, power factor and the like, even though he may need just such a tester. In that case there is always the easy way out. By this we mean one of the ready-to-assemble kit versions of capacity bridges. After building many home style versions we have added one of the *Heathkit Model C-3* condenser checkers to our collection and are very well pleased with the results of this little unit.

### The Heathkit Model C-3

The schematic in Fig. 6 shows it to be similar to the type discussed in Fig. 5, with added features. The a-c voltage for the bridge proper is furnished from a winding on the power transformer. The null indicator is an electronic eye tube which is much more convenient to use than a pair of headphones. As to ranges, four switch positions give coverage from 10  $\mu\text{fd}$ . to 1000  $\mu\text{fd}$ . Included in the bridge are two resistance ranges spanning the range from 100 ohms to 5 megohms. These are just tossed in for free, but are mighty handy especially when the batteries in the ohmmeter go flat in the wee small hours, to say nothing of the fact that they are more accurate than most ohmmeters.

When checking electrolytic condensers a leakage test is very important. If the condenser has been on the shelf for some time without use it should be polarized before testing. Both of these functions have been included in this tester by incorporating a 450 volt d-c supply in the unit. Voltages such as 25-150-250-350 and 450 may be selected and placed on the condenser on test. This will show up any leakage as well as polarize or reform an electrolytic which has been idle.


In making this test the desired voltage is selected on the range switch. When this voltage is first applied to the condenser the eye will close momentarily but reopen if the condenser is good. A partial opening of the eye or continued fluttering indicates leakage or an intermittent short.

A power factor balance control such as mentioned in Fig. 4 is included in this instrument, and calibrated in percentage.

### Types of Condensers

In the selection and testing of condensers there are several factors which enter into their proper usage. Perhaps the greatest usage for a capacity bridge, in terms of quantity, is for

(Continued on page 55)

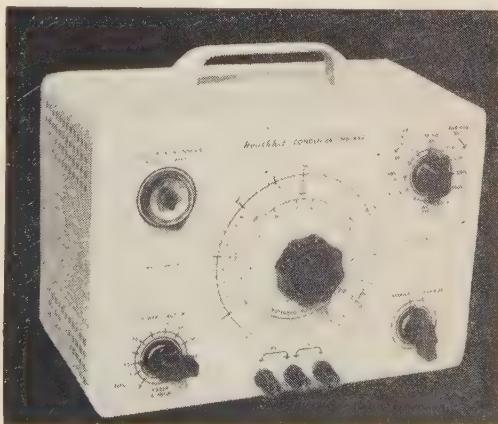

A useful item around the Ham shack is a condenser checker. The Heathkit model can also be used as an ohmmeter in a pinch.





Three days a week, Bob has a regular job as an "information" expert in the store of the Hudson Radio & Television Corporation in New York and Newark, N.J. His advice is eagerly sought by hundreds of regular visitors, whom he recognizes readily by their voices.

## Achievement in Darkness

ROBERT HERTZBERG, W2DJJ

W  
2  
J  
I  
O

Up on the east side of the Bronx, one of the boroughs of the City of New York, lives a Ham who makes his own transmitters and receivers, strings antennas over the roof, fixes ailing radio sets for neighbors, and collects test instruments, components, tubes, etc.


"So what?" you say. "There are thousands of such Hams all over the country. What's so unusual about this guy?"

Nothing much . . . except the fact that he has been totally blind since birth.

After the impact of this bit of information has expended itself, most people react by expressing deep sympathy for Robert W. Gunderson, better known over the air as "Bob," W2JIO. He doesn't ask for it or need it, for he is a thoroughly adjusted, self-reliant, gainfully employed and completely cheerful individual. He is happily married, has his own comfortable apartment, and leads a far more normal life than do some other people I know.

A couple of years ago Bob was invited to describe and demonstrate some of his tricky test equipment at one of the semi-annual dinner meetings of the Quarter Century Wireless Association in New York. He has done a very clever job of converting visual-meter conditions into audio signals, which he is able to monitor and interpret with uncanny accuracy. While he was handling a pile of equipment with unerring deftness, I happened to glance across the table at a well-known Ham who is president of a large manufacturing firm. He was furtively wiping his eyes with his napkin. Realizing that I saw what he was doing, he leaned over and whispered, "Damn it, that man is giving me an inferiority complex, and rightly so!"

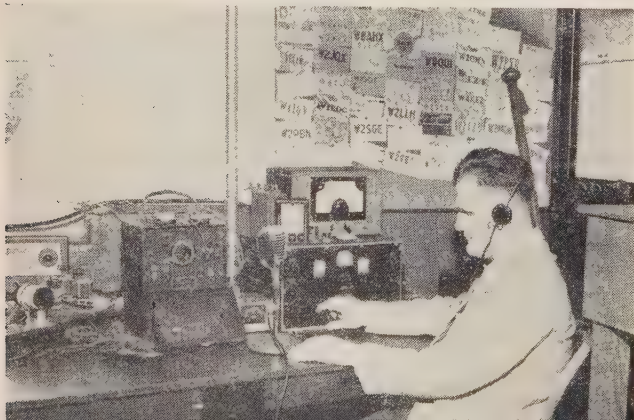Like many other Hams Bob broke into the game by making a crystal receiver at the ripe age of 10. That was exactly twenty-five years ago. After graduating from the New York



Bob Gunderson at the receiving position of W2JIO. He works both phone and CW and skips around the bands.



Institute for the Education of the Blind in 1937, he stayed on as the school's radio instructor, a position he still holds in addition to others. He has taught several hundred blind students enough electronics to qualify them for factory and service work and Ham licenses.

His classrooms at the Institute and his own apartment are cluttered with the usual gear found in Ham shacks everywhere. The only difference is that all the knobs, dials and other controls are fitted with little bumps, over which he presses his educated fingers when he adjusts them.

When I visited the school for the first time and Bob showed me through it floor by floor, room by room, table by table . . . get this, *he* showed me . . . I hesitated a long time before asking him a question that was straining at my tongue, "Uh, how do you manage the soldering part of all this construction?"

He laughed, then led me to a big work bench. He pulled a "breadboard" transmitter toward him, plugged in a gun-type iron and soldered a few joints while I watched, bug-eyed.

Bob lives at 984 Waring Avenue, Bronx 67, N.Y., just around the corner from the Institute. This makes it easy for him to get back and forth, not that distance to a destination is any handicap to him. For instance, in his capacity as technical consultant for the Hudson Radio & Television Corporation, he spends one day per week in each of the firm's three stores at 48 West 48th Street and 212 Fulton Street, in New York, and 35 William Street, Newark, N.J., and he makes the trips by subway unassisted. No seeing-eye dog, no dark glasses no white cane . . . he just goes his way. His friends swear that Nature has endowed him with human radar sensibilities!

Gunderson's job at Hudson is to answer technical questions and dispense general advice. He's been at it now about eight years, and David H. Ormont, president of the firm, is highly pleased with his services. He knows hundreds of regular visitors from their voices.


New customers who are shunted to Bob for technical dope by the floor salesmen often don't realize immediately that he is blind. They'll ask him questions, discuss some circuit feature or trouble-shooting procedure, thank him for his suggestions, walk away, and then stop suddenly, their faces the picture of astonishment. "Why, that fellow must be . . ."

Bob's pet project is the Braille Technical Press, a radio-electronics guide that he publishes monthly. He tries to collect a small subscription fee for it, but he never turns down a request from a blind person who can't afford to pay. This "magazine," complete even to schematic diagrams, has enabled numerous sightless people to enjoy one of the world's greatest hobbies, Ham radio. Practically all the money Bob earns goes into the Press, and he is grateful for any contributions from outsiders to ease his burden. How about it, gang?



*Wiring up a breadboard transmitter is no problem for Gunderson. The gun-type soldering iron greatly simplifies the job, although Bob used a regular iron for years without suffering more than a few initial minor burns.*

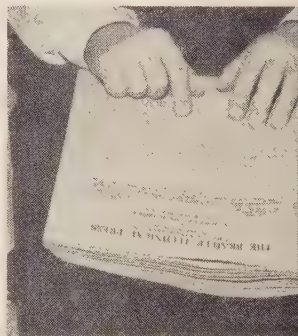*A blind person "reads" a copy of his Braille Technical Press by passing his fingers over the embossed bumps on the pages. Published monthly, this guide has enabled numerous "readers" to become good radio men . . . and women.*



*If you think this is a gag, you're very much mistaken. Bob Gunderson can and does shoot trouble in television receivers, up to the point, of course, of adjusting the picture. This set, in the living room of his apartment, is for the benefit of his wife Lillian.*



## A vintage portable X-ray unit, likely a GE model, featuring a dark metal cabinet with a handle on top, a control panel with various knobs and switches, and a coiled cable at the bottom.


1258 Van Buren St., St. Paul E-4, Minn.

Receiver

The receiver is small—on a 5"x7"x2" chassis—but its performance belies its size. It is a six-tube dual conversion superhet with noise limiter, full a.v.c., adequate speaker output, and band switching for ten and six meters. Fair selectivity was deemed necessary for optimum simultaneous operation of several nets in one band such as planned for RACES and Civil Defense operation. Dual conversion is also a must in a high-frequency receiver to eliminate images and still maintain a degree of selectivity.

The design was made as simple as possible without any special parts so it could be easily constructed. The r-f stage is a 6BA6, the mixer, 6U8, the conversion oscillator and first i-f stage, a 6BE6, the second detector, noise limiter and first stage of audio are combined in a single triple diode 6T8, while the audio output tube is a 6AQ5. The speaker plugs into a jack on the rear of the chassis, but headphones can be plugged into the jack on the front panel. Only three controls are on the panel—tuning knob, volume control and bandswitch.

The i-f channels used were chosen because surplus 135-kc. transformers were available in quantity from the "Marker Beacon" receiver BC-1206. Standard 262 kc. or 175-kc. transformers would be almost as suitable. The frequency of the conversion oscillator was made 1500 kc. so that its harmonics would not fall in any usable part of the ten-meter band. The 18th harmonic falls on 27 Mc., the 19th on 28 Mc., while the 20th falls on 30 Mc. Shielding

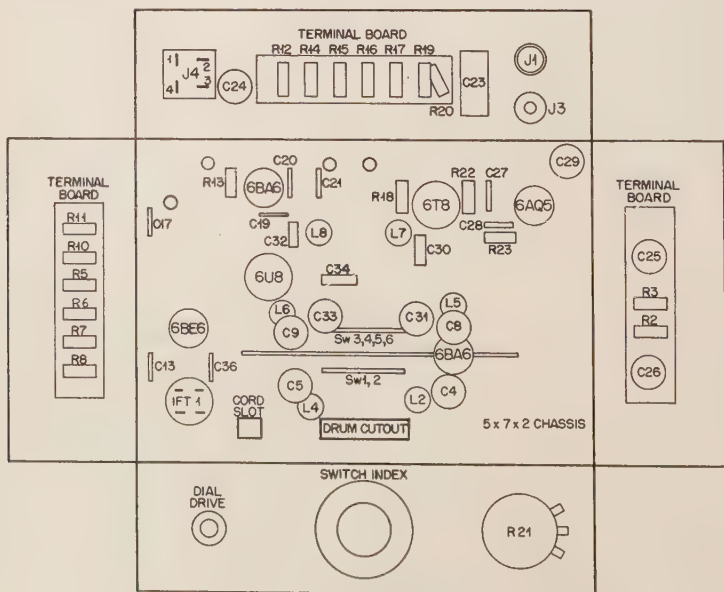


Receiver chassis bottom layout diagram.



of this oscillator coil and the addition of a transformer can be made to tune to this frequency while many surplus i-f transformers are available that can be easily modified for the low value. The harmonics falling in the six-meter band are of such a high order that they are too weak to cause any trouble. The higher i-f channel had to be either 1365 kc. or 1635 kc. The latter frequency was selected to limit the possibility of strong broadcast stations feeding through the i-f system. Standard 1500-kc. i-f

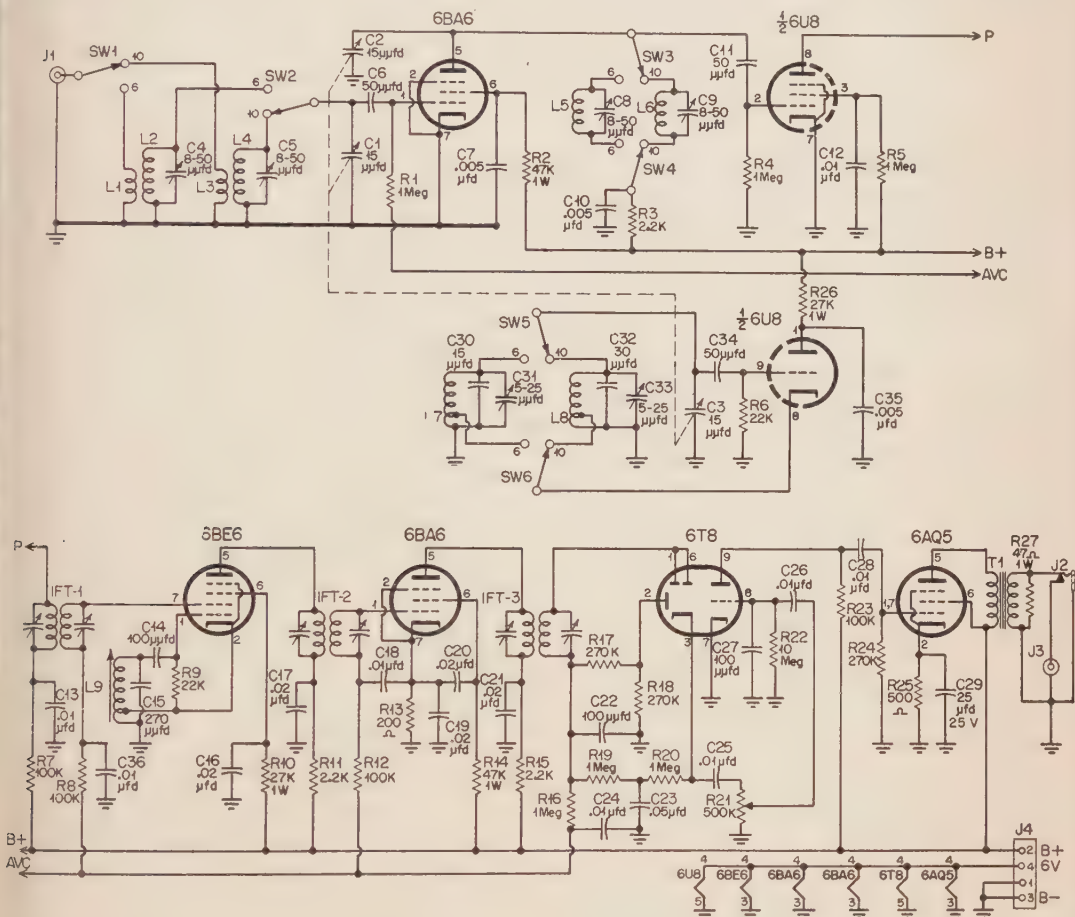The layout and method of construction was planned for ease in assembling. The tuning mechanism is a cord and drum type that gives smooth vernier tuning. The dial proper is a recessed piece of white cardboard behind a Lucite window in the panel, the pointer being



C1, C2, C3—3-15  $\mu$ fd., 3 gang variable (All Star Products).  
C4, C5, C8, C9—8-50  $\mu$ fd., ceramic variable (CRL).  
C6, C11—50  $\mu$ fd., ceramic (Erie GPK).  
C7, C10, C35—0.005 mfd. disc ceramic.  
C12, C13, C18, C24, C25, C26, C28, C36—0.01 mfd. disc ceramic.  
C14—100  $\mu$ fd., silver mica.  
C15—270  $\mu$ fd., silver mica.  
C16, C17, C19, C20, C21

—0.02 mfd., disc ceramic (Erie).  
C22, C27—100  $\mu$ fd., ceramic (Erie GP1K).  
C23—0.05 mfd., 200V. paper.  
C29—25 mfd., 25V. electrolytic.  
C30—15  $\mu$ fd., silver mica or CRL "TCZ".  
C31, C33—5-25  $\mu$ fd., ceramic variable phenolic base (CRL "NPO").  
C32—30  $\mu$ fd., silver mica or CRL "TCZ".  
C34—50  $\mu$ fd., silver mica or CRL "TCZ".

R1, R4, R5, R16, R19, R20—1 megohm,  $\frac{1}{2}$ W.  
R2, R14—47,000 ohms, 1W.  
R3, R11, R15—2200 ohms,  $\frac{1}{2}$ W.  
R6, R9—22,000 ohms,  $\frac{1}{2}$ W.  
R7, R8, R12, R23—100,000 ohms,  $\frac{1}{2}$ W.  
R10, R26—27,000 ohms, 1W.  
R13—200 ohms,  $\frac{1}{2}$ W.  
R22—10 megohms,  $\frac{1}{2}$ W.  
R25—500 ohms, 1W.  
R27—47 ohms, 1W.  
R21—500,000 ohm midget volume control

IFT-1—1635 kc. i-f. (Miller 12W-1 or surplus).  
IFT-2—135 kc. i-f. from surplus marker beacon receiver BC-1206.  
T1—output transformer 6AQ5 to voice coil.  
J1—antenna jack (Motorola pin type).  
J2—closed circuit phone jack.  
J3—phono type pin jack.  
J4—4 prong Jones socket S304AB.  
SW1, 2, 3, 4, 5, 6—2 gang, 2 position, 4 pole wafer switch (CRL #2035).

Receiver schematic and parts list. The 3-gang variable condenser may be obtained directly from All-Star Products, Defiance, Ohio by mentioning this article and enclosing two dollars (\$2.00) with your order.



## Coil Winding Data

### Receiver section

#### Six meters:

- L1—3 turns #30 at bottom of L2  
 L2—4 turns #22 on  $\frac{3}{8}$ -inch polystyrene rod spaced  $\frac{3}{4}$ -inch.  
 L5—3 $\frac{1}{2}$  turns #22 on  $\frac{3}{8}$ -inch polystyrene rod spaced  $\frac{3}{4}$ -inch.  
 L7—3 $\frac{1}{2}$  turns #22 on  $\frac{3}{8}$ -inch polystyrene rod spaced  $\frac{3}{4}$ -inch tapped 1 turn from cold end.

#### Ten meters:

- L3—4 turns #30 at bottom of L4.  
 L4—9 turns #22 on  $\frac{3}{8}$ -inch polystyrene rod spaced  $\frac{3}{4}$ -inch.  
 L6—same as L4.  
 L8—9 turns #22 on  $\frac{3}{8}$ -inch polystyrene rod spaced  $\frac{3}{4}$ -inch tapped 3 turns from cold end.

attached directly to the condenser shaft. The dial is thus protected from being damaged or the pointer being bent or torn off when carrying the packset.

Most of the resistors are mounted on terminal strips and preassembled before being put in place as units near their location in the circuit. The bandswitch and the ceramic trimmer condensers are mounted on a small aluminum partition, which also acts as a shield between the grid and plate sections of the 6BA6 r-f stage. This assembly is installed last, after all major parts have been mounted and wired, thus leaving plenty of working space. The by-pass condensers are all ceramic types and are mounted right at the tube sockets. Before the r-f coils are put in place, the i-f system can be checked and tuned. The last step is installing the r-f coils and checking the tracking, and, finally, calibrating the dial.

The front panel from the cabinet was cut into three sections and two of them used as panels for the transmitter and receiver. The top section is drilled with several large holes and the speaker is mounted behind it, fastened permanently to the cabinet. Two shelves of sheet aluminum were bolted into the cabinet dividing it into compartments for the two separate units that make up the packset. The rear panel of the cabinet is also cut off at the top one third. It is hinged back together again to make a door to the top compartment which is used

for the storage of accessories such as extension cables, headphones, mike, and maybe a screw driver or two. The rear of the speaker is covered with copper screen to prevent damage to the cone.

A short cable is used to connect the two units in the cabinet and the antenna plugs into the transmitter section through a hole in the side of the cabinet. The antenna is a fully collapsible type that is mounted on the side of the cabinet and extends to 52 inches when in use. This length is about right for six-meter operation. Although it is too short for ten meter work it will load up and the radiation is adequate for local work over several miles.

## Conclusion

Several of these *Packsets* have been built during the past year and used in a variety of activities with excellent results. The acid test


## Receiver Voltage Measurements

TUBE	PIN NUMBER—VOLTAGE								
	1	2	3	4	5	6	7	8	9
6BQ6 r.f.	-.75	0	0	6	180	50	0		
6U8	100	-2	35	0	6	150	0	0	-.75
6BE6	-1.5	0	0	6	225	75	—*		
6BA6 i.f.	—*	1.5	0	6	210	80	1.5		
6T8	-1	—*	—*	0	6	-1	0	-.5	
6AQ5	0	15	0	6	210	225			

All measurements taken with a Simpson model 260 VOM, 20,000 ohms per volt. Polarity is positive with respect to chassis ground unless otherwise indicated. Voltages marked (\*) are too small to be read with any significance other than to show probable correct operation by polarity of reading. Source voltage was 225 and total current for the receiver is about 60 ma. at this voltage.

was given during several hours of continuous operation in 90 degree temperature supply communications for a golf tournament with equipment failure. A *Packset* makes an ideal hidden transmitter for hunts and can be taken to almost any unlikely location even if you have to take a battery along. The total battery drain is less than ten amperes and a storage battery lasts a good many hours. Another use is talking back to a fixed station when running down some TVI. Although no special precautions were taken to make these units TVI-proof, they have been operated right next to TV sets with no outstanding interference. With an outside antenna they make ideal stations for local talking over considerable distance, and whether either six or ten meters are open you are all to go.

The transmitter and power supply for the receiver and transmitter were featured in the May 1954 issue of CQ. This issue may be obtained from our Circulation Manager, Bureau Issues Dept. for 40c. For those who did not see this issue, the transmitter consists of a 6 and 6 meter unit (no bandswitching) with 12AU7 and 6AQ5 output. It is modulated by a single 6AQ5 driven by another 12AU7. Power supply is a vibrator with selenium rectifiers

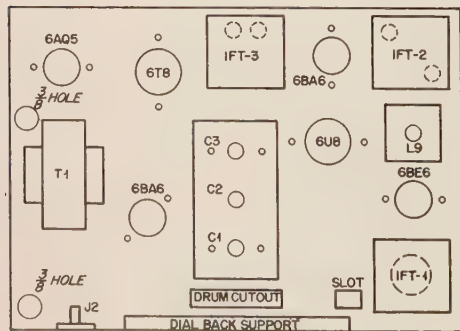

Layout plan for the top of the receiver chassis.



Gathered by DICK SPENCELEY, KV4AA

Box 403, St. Thomas, Virgin Islands, USA.

We welcome the following newcomers to the HONOR ROLL:

VK3XO 39-166

ZL4BO 39-147

DL1YA 38-153

KV4BB 35-187

### New DX Committee

*CQ* is happy to announce the formation of a new "DX Committee." This will replace the old committee which resigned last year.

In forming this committee, *CQ* wanted a group of DX men who would be representing many active areas of the U.S.A. and one which would be democratically selected. To this end we approached eight amateur radio associations and requested that they select one of their members to serve on our "DX Committee." Their cooperation was immediate and we are very pleased to present the new "DX Committee" who, with your writer, will shape *CQ's* DX policies in the future:

WIMCW, Mrs. Lou Littlefield,

*New England DXCC'ers.*

W3BES, Jerry Mathis, *Frankford Radio Club.*

W3JTC, Larry Eisler, *Potomac Valley Radio Club.*

W5FXN, Jim Price, *West Gulf Radio Club.*

W6FSJ, Wendell Pierce,

*Southern California DX Club.*

W6TT, Elvin Feige, *North California DX Club.*

W8FGX, Jake Schott, *Ohio Valley Radio Ass'n.*

W9NN, Bob Baird, *W9 DXCC Club.*

Members will serve for a period of one year, after which the incumbent may be re-elected, or a new member chosen by his respective club.

Our aim is to promote any action in the DX field which has popular demand and which would be to the betterment of Ham radio in general. To this end we solicit your ideas and suggestions and promise each will receive careful consideration by the "Committee."

### At Time of Writing

SARAWAK, VS5RO, BRITISH NORTH BORNEO, ZC5RO: We have word that Bob Roberts, G2RO/VQ5RO/VP2GRO, etc., was due to leave for Sarawak on June 1. He will be active from this spot for two weeks, especially on weekends. After Sarawak, Bob will proceed to British North Borneo and on to the locations in the above box.

### Itinerary of G2RO in Esia and Probable Calls

June 4 to June 18: SARAWAK—VS5RO

June 18 to June 28: BR. NORTH BORNEO—ZC5RO

June 29 to July 8: HONGKONG—VS6RO

July 18 to July 24: KUALA LUMPUR, MALAYA—VS2RO

July 24 to July 31: PENANG, MALAYA—VS2RO

Aug. 1 to Aug. 7: CEYLON—4S7RO

Aug. 7 to Aug. 12: NEW DELHI, INDIA—VU2RO HOME.

SAN ANDRES, HKØ: As reported in the June *CQ*, some 75 Colombian Hams visited this QTH between May 4 and May 8. Three separate stations were set up and each operator took over for a two-hour period. Various calls were heard as each HK Ham signed his home station call letters preceded by the HKØ prefix. It is estimated that 90% of the operation was on phone and about 3000 contacts were made. Stations contacting five, or more, HKØ stations will be awarded a certificate. One Ham is "permanent" on San Andres. He is Victor Abraham, HKØAI (See March *CQ*).

CRETE, SVØWK: SVØWA advises us that SVØWK planned to put Crete on the air some time in June.

COCOS ISLAND, TI9RCCR: The Radio Club of Costa Rica hopes to make an expedition to this spot in July or August. The call will be TI9RCCR.

ST. PIERRE, MIQUELON, FP8AA: We hear that Jack, W3BXE, now K2CPR, plans a return trip as FP8AA this summer.

GOA, PORTUGUESE INDIA, CR8AB: This station came on the air on May 15. He is the son of CTICB and operates on 14020 kc.

LIECHTENSTEIN, HB9MX/HE: Operation for this station is planned for the second part of July or August. 400 watts CW and phone will be used on the 7, 14 and 21-Mc. bands. Operators are HB9MX and HB9JK.

COMORO ISLANDS, FB8: Scuttlebutt has it that Jim, ST2UU, plans to appear from this QTH in August.



**SPITZBERGEN, LB5ZC:** A report from LA4ZC says that there is a possibility of activity from this rare spot in the near future. The call will be LB5ZC.

**TRINIDADE ISLAND, PYØ:** Word from PY4IE advises us that good news regarding this long awaited expedition should be available soon.

**MAWSON BASE, AUSTRALIAN ANIARTICA, VK1EG:** Bill Storer, ex-VK1BS, is now active from this QTH. Not much DX'ing has been done as yet, but schedules are maintained with VK1DY on Heard Island, 1600 GMT, 7040 kc. Bill is Postmaster there.

**JORDAN, ZC7DO:** This prefix fell on many startled ears in May. However, Paddy gives his QTH as Jordan and, no doubt, this one will count the same as the ZC1 and JY prefixes. See QTH's.

**NORFOLK ISLAND, VK9OK, VK9RH:** These stations have been quite active. VK9OK's stay was apparently cut short and he advised us that he is returning to New Zealand (May 1954), and QSL's should go via ZL1AJU.

**FORMOSA, ABIUS:** This station, ex-C3EA, has been handing out contacts on phone, VFO 14175, 0700 GMT, etc. Operator is Sgt. I/C Al Hatlestead and all QSL's go to the USA via airmail. See QTH's.

### DX Notes

The Clipperton gang is now back home for a well earned rest. On the way back they were entertained by the San Antonio, Dallas and Tulsa Hams. A total of 1108 stations were worked from Clipperton, mostly W's. Only one European was worked (OK1MB), two Africans and no Asians. Due to generator breakdown, 21-Mc. operation netted only 28 contacts. They reported that XE4PK was on the Mexican Islands of Revilla Gigado when they left. It seems that XE4PK works 7-Mc. phone. (Thanks to West Gulf Bulletin) . . . W6YY

### QSL Averages of DL1YA

Area	Stations Worked	QSL's Received	Percent
W1	107	58	54
W2	142	70	49.5
W3	84	48	57
W4	75	35	46.5
W5	31	17	54.5
W6	21	14	66.5
W7	22	17	77
W8	59	27	45.5
W9	27	17	63
WØ	24	15	62.5
All USA	592	318	53.5
Other North America	93	62	66.5
South America	70	36	51
Africa	157	79	50
Asia	94	59	62.5
Oceania	71	33	46
Europe	2322	1352	58
Totals	3399	1939	57%

advises that VR2CG can arrange skeds with FW8AP approached right. Also, solar observers at the Mt. Wilson Carnegie Observatory seem to think that we are now past the bottom of the sunspot cycle . . . X1NP, a self-confessed pirate, he operated from a ship reefed off the Australian Barrier Reef . . . VR6AC is definitely a phoney as the real VR6AC, on Pitcairn, tells ZK1 that he has only been on 75-meter phone for the past months and has only worked ZL's and VK's . . . Another, ZK4AC, claims to be on Tonga Reva. This is an island in the northern Cook Island group (Penny Islands), and falls under the ZK1 prefix. ZK1AB reports this one as NG . . . Lastly, TI2TG, reports TI5EP as a pirate 1/c. Possibly one or more of them.

### Endorsements to Honor Roll

W8NBK	40-246	W6BUO	40-148	W6CAE	39-
W6SN	40-245	W8KIA	39-239	TI2TG	38-
W6AM	40-244	KV4AA	39-236	W1HA	38-
W8PQQ	40-243	W2WZ	39-234	WØTKX	38-
W2AGW	40-243	W3EPV	39-230	DL1YA	38-
W6SYG	40-242	W1BIH	39-223	W4EPA	37-
W3EVW	40-242	W2QHH	39-223	W2ZVS	36-
W8BHW	40-242	W9FKC	39-216	W3AXT	36-
W6MX	40-241	W9HUZ	39-206	KV4BB	35-
W6ADP	40-241	W1ZL	39-205	W5FXN	35-
VE4RO	40-238	W3KDP	39-200	W6ZZ	35-
W6DZZ	40-235	W4RBQ	39-195		
W6GDJ	40-231	W6GPB	39-193		PHONE ONLY
W7BD	40-228	W9ABA	39-179	W6AM	38-
W6TI	40-221	W8VLK	39-177	W1MCW	36-
W6DLY	40-219	VK3XO	39-166	W1NWO	36-
W6EPZ	40-214	ZL4BO	39-147	TI2TG	36-
W6BUD	40-208	TF35F	39-145	W3EVW	35-

Last complete HONOR ROLL appeared in the

May issue.

Next complete HONOR ROLL will appear in the September issue.

calls may emanate from the same misguided gentleman—so much for our rogues gallery.

Several reports on Albanian contacts have been made but not confirmed, as yet, as "legal." YU1AD says that is NO legal Ham activity from ZA and he is not enough to know. OK1MB said there would be activity from ZA1KAA, ZA1KAB and ZA1KAC during the Albanian contest of May 8 (none were heard here). KV4AA). ZA2MU was heard in QSO with DM2A. The latter reports that two stations are licensed to ZA1AC and ZA1KAA. Thus, with conflicting reports just "hope for the best" . . . The RSGB Bulletin that the Sultanate of Oman, as VS9, will be dropped from the lists. This is somewhat obscure, but it means that an independent prefix will apply . . . ZC6U Palestine, has been active on 14015 with ex-HS1UT the key . . . MP4QAH, Tony (Qatar), is due to QRT July 1 and return to England . . . EAØAC was due to leave for home on May 16 . . . PJ2AA reports JZ will be QRT and return to Holland in June. W2AA who handles JZØKF's cards, just received 50 from him. He also has the logs of VK9YY covering the period Dec. 1952 to May 2, 1954 if any QSL's are missing. KF3AB has been active on 14030 (Fletcher's Ice Is near North Pole).

Roy, W3CHV/ex-SVØWG, should now be in Manila. Any missing DU QSL's please advise W3AXT, who will forward to W3CHV who will do his best to obtain them . . . LB6IE is active from Jan Mayen and has been heard on 7 Mc. . . W9ABA says LB5YB, also Jan Mayen may be heard Sundays, 2100 GMT, 14040 . . . VS was QRT on June 1 and heads back to G3JOE. ZD1SS has been heard on 14132 and 14078, CW, 7-Mc. GMT . . . AP2N should be in VU-land now . . . SV is the second, native, Greek station licensed. He is on phone and speaks good English . . . The following trian Hams have been licensed and may be contacted: W stations: OE1ER (ex-OE1CD), OE1WB, OE1NP, OE3RE . . . W and VE QSL's for EL2P and EL2X go via WIØJ . . . VR3A continues activity, 14052, GMT onwards . . . FK8AL, Johnny, wishes it known he is on each day from 0400 to 0600 GMT, 14060 14100 VFO. See QTH's . . . ZK1AB was overheard working Andy, VR6AW on 7 Mc.


### DX-ploits

FO8AJ was No. 246 for Arkie, W8NBK, moving ahead of W3GHD . . . W6SN added 8AJ for No. jumping him over G6RH . . . Don, W6AM, went to

(Continued on page 53)



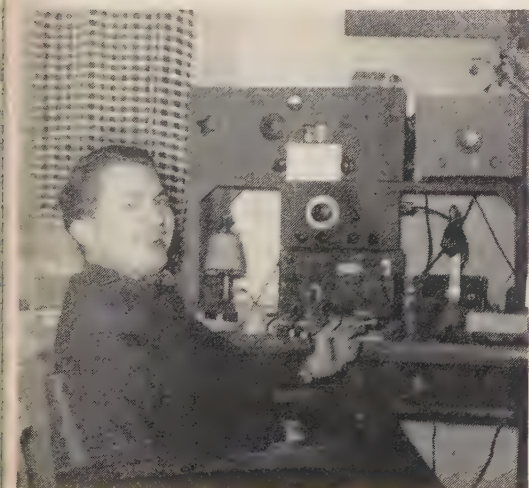W4TK, Bob Reid, Jacksonville, Fla., has been active from this QTH for 29 years. Bob runs a KW on Phone and CW on the 7, 14 and 28 Mc. bands. He is an engineer at WMBR-TV.



Very happy indeed is Mirko, YU1AD, with the operation of his rig and folded unipole ground plane antenna at his new QTH. Photo was taken by Bob, YU1GM/W4GMP. We wish him and YL Lela our best on their coming hook-up. Mirko is up to 208 countries.


Needing no introduction is Julio Badin, CX1FY, of Colonia, Uruguay.



The neat layout of W3PGB, Lee Scott, "Scotty" of Silver Spring, Maryland. Collins equipment is used and emergency gear is on top. Scotty has that perfect "El-bug" fist and operated as NU5ANY in 1922 and W5BOW in 1930.



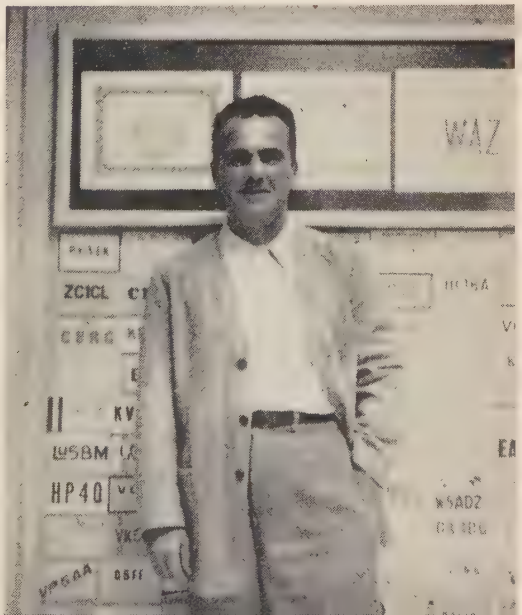L to R are JA1NQ, JA1EG, JA1GS and JA1HG, who were snapped during a meeting of their local radio association, the Akabane Club. Photo courtesy W6GPB.







Monitored by LOUISA B. SANDO, WØSCF

c/o General Delivery, Cortez, Colorado

Once again the reins of YLRL change hands. Our congratulations to all of the officers of the *Young Ladies' Radio League* who will be serving during the 1954-55 term, and who take office on July 1. Our new president is W6CEE, Vada M. Letcher. Vada received her Ham ticket in February, 1948, and a month later joined the YLRL. This was the year all three top officers were W6s, and little did Vada dream that she would be the next W6-district president. Her Class A came along in Sept. '51. Her OM, Al, is W6HWM. Their station is a *Viking I* and VFO, *HRO-50T1*, and a 136-ft. longwire all-band antenna. They also use a *Gonset Communicator* and *Master* ground plane antenna on two meters. Four YL nets take most of W6CEE's operating time each week. Vada is a past president of the *Los Angeles YL Radio Club*, present secretary-treasurer (second term) of the *Los Angeles Council of Amateur Radio Clubs*, and past treasurer of the *Inglewood Amateur Radio Club*. Although a Nebraskan, she has lived in California since '41. Her present QTH: 1214 A Franklin St., Santa Monica.

Our new vice president is W6KER, Gilda Shoblo. This makes both top officers in W6 and since they live quite near each other and both are members of the *Los Angeles YLRC*, it should make it much easier for them to handle YLRL business. The girls are happy at the prospect of working together to see "what the West can accomplish"—hi!

Gilda has been on the air since November '50, starting out with a *TCS-6* on 10-meter phone. This blew up a year later, just after she got her "Class A."



W6KER, Gilda Shoblo, YLRL's new Vice President.

Then she went on 40 CW for a while. Now she has her OM, W6MES, are using a home-built transmitter running up to 800 watts, VFO, using 813's and 8X. Their receiver is an *HQ129-X* and they have a dipole antenna on 75. Gilda hopes to be on 20 by July. They also operate mobile using an *Elmac* on 75 and 10. Gilda has just retired as president of her local YL club, but she says she will continue to operate up the club's *Lad 'n Lassie* certificates. Her special love is sewing and she also keeps a garden growing at the home QTH: 3715 Liberty Blvd., South San Diego, Calif.

The other three officers of YLRL have been elected for a second term. They are: secretary-treasurer, W3UUG, Miriam Blackburn; publicity chairman, W3QQF, Barbara Houston, and editor, W9JRM, Bernice Schmidt.

A photo and write-up on W3UUG appeared in the September 1953 column. Miriam tells us there are about 500 paid-up members in YLRL. If you are a member and would like to join, write for information and an application blank to your column editor, directly to Miriam, W3UUG, Box 2, Ingomar, Pa.

W3QQF has been in these pages a number of times. Her special interest at present is her new little daughter. As P/C she is anxious to have photos of YLs for the YLRL album—which, we may remind you, is available for conventions and YL get-togethers if you'll request in advance from Barbie at 109 Seneca Dr., Washington 20, D.C.

W9JSJR was featured in this column in October 1953 but we are happy to present her here with most of the "editorial staff." Bernice and the members of the YLRL have worked hard this past year on *Harmonics* and help from all the girls the paper has improved with each issue. With reduced finances its scope must be curtailed but as soon as the money is available Bernice and the other girls expect that *Harmonics* will again assume its place as a growing source of YLRL information. YL newswomen should be sent to your District Chairwoman. Other material can go direct to Bernice at 3849 N. Kenmore Ave., Chicago 41, Ill.

### YLRL District Chairwomen

District Chairwomen for the 1954-55 term are:  
**W1VOS**, Marjorie Snow, 218 East St., Plainville, Conn.  
**W2JZX**, Viola Grossman, 18 Phipps Ave., East Rockaway, N.Y.  
**W3**—To be appointed.  
**W4RLG**, Frances Shannon, Cottondale, Ala.  
**W5TTU**, Patricia M. Parks, Rt. 1, Rotan, Tex.  
**W6**—To be appointed.  
**W7SBS**, Lurynne Conner, Lake Shore Dr., Klamath Falls, Ore.  
**W8SPU**, Helen Smith, Sycamore, Ohio.  
**W9LOY**, Alice Bowlin, 6563 N. Tahoma, Chicago 31, Ill.  
**WØERR**, Anna Belmonte, 2720 South Dahlia, Denver, Colo.  
 Canada: **VE3AJR**, Olive Daykin, 124 Erie Street, Leamington, Ontario.  
 Canal Zone: **KZ5DG**, Grace Dunlap, Box 10, Balboa Heights, C.Z.  
 Hawaiian Islands: To be announced.

There were no nominees for the 3rd district. Incoming president W6CEE will appoint a W3 D/C. W6KER was on the ballot for D/C but since she won the election as VP, Vada will appoint another W6 YL to be D/C. The address above for W4RLG is her home QTH. For the next few months write to Frances at the U.S. Army Hospital, Ward 28, Ft. McClellan, Alabama. Frances is "taking it easy" while the doctors do battle with tuberculosis, but she writes she is making progress, and we hope she will soon be well again. Remember, these D/C's will be happy to receive news from you for YLRL Harmonics.

### YL-OM Contest Cups

When the rules for this year's YL-OM Contest were issued, only first place winners in each category were eligible for cups. This was because the cups issued last year for second and third places were incorrectly inscribed. At the time the rules for this year's contest were being formulated, W2OWL did not know whether these cups could be redone so they could be issued again this year, as YLRL could not incur the additional expense of purchasing new cups. It now appears that the second place cups can be redone and these are being issued to the following: 2nd place YL phone, W1SCS; 2nd place YL CW, W9JUI; 2nd place OM phone, W8AJW; 2nd place OM CW, W9VEZ.

### With the Clubs

At its April meeting three new girls joined the Los Angeles YLRC—K6BXX, Ruth; K6ALZ, June; KN6BBM, Verdona. The club now numbers forty-two members. Another member has received her call, KN6EIA, Ellen. First timers for that meeting were KN6DRS, Jean; KN6EJE, Frances, and KN6DPY, Pat. VK2US entertained the girls with colored slides taken in Australia.

The Chicago LARKs are all set for conventions or other Ham doings. They have club pins, triangular in shape with LARK in script across the wide end. They also have kerchiefs with a bird and LARK on them, as well as their blouses just alike to wear to Ham affairs. Two club members recently received their General Class tickets; W9YXX, Rita, and W9SPI, Marge.

The LARK's vice president, W9MYC, Gladys Jones (fourth from left, top row, in group photo) is a gal from whom we could all take a tip. Gladys writes, "Most of my rigs I have built myself; in fact, I would rather build than operate." And her OM isn't even interested in Ham radio! There are two other Hams in the family, however, a son, Bob, W9DWD, and a brother-in-law, W9DOU. Besides Bob, their family consists of another son, a twin to Bob, and a daughter who is a freshman in college. Gladys has been on the air for a little over three years. She operates mostly 80 and 40, both CW and phone, and can get on 160, 10 and 2. All of her rigs are under 60 watts in power, and she really enjoys putting them together. W9MYC also operates as W9ZUZ at her summer home in Wisconsin.

### Congratulations

To W1QON, Eleanor, on the arrival of her second jr. op, a daughter, on April 23rd. . . . And to W7RSA, Chris, who also took time out to have a baby, but is back with the NYLON net. . . . To W7RHM, Lana (another NYLON member), who is CD coordinator for the Gray's Harbor (Wash.) area. Lena has been so enthusiastic about her Hamming that she now has her mom, Ceil, on the air as W7RVG. Lana, crippled by polio, is going to Portland for eight or nine months to attend a rehabilitation school.

Editor of YLRL HARMONICS. W9SJR, Bernice Schmidt (second from left, front row), and her staff of helpers, all members of the Ladies Amateur Radio Klub (LARK) of Chicago. L. to r., front row: W9YBC, Gloria; W9SJR, Bernice (also LARK president); BCB, Helene; SYX, Peg, and YXK, Rita. Second row: W9IKS, Edna (club secretary-treasurer); LOY, Cris; YWH, Evelyn (membership secretary); MYC, Gladys (LARK vice president), and AYX, Jackie. Other LARK members include: W9BCA, Helen; DXX, Alice; KQC, Virginia; SPI, Marge; SSL, Shirlene; TIX, Kathleen; WOI, Vera; and WN9's BJH, Stella; TME, Rosemary, and YKV, Sue.



W6CEE, Vada M. Letcher, newly elected President of YLRL.

To Jeanne, KL7RN, and her OM Dick, KL7IS, on their rescue from a crash landing on Mt. McKinley. Jeanne and Dick were flying supplies to a mountain climbing party when a down draft caught their plane and forced them to crash land, 7000 feet up on the mountain. After five days they were rescued by an Army helicopter. Winds up to 120 miles an hour detained their rescue, and though their plane was not badly damaged in the landing, it was reduced to a pile of rubble by the wind. W7HHH, Bea, who talked with Jeanne on 20 meters soon after her rescue, says Jeanne was terribly burned by the wind and sun and that her hair was so badly tangled she had to have most of it cut off. Otherwise she is okay and went back to work right away. Jeanne credits the other Hams who were right in there pitching to help with their rescue.

Till next month, 33, WØSCF.

### Were You in the Far East?

The Far East Amateur Radio League has served notice that unclaimed QSL cards for J, JA and KA call-signs issued to former occupation personnel will be destroyed around the first of the year (1955). The FEARL QSL Bureau has several thousand QSL cards on hand and desires to clean house. If you held a J, JA or KA call and want your occupation QSL cards, please write to the: FEARL QSL Bureau, P.O. Box 111, APO 500, c/o Postmaster, San Francisco, Calif. A large self-addressed, stamped envelope should be included with your request.





# Ionospheric Propagation Conditions

Forecasts by

GEORGE JACOBS, W2PAJ

144-40 72nd Ave.

Flushing, Long Island, N.Y.

## General Propagation Conditions

- 6 METERS:** Some good Sporadic E openings should occur during the month.
- 10 METERS:** Very little DX, but very frequent Sporadic E short skip openings up to 1400 miles.
- 20 METERS:** Fair to good world-wide DX from shortly after sunrise to a few hours after sunset. Daily short skip openings up to 1400 miles.
- 40 METERS:** Good DX to most areas from shortly before sunset to shortly after sunrise, but considerably higher static level.
- 80 METERS:** Static level generally high on most days. DX possible during hours of darkness on day static level is low.
- 160 METERS:** Higher atmospheric noise levels and summer absorption will not permit DX on this band until early Fall. Short skip QSO's possible during dark hours.

This overall picture of band conditions is intended to indicate qualitative changes in each band from month to month. For specific times of band openings for a particular circuit, refer as usual to the *Propagation Charts* on the opposite page.

## Sunspot Cycle

The July Propagation Tables are for a predicted smoothed sunspot number of 6. The observed monthly Zurich sunspot number for April, 1954, was 1.8, resulting in a smoothed sunspot number of 10.7, centered on October, 1953. The smoothed sunspot numbers continue to decrease as we approach the minimum of the present cycle.

## Propagation Technical Conference

Scientists and engineers are continuously investigating the solar system and the earth's atmosphere in hope of solving some of the secrets concerning radio transmission. In early May, the spring joint meeting of the International Scientific Radio Union (URSI), and the Professional Group of Antennas and Propagation of the Institute of Radio Engineers was held at the National Bureau of Standards, Washington, D.C.

A number of talks were given concerning the propagation of v-h-f signals far beyond the horizon. Newman, Ames and Rogers of the Air Force Cambridge Research Center delivered a paper entitled "VHF Field Strength Measurements Far Beyond The Radio Horizon." They discussed measurements that have been made at 220 Mc., on a 200-mile overwater path extending along the New England Coast. The median signal level in August, 1953, was about 50 db. below free space; in January 1954, the median decreased to 75 db. below free space. While these are relatively weak signal levels, it is significant that the signal was always present and did not fade out. Photographic records of back-scattered signals indicate that the higher summer signals were largely a result of super refraction.

In other experiments, fields at 220 Mc. have been explored at distances far beyond the radio horizon with an airborne receiver. The transmitter was located in the vicinity of Boston and about 80 feet above sea level. Measurements were made on flights over the Atlantic

Ocean. Signals have been consistently recorded out to distances of 350-400 miles.

Observations made on "the big signal" on 49.6 and 49.8 Mc. were discussed in a paper by Dyce of Cornell University. It was disclosed that the 49.6 and 49.8 Mc. signals transmitted continuously from Cedar Rapids, Iowa, have been monitored for almost 2 years at Ithaca, New York, using a 6-element Yagi antenna pointing northward. The purpose of this experiment was to observe the signal reflected from the aurora. The signals heard during a visible aurora have an extremely rapid fading rate characteristic. When auroral propagation occurs, it appears to reach a double-humped maximum centered on midnight. The azimuth angle of arrival during aurora was generally found to be from the northwest. Dyce mentioned that radio amateur auroral observations have played an important part in his studies of auroral propagation, and that the reports received from Amateurs were in good agreement with the data obtained at Cornell. It was also reported that on April 11, 1954, the first 220 Mc., amateur QSO via auroral propagation took place.

Peterson and Leadabrand of Stanford University delivered a paper entitled "Long Range Radio Echos from Auroral Ionization," and discussed radio echos believed to originate from auroral ionization that are consistently observed at Stanford University, California. The observations were unusual in that the signals were being received over greater distances than previously reported. Stanford is between 1000-2900 miles south of the auroral zones. The reception was observed on frequencies in the 6, 12 and 17-Mc. bands, which are lower than those on which auroral reception has previously been observed.

## Prediction Flash

**Ionospheric storminess is usually at a minimum during July. No ionospheric disturbances are forecast, but night-time conditions may be unstable throughout July 11-13. Good propagation conditions are expected during most of the remaining month.**

The strength of the echos were found to be surprisingly strong and can be distinguished by their amplitude fluctuation (flutter), and Doppler shift (change of tone when received with the b.f.o. on). Bearings taken on the echos indicate reflection from ionization at points along the auroral zone all the way from Eastern Canada to Alaska.

K. L. Bowles, of the Geophysical Institute, discussed auroral and meteor echos observed at College, Alaska on a frequency of 106 Mc. College is close to the center of the auroral zone and visible aurora is commonly seen overhead. Bowles found that the echos seemed to come from the direction of the geomagnetic North Pole, and from a distance of 600-650 miles north of College. This appears to be in good agreement with the observations made at Stanford since Stanford is about 1800 miles south of College, Alaska.

R. Dyce also spoke about auroral echos observed at College, Alaska on 50 Mc. His results were very similar to those obtained at 106 Mc. The auroral echos were obtained only from azimuth angles within 60 degrees of magnetic North and at ranges chiefly between 250 and 450 miles north of College.

## Sporadic-E

Probably as puzzling as aurora to propagation researchers is the mystery of sporadic E. Peterson of Stanford University discussed the results of scatter soundings taken throughout the past year and a half. Peterson stated that it appears that the average occurrence rates of sporadic E throughout the world can be surprisingly predictable. The monthly average daily rate is very strongly dependent upon geomagnetic latitude. In the auroral region most of the sporadic E is observed during the hours around midnight while in equatorial regions sporadic E is primarily a daytime phenomenon.

Seasonal variations in occurrence rates are likewise found to be a function of geomagnetic latitude. At middle latitudes, a pronounced summer maximum of occurrence is observed while near the Poles and the Equator relatively little seasonal variation is found. A minimum of sporadic E occurrence is found during the equinox periods (March/April and September/October), at middle latitudes, but about twice as much is observed in the Fall as in the Spring. The scatter soundings indicate that during much of the time, both polar and equatorial types of sporadic E are observed in the United States. Peterson suggests that the marked seasonal variations at middle latitudes may result from a northward shift of

(Continued on page 58)



# NOVICE SHACK

Conducted by HERB BRIER, W9EGQ

385 Johnson St., Gary 3, Ind.

A standard method of eliminating television interference (TVI) caused by harmonic energy is to install a low-pass filter between the transmitter and the antenna. In theory, installing a low-pass filter is easy, but in practice, doing so sometimes introduces complications difficult for the new amateur to solve, especially if he does not have grid-dip oscillators, standing-wave bridges and similar gadgets. This month I shall discuss low-pass filters and simplified methods of using them.

## Low-Pass Filters

A low-pass filter is designed to reject frequencies in the television channels. It consists of a number of tuned circuits resonant at those frequencies to be attenuated, which are connected in cascade and

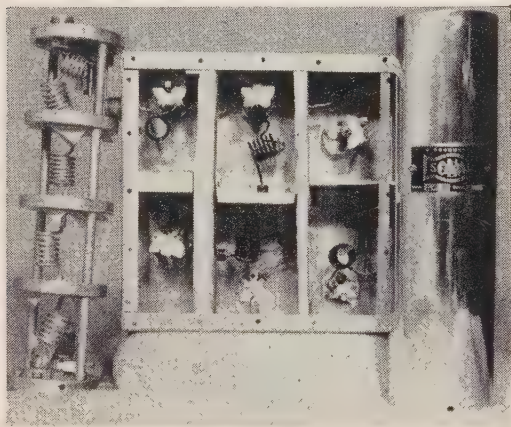


Fig. 1. Internal views of two low-pass filters for the prevention of harmonic radiation directly through the antenna. The square box is a home-made version of the tubular filter (Sonar LP-7). The jacket for the Sonar filter is on the right. When the shield is replaced on the box, or the jacket on the LP-7 filter, they become r-f tight.

mounted in an r-f tight box. All frequencies below cut-off frequency of the filter are passed with practically no attenuation, while higher frequencies find the going tough, if not impossible.

Modern, commercially manufactured low-pass filters will safely handle the full output of a 1000-watt transmitter when properly installed. They pass frequencies up to 30 Mc. with less than  $\frac{1}{4}$ -db. attenuation, while frequencies above approximately 50 Mc.

are attenuated at least 70 db.\* They are used designed for use with 50-ohm or 75-ohm coaxial cable feedlines. If you are using an antenna with a different kind of feed system, don't let this worry you; they can be adapted for use with any antenna or feed system.

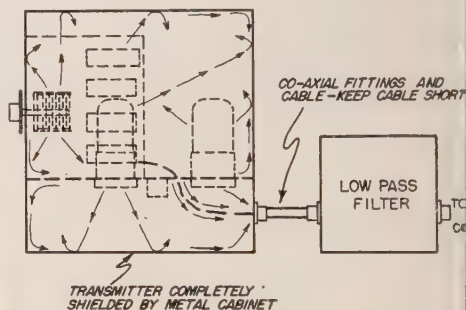


Fig. 3. This is the effect that the Novice should strive for. Note that the r-f energy (indicated by the arrows) is confined inside the shielding. Compare this with Fig. 4.

Figure 1 is interior of a modern, commercial low-pass filter, the Sonar LP-7, and of a home-built

Probably the first thought that comes to mind is why should a Novice, limited to 75 watts input, need a 1000-watt filter. The answer is easy. Actual costs very little more to build an effective 1000-watt filter than it does to build a 50-watt one. And a filter with adequate power-handling capabilities does not have to be "babied." Of course, this is a feature worth having. In fact, the suggestions to follow are based on it. With a low-pass filter of adequate power rating, it is not absolutely necessary to have it matched perfectly to prevent it from blowing

## Installing A Low-Pass Filter

Figure 2 is a photograph of the proper way to connect a low-pass filter to a transmitter, no matter how it is connected to the other end of the filter. In fact, it makes no difference which end of the filter is connected to the transmitter.

The sketch, Fig. 3, will quickly show why this is a good installation. The entire transmitter is shielded right up to the output of the filter, and the output must go through the filter; thus it can do the job it was designed for with maximum effect.

\* Equivalent to a power ratio of 10,000,000 to 1.

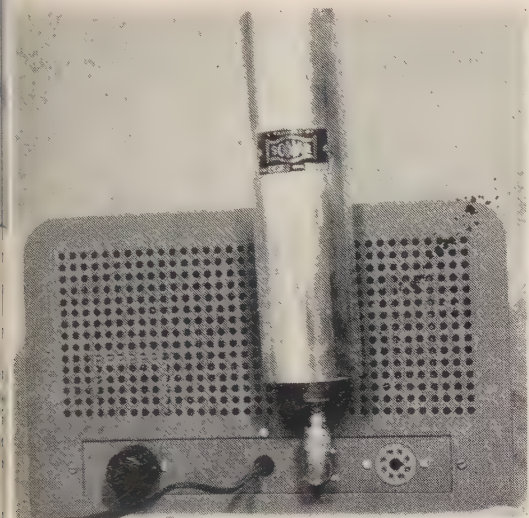


Fig. 2. A filter properly installed on a shielded transmitter. See text and Fig. 2 for details. The connector between the transmitter and the filter is constructed of two 83-1SP fittings and a length of RG8/U cable, with its outer vinyl coating removed, just long enough so that the backs of the fittings touch. A bead of solder around the joint makes a rigid unit. The right-angle connector is an 83-1AP. Fastening the filter firmly to the transmitter with a metal strap is also recommended.

In contrast, in an arrangement like Fig. 4, TVI can be radiated directly from the unshielded transmitter output terminal and from unshielded components in the transmitter. Even worse, interference can flow around the filter to reach the antenna.

The important thing here is to realize how little power has to get by the filter to nullify much of its effectiveness. If only 1% of the interference gets around the filter, it will reduce the effectiveness of the filter to a maximum of 20 db.

*Moral:* keep that r.f. bottled up, if you expect much from a low-pass filter. However, it is not usually necessary to knock yourself out to shield a low-power transmitter operating on the 3.7-Mc. and 7-Mc. bands. For example, putting a bottom plate on the chassis and shielding the coil in a can at least double the coil diameter, and installing a coaxial fitting for the output terminal would go a long way towards eliminating the objectional features of Fig. 4, especially if the transmitter uses metal tubes. Once you have the big leaks plugged up, you can start on the small ones.

The transmitter pictured in Fig. 2 is the Heath AT-1 35-watt reviewed in the April column. As mentioned in the review, there was enough direct harmonic radiation from it on 14 Mc. and higher to cause interference to a television set a few feet away, even with no antenna connected to the transmitter. Later, I discovered that touching the dials or running my hands along the a-c power cord increased the interference.

I pulled the transmitter from the cabinet and grounded the bottom rotor contacts of the variable condensers to the chassis  $\frac{1}{4}$ -inch below them. These grounds were in addition to the original ones. Then, noting that the tinned wire between the band-

switch and the coaxial output connector passed near the a-c cord under the chassis, I replaced the wire with a length of coaxial cable, grounding the outer braid to a mounting screw on the coaxial connector and to the chassis near the bandswitch.

These changes eliminated all TVI from direct radiation after the transmitter was replaced in the cabinet. In addition, the low-pass filter does a much better job of keeping interference off of the transmitting antenna. Only on 21 Mc. and 28 Mc. is there any TVI now—and it is very slight.

### Connecting The Antenna To The Filter

The simplest type of antenna to feed through a low-pass filter is undoubtedly a  $\frac{1}{2}$ -wave doublet (or a properly adjusted beam) fed in the center with coaxial cable. It is only necessary to put a coaxial fitting on the end of the cable, screw it to the low-pass filter, and adjust antenna coupling for the same power input as obtained without the filter.

Both low-pass filters and coaxial cables are usually available in either 52-ohm or 75-ohm impedance ratings. I would suggest standardizing on the 52-ohm types. Nevertheless, using a 52-ohm filter with a 75-ohm cable, or vice versa, will not prevent the filter from doing the job it was designed for.

3.7-Mc. and 7-Mc. doublets fed with 75-ohm "ribbon" can also be fed in the same manner. Theoretically, doing so should increase radiation from the line, but repeated tests have never indicated to me that it affects antenna performance on these bands. But I do not recommend such unbalanced operation on higher frequencies or with high-impedance feed lines.

Probably the most-used antenna by Novices is a random length of wire fed directly from a transmitter with a  $\pi$ -network output tank circuit. Unfortunately, this simplicity evaporates when an attempt is made to insert a low-pass filter between the

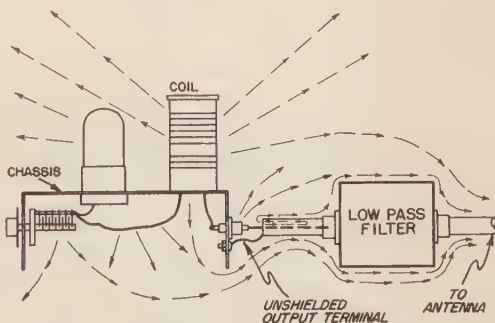


Fig. 4. A low-pass filter used in this fashion is almost valueless. The undesired harmonic r.f. energy radiates directly into TV sets, or flows around the filter to the transmitting antenna.

transmitter and the antenna. The usual result is very high amplifier plate current combined with practically no r.f. energy reaching the antenna.

The only practical solution is a link-coupled antenna tuner. See Fig. 5. To adjust it, first set the output condenser of the  $\pi$ -network to maximum capacity and tune the input condenser to resonance, as indicated by the plate current dip. Next, connect the tuner to the transmitter through the low-pass filter. Set  $C1$  to maximum capacity and clip the antenna to the top of  $L2$ . Turn on the transmitter



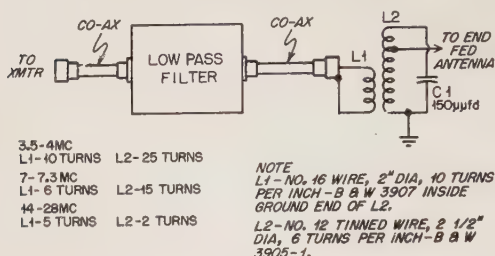


Fig. 2. Simple antenna coupler designed so that a low-pass filter may be used with an end-fed antenna.

and retune the input condenser of the *pi*-network for minimum plate, which may be higher than before. Tune *C1* for maximum plate current and again resonate the *pi*-network input condenser. Then, without touching *C1*, decrease the capacity of the *pi*-network condenser to bring the transmitter input up to normal, retuning the input condenser to resonance after each adjustment of the output condenser.

Should it be impossible to find a setting of *C1* that causes the final amplifier plate current to rise, tap the antenna down a few turns on *L2* and try again. Eventually you will find a position that will permit loading the antenna. In general, the closer the antenna is to being an integral multiplier of a  $\frac{1}{2}$ -wave long, the closer to the top of *L2* the antenna may be tapped.

On the other hand, if the amplifier plate current goes to a very high value, which cannot be reduced; as soon as the coupler is connected, add capacity in parallel with the *pi*-network output condenser until you can resonate the network with the input condenser.

Increase the capacity in steps equal to the maximum capacity of the output condenser. It may take quite a large amount of extra capacity to control the loading.

Other types of multi-band antennas are usually tuned up with the aid of a link-coupled antenna

tuner. If you have such a tuner, it is a simple matter to insert a low-pass filter in the link circuit. Should the addition of the filter cause the tuning to become erratic or parts of the link circuit to run warm, winding a new link coil around the antenna. The link winding may contain between a third and a half of the turns on the antenna coil. Vary load to the transmitter at the input link.

An antenna coupler may also be used with a fed dipole antenna fed with 300-ohm ribbon and with off-centered "Windom" antenna\* which is currently so popular with many amateurs. Either of these antennas may also be fed through a set of *Balun* coils. Full instructions for using these are packed with them.


Next month I hope to go into some other type of low-pass filters and supply some details of their mountings, etc. By the way, don't adjust the condensers in a filter to secure better loading—it just doesn't work that way.
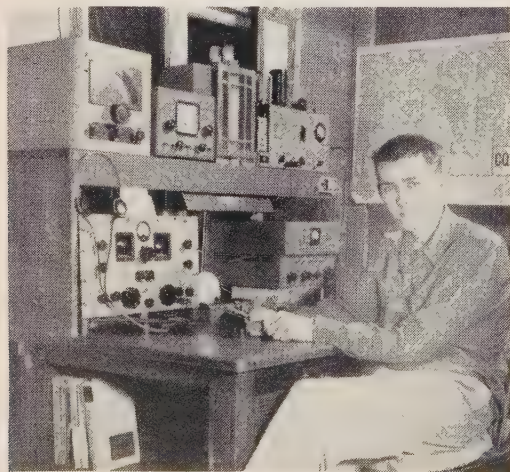
## Letters And General News

Regarding obtaining Novice and Technician Licenses by mail (the only way they are now issued) as described in the May column, the FCC has suggested a clarification regarding those eligible to administer the code examination. The following may administer it: Holders of amateur "Extra Class," "Advance Class" or "General Class" license. Also those who shall have held,



In four months of operation, Tommy, (1N3WST), has worked 38 states, Canada and Puerto Rico, with the equipment shown in this picture.




Ed, KN6BTY, Redding, California, and his 7-Mc. Novice station. Ed can hardly wait for his "General" so that he can call rare DX he hears outside the Novice Bands.

the five years prior to the date of the examination, commercial radiotelegraph license issued by the FCC within that time shall have been employed in the service of the United States as the operator of a non-commercial radiotelegraph station. Novice, Technician and Conditional Class licenses are not eligible to administer the code test.

Eligible persons who desire to be examined for a license should request the examination papers from the Engineer-in-Charge of the FCC radio district in which the applicant is located. The examination should be completed within fifteen days of the date it is received. For some reason, the examination cannot be completed within this time, the papers must be returned to the Engineer-in-Charge. In either case, the papers are returned to the FCC from which they were received.

Dick, WN9EJF, also asks two questions that may puzzle other Novices. "Dear Herb: Must a Novice desiring a "Technician Class" license take the examination by mail? Also, if you have a "Technician

\* See CQ, March, 1954, page 18.

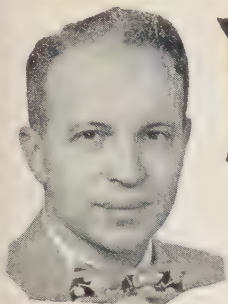


Leo I. Meyerson, WØGFQ  
C.U. on 10-20-40 & 75 Meters.

## Pay Only 10% Cash Down 18 Months to Pay on Major Equipment

Now it is easier than ever to buy from WRL. Pay as little as 10% down and the balance in 18 months. No red tape — we handle our own financing. We will give you a generous trade-in allowance on your present equipment. We have over 600 reconditioned used items — with new factory guarantee. Send for free list. You will profit most when you deal with WRL — THE WORLD'S MOST PERSONALIZED RADIO SUPPLY HOUSE and THE WORLD'S LARGEST DISTRIBUTOR OF AMATEUR RADIO TRANSMITTING EQUIPMENT.

Use WRL's EASY PAY PLAN  
10% Cash Down • 18 Months to Pay

COMPLETE  
BAND SWITCHING

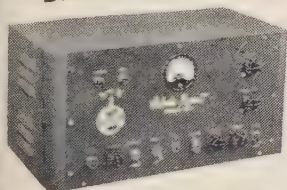

New Model 40A  
**GLOBE SCOUT**

50 Watts CW — 40 Watts Phone

**\$895** Per Month Kit Form  
(12 Months) **\$8995**

**\$10.00** Wired  
Cash Down **\$9995**

Complete bandswitching 160 thru 10 M. Combination pi-network antenna tuner. 3 stage modulator allows 100% modulation of final. Complete power supply.

### NC-183 D RECEIVER

Dual conversion on the three highest ranges plus every feature you want in a truly modern receiver!

(Less Speaker) ..... **\$38350**

**\$2090** Per Month  
18 Months  
**\$3835 CASH DOWN**

### HRO-60 RECEIVER

With Automatic Dual Conversion  
Less Speaker ..... **\$53350**

**\$2908** Per Month (18 Mo.)  
**\$5335 (CASH DOWN)**

LEO GIVES BEST DEAL ON ...


**National RECEIVERS**

Now Available  
For Immediate Delivery

**NEW NC-98**

**\$749** Per Month  
(18 Months)

**\$149.95** **\$1500**  
CASH DOWN

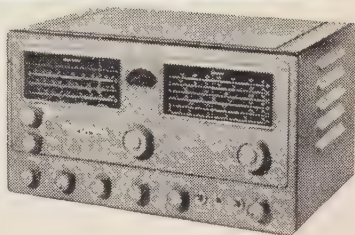

Here's unbeatable value! Now for the first time a crystal filter, an S-meter, choice of electrical bandspread on amateur or SWL bands, an RF stage and 2 IF stages and dozens of other high priced features for only \$149.95! **SPEAKER for NC 98—Only \$11.00**

**NC-88 (BUILT IN SPEAKER) \$119.95**

**\$954** Per Month  
12 Months

**\$1200**  
CASH DOWN

**FREE**

SEND TODAY

Check Our Generous Allowances  
We Need More Trade-Ins

### NATIONAL RECEIVERS AND ACCESSORIES

MODEL NO.	12 MONTHLY PAYMENTS	CASH DOWN	CASH PRICE
NC-125 RECEIVER	<b>\$15.89</b>	\$20.00	\$199.95
SW-54 RECEIVER	<b>3.97</b>	5.00	49.95
SELECT-O-JET	<b>2.29</b>	2.88	28.75
NFM-83-50 ADAPTER	<b>1.43</b>	1.80	17.95
<b>SPEAKER FOR HRO-60 OR NC-183D \$16.00</b>			



C-7

WRITE FOR DETAILED EQUIPMENT SPECIFICATION SHEETS



**World Radio LABORATORIES**

WRITE - WIRE - PHONE 2-0277 COUNCIL BLUFFS, IOWA

WORLD RADIO LABORATORIES  
3415-27 W. Broadway  
Council Bluffs, Iowa

Please send me:

- ☐ New Log Book **25c**  
☐ Free Catalog  
☐ Radio Map **25c**

- ☐ NC-98 Info.  
☐ NC-88 Info.  
☐ GLOBE SCOUT Info.  
☐ Used Equipment List

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_




# What's NEW

# in HAM RADIO
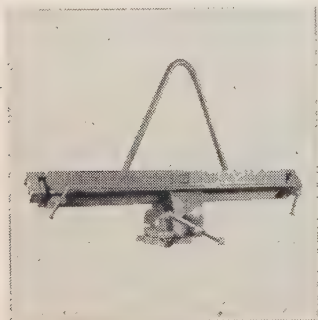
## Parts Products Catalogs

(Tell them you saw it in CQ)

By Jove, why didn't some chappy think of this before? Here is an imported English sheet metal brake! Now you can bend aluminum, copper, brass and light steel to form boxes, chassis and brackets without having to use a hammer and the edge of an apple crate! This A. B.



Parker sheet metal folding machine clamps in any heavy workshop vise and is ready to go. This is a "natural" for any Ham that does any construction work at all, and is a "must" for small shops, schools and laboratories. Want one? I thought so! Just write to their representative for all the details: Television Accessories Co., Dept. 11, Box 6001, Arlington 6, Va. The retail price is \$14.95, F.O.B.


All the Hams at Barker & Williamson put their heads together with the engineering staff, and when the smoke and fury had cleared away, the preliminary design of the B&W Model 5100 had been sketched out. As you well know, it takes ardent amateurs to fully realize what the average Ham wants in the way of a transmitter, and B&W really hit the bull's-eye in their latest design: The Model 5100 is a 150-watt CW (135-watt phone transmitter) designed for v.f.o. operation on all bands! Yessir, the 5100 has a built-in calibrated v.f.o., is fully band-switched and contains all the latest engineering advances to effectively minimize TVI. Intended for permanent station operation, the transmitter may be used to drive a high powered r-f final amplifier and class "B" modulator. The Model 5100 employs a pair of 6146 tubes in a pi-network output circuit. A string of 6AQ5 doubler stages follow the 6BJ6-6BJ6 v.f.o./buffer unit. Unitized construction is used throughout for easy servicing.

The CW men will be interested in the beautiful keying waveform provided by the blocked-grid keying system. No chirps, no pops, no cracks! It really sounds beautiful. The phone men will be glad to



know that B&W is bringing out a matching adapter for single-sideband operation of the Model 5100. Sure sounds like a good little rig, doesn't it? See a B&W 5100 transmitter NOW at your local Ham store!

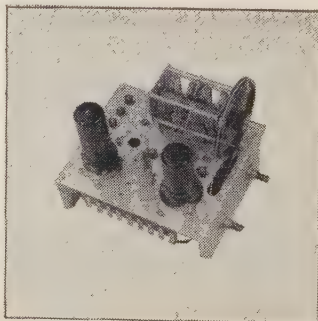Want a v.f.o. exciter the easy way? Tired of building up chirpy-



blurpy VFO's and parasitic-infested doubler stages? Disgusted with TVI? Well, just cast your eyes on this little gem. The GELOSO v.f.o. exciter. This imported unit employs a 6J5 Clapp oscillator, 6AU6 isolation stage, and a 6V6 frequency multiplier, providing sufficient output on 80, 40, 20, 15 and 10 meters to drive any of the popular pentodes (807, 2E26, 6146, etc.). A full vision, calibrated dial cover-

ing the above bands is supplied. Measuring only 5½x6½", the exciter provides the basic heart of your new rig, fixed or mobile. sir, it's not a kit—fully wired and aligned—all set to go the moment you hook it to a suitable power supply. It certainly looks like an easy way of getting on the air.

The exciter is manufactured in Italy by Geloso Electronics Co., one of the largest manufacturers of electronic equipment in Southern Europe. The exciter has been used in many foreign countries some time (See JY1US, page Jan. 1954, QST), and arrangements have now been made to import it into the United States. For the story on this popular little exciter, write to Gilfer Associates, Box 17, Grand Central Station, New York 17, N.Y.

Attention all SSB fans! Hear this! A new, improved version of the popular Multiphase 10A exciter has been announced by Geloso Electronics, Inc. This new unit is known as the Model 10B and contains several new operating features, such as carrier insertion, "tune" operation of the exciter, new audio input circuit has been added for two-tone tests or patch input. A new voice control relay is also provided with a receiver muting circuit.

The new Model 10B provides 10 watts of peak output on all bands, 10 to 160 meters, using 600 ohm coils. Those Hams still stuck



to AM will be happy to know it has over 40 db. of unwanted carrier suppression. You can use this baby without using a v.f.o.! Further information on the Model 10B and other Geloso products is available.

(Continued on page 4)

*For* **LONG TRADES**

**LOW TERMS**

*See* **Henry**



Bob and Ted Henry, with stores in Butler, Mo. and Los Angeles, Calif., carry complete stocks of all ham equipment for immediate delivery. Bob and Ted, being hams themselves, know you want easy terms, truly top trade-ins, low prices, and fast delivery, and you get them all from Henry.

### TOP TRADE-INS—

Henry wants to trade and trades big. YOU get truly liberal allowances on your equipment. We also pay cash for used equipment.

### EASY TERMS—

The best terms anywhere because Henry finances all the terms with his easy time payment plan. 10% down (or your trade-in accepted as down payment).

### FAST DELIVERY—


Shipments 4 hours after receipt of order. Send only \$5.00 with order, and shipment will be made COD immediately.

### SAISFACTION—

Ask any ham about Henry Radio Stores. We want you to be satisfied. 10 Day trial on all receivers.

Henry has

# hallicrafters

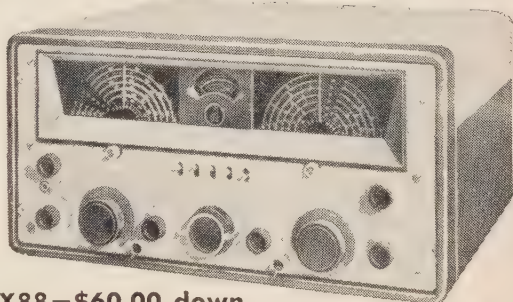


### SX88—\$60.00 down

18 monthly payments of \$32.40—\$595.00 Cash Price

**SELECTIVITY**—For the first time, selectivity from 10 KC to 250 cycles in six steps. Single side band suppressed carrier.

### SX71

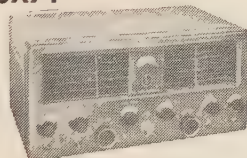

### \$25.00 Down

18 monthly payments of \$13.60 —\$249.95 Cash Price.

For top performance with extra pull power and ability to tune in stations. Covers broadcast band 560-1600 KC plus four short-wave bands covering 1650 KC-34 MC and 46-56 MC.

	Cash Down	18 Monthly Payments	Cash Price
S38C	\$ 5.00	\$ 2.61	\$ 49.95
S53A	10.00	5.45	99.95
S40B	12.00	6.54	119.95
S76	20.00	10.89	199.95
SX62A	35.00	19.07	349.95
HT20	45.00	24.50	449.50

Some demonstrators available at reduced prices.

You just can't beat HENRY for Long-Trades on these items. Find out Today!

Write, wire, phone or visit either store today.

## Henry Radio Stores

Butler 1, Missouri  
Phone 395



BOB HENRY  
W0ARA



BRadshaw 2.2917

11240 West Olympic Blvd. Los Angeles 64



W6U0U  
TED HENRY





# The VHF-UHF News

FURMAN C. COBB

c/o CQ Magazine, 67 West 44th St., New York 36, N.Y.

Well, there is no question about the first transcontinental 144-Mc. relay being a success, but it is fairly difficult for this columnist to write it up. Although it is June 7, we have no reports from west of Dallas, Texas on the problems that faced the crews in W6 and W7 land. Since the eastern terminal of the message turned out to be W1HDQ we can scarcely expect any news from that quarter. Inasmuch as CQ was the instrument of getting this thing started (see the January and March issues) we feel obliged to say many thanks to those who appreciated all of our efforts. No claim is being made that we were the only people involved, but it would appear reasonable to have expected some cooperation from the many fellows that proclaimed interest. I expect that it looked like "too good a thing" for the "come latelies" not to crowd out a newcomer with a good idea.

On the credit side of the ledger I do want to express my warm thanks to W2ORI, W2UK, W5AJG, W8WXV and W9WOK for their thoughtfulness in immediately dispatching to me carbon copies of their activity reports. Much credit is due to the *Two Meter and Down Club* which sparked the effort from west of the Mississippi River. In this regard, I believe that Bill Myers, W6IHK, did an outstanding job through his bulletins and letters.

## The Messages

By my count there were twelve messages that covered over 1000 miles. These included messages

from W1HDQ, W2QED, W5CA/7, W6W6IHK/7 and WØZJB. Not all of them were ed from coast to coast. The principal coast-to-coast message was #2 from W6EMM. I am given derstand without possible confirmation from W that it took a total of 15 hours. However, the rumor that the delay was here in the east due absence of W1HDQ. No message was received CQ so I'm not in a position to state the actual elapsed time.

A newspaper report appeared in the *New Times* on Tuesday, June 1 and seems to have initiated by W5CA/7 from atop Capillo Peak, Mexico. It stated that good conditions enabled success of the venture, although this seems agree with other observations.

J. C. Miller, W2ORI (Lockport, N.Y.) was ing in on both W2UK and W8WXV and st by in case they should have trouble over the mile path. Conditions are reported by W2 being above normal on Saturday morning and approximately 6:00 p.m. that evening. Then tions rapidly changed to the poorest observed a year. . . . R. E. Thomas, W2UK (New Brunswick, N.J.) handled ten messages and credits the lent cooperation of W2ORI as being of tremendous value in keeping things moving. . . . Leroy W5AJG (Dallas, Texas) handled nine messages May 29 when conditions were poor, although improved during the evening. As might be ex

(Continued on page 46)



This was operating post W6EMM while original first trial message on. In the back row are: Jr.; W6IHK, W6GUE, and KN6EGP. Seated W6AEA, W6MJ and This was another ph "Max."

# CRYSTALS

*Guaranteed to oscillate!*  
*Your choice of frequencies!*  
*Largest selection in the world!*

## NOTE!

Every crystal tested for activity before shipment! All nos. listed are fundamental frequencies in kilocycles.

### FT-243

Lots of 10 or more, Ea. .... **.69c**  
Lots of 5 or more, Ea. .... **.79c**  
Individually, Ea. .... **.99c**

1110	2450	2715	3015	3455	6362	7500	8000
1129	2455	2720	3020	3465	6373	7510	8006
1150	2460	2725	3025	3500	6375	7520	8008.3
1195	2465	2730	3030	3510	6405	7530	8010
1252	2470	2740	3035	3525	6406	7540	8016.7
1900	2475	2750	3040	3540	6425	7550	8020
1915	2480	2750	3045	3580	6440	7560	8025
1930	2485	2755	3050	3583	6450	7570	8030
1940	2490	2760	3055	3640	6473	7580	8033.3
1950	2495	2765	3060	3655	6475	7590	8040
1965	2500	2770	3065	3680	6500	7600	8041.7
1985	2505	2775	3070	3700	6506	7610	8050
2000	2510	2780	3075	3760	6525	7620	8058.3
1980	2515	2785	3080	3800	6540	7630	8060
1985	2520	2790	3085	3825	6550	7640	8066.7
2010	2525	2795	3090	3885	6573	7650	8070
2015	2530	2805	3095	3940	6575	7660	8073.3
2020	2535	2810	3100	3955	6600	7666.7	8075
2017	2535	2830	3105	3980	6606	7670	8080
2020	2545	2835	3110	3990	6625	7680	8083.3
2025	2550	2840	3115	3995	6640	7690	8090
2035	2557	2845	3120	4000	6650	7700	8091.7
2040	2560	2850	3125	4006	7000	7710	8100
2055	2565	2855	3130	4025	7006	7720	8106.6
2060	2570	2860	3135	4040	7025	7730	8108.3
2065	2575	2865	3140	4042	7040	7740	8111.0
2090	2580	2870	3145	4050	7050	7750	8116.7
2105	2585	2875	3150	4073	7073	7760	8125
2125	2590	2880	3155	4075	7075	7770	8130
2130	2595	2885	3160	4100	7100	7780	8133.3
2135	2600	2890	3165	4106	7106	7783.3	8140
2140	2603	2895	3170	4125	7125	7790	8141.7
2145	2605	2900	3175	4140	7140	7800	8150
2155	2610	2905	3180	4142	7150	7810	8158.3
2165	2615	2915	3185	4150	7160	7820	8160
2175	2620	2920	3190	4173	7173	7830	8163.4
2180	2625	2925	3195	4175	7175	7840	8166.7
2195	2630	2930	3200	4185	7200	7850	8170
2300	2635	2935	3202	4200	7206	7860	8173.3
2305	2640	2940	3205	4206	7225	7870	8180
2320	2645	2945	3210	4225	7240	7880	8183.3
2350	2650	2950	3220	4235	7273	7891.7	8190
2355	2655	2955	3225	4240	7275	7890	8191.7
2360	2660	2960	3230	4250	7306	7900	8200
2365	2665	2965	3235	4273	7300	7910	8206.6
2370	2675	2970	3240	4275	7325	7920	8208.3
2375	2680	2975	3240	4300	7340	7930	8210
2390	2685	2980	3300	4306	7350	7940	8216.7
2415	2690	2985	3310	4315	7375	7950	8220
2430	2695	2990	3320	4325	7400	7960	8225
2435	2700	2995	3340	4335	7406	7970	
2440	2705	3005	3410	4340	7425	7980	
2442	2710	3010	3420	4350	7440	7990	

### DC-34 & DC-35

PIN SPACING 3/4"

Your Choice, Ea. only — **.99c**

1690	2422	2745	3155	3630	3890	4130
1705	2155	2435	2764	3161	3650	3895
1720		2446	2775	3190	3655	3905
1738	2175	2466	2776	3201	3685	3920
1746	2195	2467	2807	3279	3695	3935
1770	2202	2478		3280	3700	3940
1790	2215	2491	2831	3280	3700	3940
1810	2220	2500	2851	3297	3702.5	3950
1830	2235	2510	2853	3311	3705	3960
1850	2240	2514	2894	3317	3710	3965
1870	2255	2527	2895	3365	3730	3985
1890	2258	2540	2899	3385	3745	3995
1910	2275	2559	2925	3390	3750	4010
1930	2280	2586	2926	3395	3760	4015
1950	2295	2587	2960	3412.5	3765	4020
1970	2310	2605	2971	3422.5	3770	4030
1990	2315	2625	2980	3462	3775	4035
2010	2326		3000	3480	3790	4050
2030	2335	2643	3010	3485	3792.5	4055
2050	2340	2665	3023	3500	3807.5	4065
2075	2355		3027.5	3520	3825	4080
2082	2360	2685	3055	3540	3830	4085
2090	2375	2710	3077.5	3555	3850	4090
2105	2390	2711	3095	3575	3855	4095
2106	2395	2725	3117	3580	3870	4097.5
2131	2415	2732	3149	3610	3885	4115

### FT-241 LOW FREQUENCY CRYSTALS

Lots of 10 or more, Ea. .... **.79c**

Lots of 5 or more, Ea. .... **.89c**  
Individually, Ea. .... **.99c**

451	456	461	465	470	476
452	457	462	466	472	477
446	448	453	450	463	468
447	450	454	459	464	469

## NOVICE BAND

## FUNDAMENTAL FREQUENCIES

Individually, Ea. .... **\$1.25** Lots of 10 or more, Ea. .... **.99c**

AVAILABLE IN EITHER DC-34 OR FT-243 HOLDERS. Specify your needs.

Frequencies in steps of every 1 KC: from 3701 THROUGH 3748. Example: 3701, 3702, 3703, etc.  
FOR DOUBLING INTO 7 MC BAND. Frequencies in steps of every 1 KC: from 3588 THROUGH 3599. E.g. 3588, 3589, etc.

## NOVICE BAND FUNDAMENTAL FREQUENCIES AVAILABLE IN FT-243 ONLY.

Individually, Ea. .... **\$1.25** Lots of 10 or more, Ea. .... **.99c**  
All frequencies from 7175 KC THROUGH 7198 KC in steps of 1 KC, fractions omitted. Examples: 7175, 7176, 7177, etc.

## MISC. & SHIP BAND FREQUENCIES

81.95 KC Octal tube type (Used in SCR-584 & SPM-1) ....	\$3.99	2638 KC DC-34 ....	\$2.99
200 KC FT-241 ....	1.99	2638 KC FT-243 ....	2.99
200 KC Type DC-15 in octal tube holder ....	1.99	2642 KC FT-243 ....	2.99
327.8 KC No. D-16834P. (Used in TS-102/AP) ....	9.95	2647 KC FT-243 ....	2.99
500 KC FT-241 ....	1.99	2670 KC DC-34 ....	2.99
1000 KC FT-241 ....	2.49	2738 KC type I-C ....	2.99
1000 KC Type DC-9, in octal tube holder ....	3.45	2738 KC FT-243 ....	2.99
2000 KC FT-243 ....	1.99	2738 KC MC-7 ....	2.99
2142 KC DC-34 ....	2.99	3000 KC FT-243 ....	1.99
2174 KC DC-34 ....	2.99	3088 KC FT-243 ....	2.99
2182 KC FT-243 ....	2.99	3093 KC FT-243 ....	2.99
2500 KC FT-243 ....	1.99	3098 KC FT-243 ....	2.99
2632 KC FT-243 ....	2.99	3103 KC FT-243 ....	2.99
2637 KC FT-243 ....	2.99	3188 KC FT-243 ....	2.99
		3193 KC FT-243 ....	2.99
		3198 KC FT-243 ....	2.99
		3203 KC FT-243 ....	2.99
		5000 KC FT-243 ....	1.99
		10,000 KC Type SR-5 ....	1.99

## FT-243

Lots of 10 or more, Ea. .... **.34c**  
Lots of 5 or more, Ea. .... **.49c**  
Individually, Ea. .... **.49c**

4035	4540	5090	5675	5892	6400	6973	7975
4045	4580	5127.5	5687.5	5900	6406.6	6975	8240
4080	4610	5165	5700	5906.7	6425	7450	8250
4095	4620	5180	5706.7	5907.5	6673.3	7473.3	8273
4110	4635	5205	5725	5925	6675	7475	8275
4135	4680	5235	5730	5940	6700	7506.6	8300
4165	4695	5245	5740	5950	6706.6	7525	8306
4175	4710	5285	5750	5955	6725	7573.3	8325
4190	4735	5295	5760	5973.3	6740	7575	8340
4215	4780	5300	5773.3	5975	6750	7606.6	8350
4220	4785	5305	5775	5995	6773.3	7625	8375
4255	4815	5327.5	5780	6206.6	6775	7673.3	8400
4280	4820	5335	5782.5	6225	6800	7675	8425
4295	4840	5385	5800	6240	6806.6	7706.6	8450
4300	4845	5397.5	5806.7	6250	6825	7725	8475
4330	4852.5	5435	5820	6273.3	6840	7773.3	8500
4340	4880	5437.5	5825	6275	6850	7775	8525
4395	4900	5485	5840	6300	6873.3	7806.6	8550
4397.5	4930	5500	5850	6306	6875	7825	8575
4445	4950	5545	5852.5	6325	6900	7873.3	8600
4450	4980	5582.5	5860	6340	6906.6	7875	8625
4490	4995	5587.5	5873.5	6350	6925	7906.6	8650
4495	5030	5645	5875	6373.3	6940	7925	8675
4535	5035	5660	5880	6375	6950	7973.3	8690



## FT-171

Lots of 10 or more, Ea. .... **.79c**

Lots of 5 or more, Ea. .... **.89c**

Individually, Ea. .... **.99c**

1151.8	2150	2415	2911	3510	3807.5	4050	5225
1562.5	2155	2435	2940	3520	3810	4080	5492.5
1738	2191	2442.5	2967	3550	3812.5	4097.5	6000
1746	2220	2467	2990	3562	3825	4110	6210
1940	2258		3010	3569	3870	4112	7165
2010	2260	2500	3010.5	3570	3880	4177.5	7950
2030	2280	2532.5	3175	3580	3945	4245	8000
2040	2282.5	2545	3202.5	3637.5	3950	4255	9200
2045	2290	2550	3205.5	3660	3955	4280	9590
2065	2300	2557	3215	3687.5	3966.5	4310	
2082	2305	2582	3237.5	3682.5	3970	4345	
2105	2320	2630	3250	3695	3975	4350	
2123	2340	2665	3322.5	3700	3980	4360	
2125	2360	2725	3400	3712.5	3995	4400	
2131	2390	2780	3422.5	3760	4012.5	4735	
2145	2405	2835	3500	3790	4037.5	5200	

Indicate second choice freqs. wherever substitutions may be made.  
**NOTE!** All items subject to prior sale and change of price without notice. MINIMUM ORDER: \$2.50. All orders MUST be accompanied by check, cash or M.O. WITH PAYMENT IN FULL. NO C.O.D. CALIFORNIA BUYERS add sales tax. INCLUDE APPROXIMATELY 5c PER CRYSTAL FOR POSTAGE. DEALERS & JOBBERS: WRITE FOR SPECIAL QUANTITY DISCOUNTS. Be sure to ask for FREE crystal catalogue giving complete list of frequencies.

**U. S. CRYSTALS, INC. DEPT. C**

805 S.





got enough EARS?

BE ON THE CONSTANT ALERT

All Departments Can Now Listen to Every Vital Message

**MONITORADIO** for a thoroughly coordinated 2-way communication system.

Now every member of every department can have radio communication for as little as \$49.95

Write today for further information.

- Nation's most complete line of monitor receivers.
- Crystal controlled or tunable for any VHF FM communication system.
- Mobile or stationary receivers.
- Prices to meet any budget.
- Certified for civil defense use.


**MONITORADIO RADIO APPARATUS CORPORATION**

55 North Jersey St., Indianapolis, Ind. Phone: ATLantic 1624

(from page 40)


writing the manufacturer at 1247 W. Belmont Ave., Chicago 13, Ill. Ask for W9DYV.

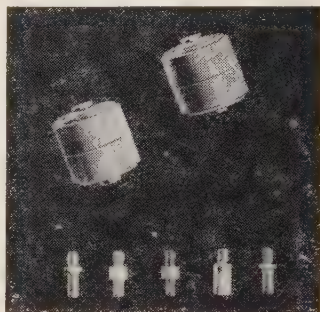You still can't beat the Centralab Hi-Vo-Kap condensers for high-voltage TVI filters in the Ham rig. True, these 500  $\mu$ fd. 20,000-volt condensers are designed to be used in the picture tube supply in TV sets, but that is a minor affair in the Ham's world. These new condensers are designed so the terminals will not twist out or break off. Even Heavy-handed Harry can drop



'em on the floor and step on with no harm done except to bunions.

All Centralab Hi-Vo-Kaps tested at twice rated working age on the basis of 1000-hour load tests, and each unit is tested before shipping. Internal ductance is low, and two of condensers placed each side v-h-f choke will prevent harmonic currents from running rampant on your power leads! Write for letins 28-2 and 42-201 for complete details on these interesting components. Centralab, 900 East Avenue, Dept. E44, Milwaukee, Wisc.

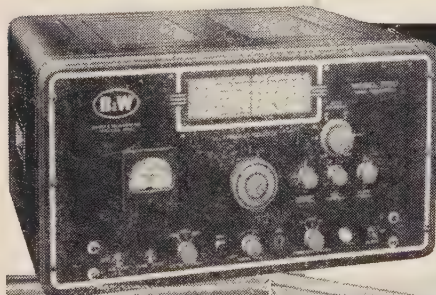




## Bonus Features in the B&W model 5100 Transmitter

Only B&W Offers all these Features

at this  
Low Price

**\$442.50** Am  
N

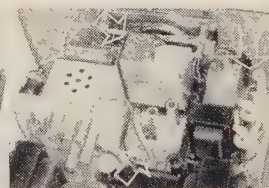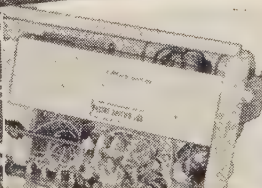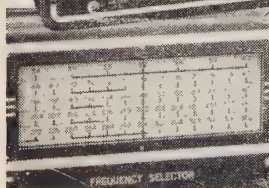Factory wired & tested  
complete with tubes



**Built-In VFO**—Accurately calibrated for 80, 40, 20, 15, 11, & 10 meter bands. Over 7" of dial space.

Optional crystal control using 80 meter crystals. Separate circuitry assures clean, clear keying at all speeds on both VFO or crystal operation.

**Built-In Low Pass Filter**—Pi-network final followed by low-pass filter (75 ohm unbalanced output), plus functional cabinet design and thorough bypassing of all critical leads, keeps TVI to a minimum.

**Unitized Construction**—Any major section (oscillator, multiplier, etc.) is quickly un-plugged and easily removed for servicing. Found only in the B&W Model 5100.

**Watch for this B&W**

A companion Single band Adapter for the 5100 available by Sept. Housed in a smaller, more compact cabinet, the B&W Adapter will let you operate on either CW, AM telephony or SSB with comparable power output on all bands. The B&W Model 5100 Transmitter Will Never Grow Old.

**BARKER & WILLIAMSON, Inc.**

237 Fairfield Ave., Upper Darby, Pa.

Input Pwr.—150 watts CW  
135 watts PEP  
Size—22" w., 11 1/2" h.,  
Weight—95 pounds.

another great first  
from the inventor of the Walkie-Talkie

# INDUCTO - PATCH

## Now - 2-Way inductive telephone patching

No Fuss, No Bother—  
Just Set Your "Phone"  
in the Inducto-Patch  
  
Easy to Install



No R.F. Feedback—  
No Interference with  
the Telephone System  
  
Simple Operation



**\$9.95**  
PPD.

**NO PHYSICAL  
CONNECTION TO  
THE TELEPHONE!**

**FREE!**  
**W6TXG**

To introduce Inducto-Patch, a Call-Letter Plate with your Call-Letters engraved in gold, will be given free with each purchase.

### EDWIN B. BLOCK

One of the nation's leading electronic designers for over 25 years, and now Chief Engineer of Abernathy Electronics. Inventor of the I.F.F. System, the first successful condenser microphone, the telephone induction coil, and credited with much of the development of the world-famed Walkie-Talkie.

### SPECIFICATIONS:

#### Physical

Weight ..... 10 ozs.  
Size ..... 6"x4"x3" high  
Color ..... Telephone Black

#### Electrical

To Xmtr    From Receiver

Impedance	25KΩ	3.2 to 500Ω
Power	-60 DB	1.5 to 5 watts
Cable	Shielded	Speaker Cord

## Now! Two-Way inductive telephone patching

Simply lay telephone handset in the Inducto-Patch and the exclusive "Inducto-Patch Circuit" (patents pending) does the rest. Easily installed in your rig. Operates automatically with your "Send-Receive" Relay or Switch. Completely equipped with shielded cable, the Inducto-Patch circuit assures perfect telephonic transmission and reception.

The Inducto-Patch is expressly designed to accomplish an inductive coupling to the land lines in BOTH directions.

By an exclusive method (patents pending), Abernathy Electronics Chief Engineer, Edwin B. Block, has perfected transduction INTO the land lines (from your radio receiver to the telephone conversant) by the Law of Magnetic Energy Transfer.

The comparatively simple and well-known principle of inducing the signal FROM the telephone instrument into the input of an audio system was also perfected by Edwin B. Block (1945). This input coil is widely used for telephone recording, monitoring, and as an audio probe. By a combination of transduction and induction, and a receptacle for the telephone receiver end of the handset, TWO-way Inductive Telephone Patching has been accomplished FOR THE VERY FIRST TIME.

Inducto-Patch carries a positive Money-Back Guarantee. Complete directions, ten feet of shielded cable, and a plate bearing your call-letters accompany your Inducto-Patch.

## ORDER TODAY!

**Abernathy Electronics, Inc.**

Winnetka, California

# INDUCTO-PATCH

**ABERNATHY ELECTRONICS, INC.**

**Winnetka, California**

Gentlemen: Enclosed please find \$\_\_\_\_\_ for \_\_\_\_\_ Inducto-Patch(es) @ \$9.95 each.


Name \_\_\_\_\_ Call Letters \_\_\_\_\_

Address \_\_\_\_\_ City \_\_\_\_\_ Zone \_\_\_\_\_

State \_\_\_\_\_


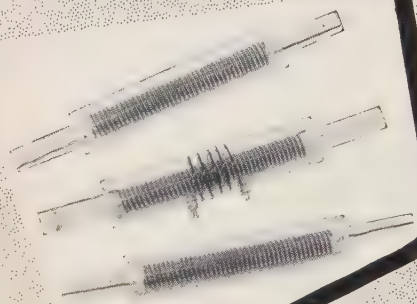
# build Your 'V-P' BEAM with "ORIGINAL" DESIGN



## MOSLEY 'V-P' Loading Coils

Whether you're running ten watts or the full gallon — for top performance from your V-P Beam, use *Factory Made and Factory Matched* MOSLEY V-P LOADING COILS! Only MOSLEY is licensed by the designers of the V-P Beam, W0VZC and W0QFG, to manufacture the *Original Design* Coils that make this amazingly efficient, compact 20 Meter Beam possible!

- Performance Comparable To Full Size Beams When Matched With Elements Of Proper Length!
- Sturdy — Completely Weather Protected!
- All Metal Parts Non-Ferrous!

Cat. VP20-2, 2 Element, 20 Meter Coils.  
Amateur Net \$16.95

Cat. VP20-3, 3 Element, 20 Meter Coils.  
Amateur Net \$24.95

\* See May '54 QST — P. 27

Available From Your Favorite Radio  
Parts Or Ham Equipment Jobber

**Mosley**  
*Electronics, Inc.*

8622 ST. CHARLES ROCK ROAD  
ST. LOUIS 14, MISSOURI

## VHF NEWS

(from page 42)

conditions on the 30th were much better and was worked in all directions. CW was used bet. W5AJG and W5UZW. The W0ZJB Msg. #9 to Mayor of Houston was put on the air from K7AM during their 2200 CST newscast. . . . *Al Blum* (Shiloh, Ohio) says that there was much traffic for the poor conditions, but is very glad that everything turned out o.k. . . . *John Lantz* (W9WOK (Bensenville, Ill.) was busy on both 29th and 30th and adds that W8SRW, W8W9BPV, W0IHD and W0ETJ should also be given credits for valuable assists.

## V.H.F. Scatter

The attention of a certain contemporary writer directed to the "World's Record" on the 420-Mc. which is held by F9BG and FA8IH over a distance of 610 miles. . . . The first XE to XE 144-Mc. contact place on May 16 between XE1VA/mobile (using a picture in CQ, May 1954 on page 62) and Jeff XE1GL near Cuernavaca. . . . Speaking of 144 operation in Mexico. A recent visitor to the CQ offices was Roberto Villaseñor, XE2FC, of Toluca. Roberto is putting finishing touches on a rig for a band with 100 watts input. He will use it with an element beam. Quite a bit of TV DX has been reported in Tampico and Roberto hopes for contacts across the Gulf. . . . Can you imagine the surprise of Don VK2NO, a few months ago when he received a report from Dimitir Sibirsky, Sofia, Bulgaria on 144 Mc. CQ. The report was for May 8, 1947! It came out to within two hours and seems to be on target and up. Oddly enough, the report not only took years to reach Don, but was also postmarked Piquette, Ohio. Can any of our readers explain?

## What the Gang Is Doing

Louie Cox, W7ACD (Shelley, Idaho), says that fellows should've paid attention to the "Piggyback" pre-amp that was described in the June 1953 issue of CQ. Lou reports that he is using one on 6-meters and it really helps out on those weak signals. W7ACD also heard or worked the following on 50-Mc. in the month of May: W5SFW, W5HVP, W5MJD, W0HWW, W0ZJB, W6ANN, W0WKB, W9VZF, W6EIB, W6BWG, W9QUV, W0YUQ, W9WOK, W4CPZ, W4QXC, W6TMM and W6TBT. The band was open on May 13, 22 and 26 from Shelley.

Sam Thompson, W7POL (Klamath Falls, Oregon) reports that he is getting ready to fire up on both 2 meters. He plans on a 600-watt rig with a Tera converter ahead of his NC-183 on 2 meters. A "Back" ahead of the receiver will be used on 6. The tennas will be a 12-element beam on 144 and a 4-element on 50 Mc. Good luck to Sam on stirring up a job in a rare spot.

Hartzell Boren, W9FVI (Greenwood, Ind.) sends long letter complaining about the lack of "John" John" dope in the column, but not one word on 144 in his area. I must admit to some confusion at this point. How is this department to obtain said information? Maybe W9FVI can supply some carrier for his letters don't have anything "printable" in them.

C. G. Hoffman, W9ZHL (Terre Haute, Ind.) says to forget the annual VHF Picnic at the Turkey State Park on July 25th. This has always been a disappointing VHF meeting in the mid-west and is never attended. If possible, be sure to come and make sure you've been working on the air. Chuck also reports the 6-meter CD net is moving along and now includes mobiles and 10 home stations with activity throughout the entire day.

Have you a copy of the  
"Mobile Handbook?"

Have you ordered "Single Sideband  
Techniques?"

## ANTENNASCOPE-54

(from page 20)

onic frequency to harmonic frequency. Fig-  
e 5c shows the current distribution of a 3rd-  
harmonic antenna, also called three half-waves.  
Notice that it contains as many high-current  
points as there are  $\frac{1}{2}$ -waves in the antenna.  
The Antennascope may be connected at any  
of them to analyze the antenna. Also, a low-  
impedance feed line may be connected at any  
of them, although better balance is obtained  
feeding it as close to the center as practical.  
In general, the first maximum current point in  
any antenna occurs  $\frac{1}{4}$ -wave from the end, with  
subsequent, high-current points occurring each  
end  $\frac{1}{4}$ -wave from the end.

If the Antennascope meter should indicate  
current flow when the Antennascope is connect-  
ed to a long antenna and before the Dipper is  
connected, then, in all probability, r-f energy  
is being picked up by the antenna from a pow-  
erful broadcast station. By plugging a pair of  
phones into J1 of the Antennascope-54 or con-  
necting them in series with one meter lead on  
the Antennascope Jr., the interfering signal can  
be identified aurally.

Often, reversing the antenna connections to  
the Rx terminals will drop the strength of the  
desired signal to zero. Or, if it is not too  
strong, the Dipper may be tone modulated\*,  
and the Antennascope nulled for minimum  
length of the tone in the phones. Other-  
wise, you will have to wait until the interfering  
station leaves the air before testing the an-  
tenna.

### High-Impedance Measurements

On occasion, it may be necessary to measure  
very-high impedance, such as the feed point  
of certain co-linear arrays Fig. 5d. A  $\frac{1}{4}$ -wave  
line may be used to bring the impedance with-  
in the range of the Antennascope. Knowing  
the line impedance ( $Z_0$ ) and the resistance of  
the load ( $Z_L$ ) required to produce a null, the un-  
known impedance is easily calculated by re-  
arranging formulas (2) or (3):

Most grid-dip oscillators can be tone modulated by  
inserting the output of a small audio oscillator into  
their phone jacks.

(Continued on next page)

## UHF TRANSMITTER-RECEIVER

APS-13

\$495



Freq. range 415-  
420 MC. 5 stages  
of 30 MC. IF ampli-  
fier. Complete with  
R.F. and I.F. sections. Less dynamotor, tubes, and tube shields.  
With schematic. Excellent condition. A HOT BUY!

### ARB NAVY RECEIVER

105 to 9050 KC. Four Bands, Calibrated Dial, LF-Ship-BC  
—80 & 40 Meter—Complete with Tubes and Dynamotor. For  
24 Volt operation; easily converted to 110 V—12 or 8 Volt  
Size: 8 1/4" x 7 1/4" x 15 1/4". Excellent cond. **\$24.50**

DU-1. DIRECTION FINDER LOOP AMPLIFIER for ARB  
receiver. With tubes and loop. **\$19.95**  
Excellent condition with schematic.

## C.A.P. SPECIAL

### BC-625 VHF TRANSMITTER

Freq. range 100-156 MC. With modulation section and  
speech amplifier. Less tubes & crystals, with con-  
version dope. Used, good condition. (See Nov/53 CQ.) **\$9.95**

### ARC-5/R-28 2-METER RECEIVER

Here is the 2-meter superhet you have been looking for!  
Absolutely one of the BEST available today! Tunes from 100  
to 156 Mcs. in four crystal channels. (Easily converted to  
continuous tuning.) Tube lineup is as follows: 717A—R.F.,  
717A—Mixer, 2—12SH7—1st & 2nd I.F. 16.9 **\$24.50**  
Mc. Excel. Cond. See Dec./53 CQ for conversion.  
16.9 Mc. EXCEL. COND. See Dec./53 CQ for conversion

### TG-34A PORTABLE KEYS

115 or 230 V. @ 50 to 60 cycles. Reproduces audible code  
practice signals, by use of self-contained speaker activated by  
dit-dahs recorded on paper tape. Also provides keying oscillator  
for use with hand key. Approx. wt: 45 lbs.

BRAND NEW..... **\$24.50** USED..... **\$14.50**

### ARC-4 MOBILE TRANSCEIVER

140-144 MC. Complete with control box, tubes, 12/24 VDC  
dynamotor with schematic. This is a special **\$32.50**  
reduction for this month only. Like new.....

RS-38 MIKE. Carbon type for ARC-4. NEW..... **\$4.95**  
Used..... **2.75**

### TG-10 CODE PRACTICE SET

Includes push-pull 6L6 amplifier, variable speed synchronous  
drive motor and rewind. Complete with tubes, but less tape  
and reel. CHECKED OUT. Approx. wt: 65 lbs. **\$22.50**  
Excellent condition .....

### MP - 22 MOBILE ANTENNA MOUNTING

Per PAIR..... **\$3.50** EACH..... **\$1.95**  
15 FT. ANTENNA IN 3 SECTIONS..... **\$1.95**

### MOBILE—AN-75—PORTABLE ANTENNA

Antenna AN-75 is used for either portable or vehi-  
cular operation. For portable operation, the antenna is  
clamped to the radio housing. For vehicular operation,  
the antenna is clamped under the hood of the vehicle  
or to some stationary support.

When collapsed, length is 12", extends  
to 84" flexible and light weight. New.... **\$1.95**



GET ON OUR MAILING LIST!  
New items being released monthly  
at bargain prices!  
New Ham Flyer Now Ready!  
SEND FOR IT TODAY!

ALL SHPTS. F.O.B. WHSE. Calif. residents add sales tax.  
25% deposit required. Specify shipping instructions and ADD  
SHIPPING COSTS TO EACH ORDER. All items subject to  
prior sale and change of price without notice.

## ARROW SALES, INC.

Mailing Address: Box 3878-Q.

North Hollywood, Cal.



**A. C. Household ELECTRICITY**  
*Anywhere... IN YOUR OWN CAR!*

**BE PREPARED FOR ANY EMERGENCY WITH ATR INVERTERS!**

**Ideal for Emergency Lighting, Power Applications for Civil Defense, Red Cross, Rescue Work, etc. Simply Using Extension Cords.**

**EASY TO INSTALL EASY TO OPERATE**

**Also... DICTATE REPORTS ACCURATELY-PROMPTLY! make your car, boat or plane a "rolling office"**

**WITH ATR INVERTERS**

for changing your storage battery current to A. C.

**Household ELECTRICITY Anywhere in your own car!**

LIST PRICE **\$2250** AND UP

**ATR INVERTERS** especially designed for operating standard 110 volt A. C.

- TAPE RECORDERS • DICTATING MACHINES
- WIRE RECORDERS • ELECTRIC RAZORS

See your jobber or write factory today for complete information

**ATR AMERICAN TELEVISION & RADIO CO.**  
 Quality Products Since 1931  
 SAINT PAUL 1, MINNESOTA—U. S. A.

(from preceding page)

$$Z_r = (Z_0)^2 / Z_a$$

A  $\frac{1}{4}$ -wave, 300-ohm line will invert ohms to 90 ohms; 2,000 ohms to 45 ohms, so on.


For accurate results, the line must be wave long at the test frequency, and each of the antenna must resonate to the same frequency.

Quarter-wave lines (or odd integral multiples thereof) may be used, instead of  $\frac{1}{2}$ -lines, in the antenna tests already described, but the line impedance must be known, the actual antenna impedance calculated the aid of formula (8).
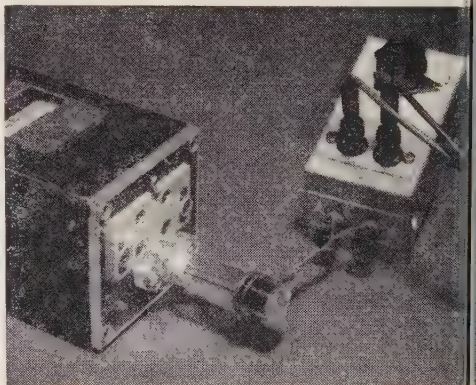
### Measuring Very Low Impedances

The feed-point impedance of parasitic and low-frequency mobile antennas may be less than ten ohms. Although this low impedance may be inverted through the use of a  $\frac{1}{4}$ -wave line, there is a simpler way of surmounting it.

Just connect a non-inductive resistor bet



Method of using the Antennascope Jr.

the "hot" Rx terminal and the load. The measured impedance will be the load impedance plus the added resistance. For example, a 50-ohm resistor is used and the Antennascope reads 54 ohms, the actual load resistance is four ohms.

### Vertical Antennas

To determine the characteristics of a  $\frac{1}{2}$ -wave antenna, connect the Antennascope between the antenna and ground or the ground radials and proceed as before. The radiation resistance will be in the 30 to 35-ohm range.

The impedance at the feed point of a ground plane antenna may be increased by "drooping" the radials downward. The Antennascope indicates when the impedance has reached the desired value, which is usually about 50 ohms, to match 50-ohm coaxial cable.

(Continued on page 50)

## 'COMMANDER' TRANSMITTER

NOW . . . permits power inputs up to 50 watts AM

## COMMANDER

... an extremely compact and versatile transmitter, advanced in design, modern in circuitry. It covers a continuous frequency range from 1.7 to 54 mcs and may be operated xtal control as-is or with the Gonset VFO. A 6146 output tube and two 7C5's as modulators permit plate voltages of 400 to 500 volts—inputs, (modulated) to 50 watts. Two high Q coils provide

coverage of 75-40-20-15-11 and 10 meter amateur bands and are readily changed from front of housing. The output circuit eliminates loading problems frequently present with pi networks where the load is a short, loaded mobile antenna. Circuit also couples into balanced or unbalanced lines, can be quickly

converted to "PI" or "L" networks by simple wiring change. Driver is bandswitched. The Commander uses any standard carbon or PA-type dynamic or crystal microphone. No preamp required.

An excellent VFO is available as a companion unit for the Commander. This is an extremely stable, low drift unit and uses no tubes—requires no operating voltage—coax cable, (furnished) plugs into fitting on Commander panel. Unit covers 75-40-20-15-11-10 meter amateur bands. Very rugged and compact—can mount next to transmitter or on steering column.

COMMANDER (with tubes) . . . Net 124.50

VFO . . . . Net 29.95

FIRST WITH  
THE FINEST!



801 SOUTH MAIN ST. BURBANK, CALIF.



# ELECTRICAL ENGINEERING

-or-

PHYSICS  
GRADUATES

*Here is an ideal way for the engineer or physicist with some aptitude for writing to enter the field of advanced electronics. In this area you can make immediate and effective use of your academic training while acquiring additional experience.*

Hughes Research and Development Laboratories are engaged in a continuing program for design and manufacture of integrated radar and fire control systems in military all-weather interceptor aircraft. Engineers who produce the maintenance and operational handbooks for this equipment work directly with engineers and scientists engaged in development of radar fire control systems, electronic computers, and other advanced electronic systems and devices.

-Scientific and Engineering Staff-

## HUGHES

RESEARCH AND  
DEVELOPMENT LABORATORIES

—Culver City, Los Angeles County, California.

Relocation of applicant must not disrupt an urgent military project.

## MAKE WAY! This boy's in bad shape!



cataplexy of the capacitors, rheumatiz of the resistors, dysentery of the dials, bursitis of the bandswitch, cirrhosis of the shields, filariasis of the filters? Tch, tch, a pity . . . such a nice old receiver. Well, as we were saying, it's too bad it wasn't traded before it was too late. If your old receiver is creaking at the joints and can't seem to stand the gaff of present-day QRM and wearying contest sessions, it'll pay you to drop a card to our Communications Equipment Division. Tell us the model number of the receiver you want and the receiver you'd like to trade—you'll be surprised at our terrific trade-in offer. By the way, if you don't have our latest Supplement (No. 139), we'd sure like to send you a copy. Write Allied Radio Corp., 100 N. Western Ave., Dept. 16-G-4, Chicago 80, Ill.





## VAARO VARIABLE IS THE ORIGINAL ALL-BAND SINGLE UNIT COIL WHICH GIVES YOU 75 - 40 - 20 - 15 - 11 and 10 METER BANDS.

Can be INSTANTLY TUNED to ANY  
DESIRED BAND or FREQUENCY by  
moving the SLIDER until transmitter  
loading is obtained. "ALL  
BANDS IN ONE COIL"

FINEST MOBILE COIL  
EVER BUILT:

- Factory Pre-tuned. • No Grid  
Dipping. • 3-Second Band Chang-  
ing. • Corrosion & Shatterproof  
Construction. • No Loose Con-  
nections. • Continuous Coverage  
from 3750 kcs to 30,000 kcs. •  
Highest "Q" Available. • Fits All  
Whips & Bases.

V-102B—0 to 500 Watts Input—  
\$17.95 Amateur's Net

V-103B—0 to 1,000 Watts Input—  
\$19.95 Amateur's Net

COMPLETE ANTENNA from Base  
Mounting to Whip Tip ALSO  
AVAILABLE...

NEW LITERATURE READY.

AT YOUR DEALERS, or WRITE

VAARO ELECTRONIC ENG. CO.

P.O. BOX 5035 LONG BEACH, CALIFORNIA




## READY-TO-USE 2 METER CONVERTER

Now you can receive 2-meters on a conventional Short Wave  
Receiver. Especially designed Push-Pull 6J6 R. F. Amplifier  
into 6J6 Oscillator-Mixer. Balanced line input, coaxial output.  
All slug-tuned adjustments, high quality components. Output  
frequency is 21 to 25 MC. Highly stable oscillator. SMALL  
SIZE 5" long, 3 1/4" wide, 3 1/2" deep. AN EXCELLENT BUY  
OF COMPONENT PARTS ENABLES US TO SELL AT  
THESE LOW PRICES. We guarantee satisfactory results.  
COMPLETELY WIRED, TESTED, ALIGNED UNITS—with  
TUBES. MODEL 1A—

WITHOUT POWER SUPPLY..... \$16.95

MODEL 2A—

WITH A.C. POWER SUPPLY..... \$21.95

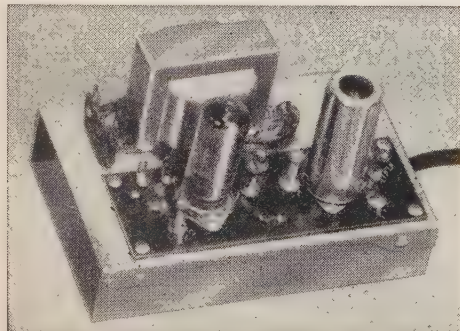

MODEL 2A (ILLUSTRATED) WITH A.C. POWER SUPPLY  
FOR ADDITIONAL DETAILS REFER TO CQ MAGAZINE:  
PAGE 32, DEC., 1953

IN KIT FORM WITH COMPLETE, SIMPLIFIED INSTRU-  
CTIONS.—Less Tubes.

MODEL 1—without Power Supply..... \$ 9.95

MODEL 2—with A. C. Power..... 14.45

SEE YOUR LOCAL DISTRIBUTOR or CONTACT US.

**K & L RADIO PARTS CO.**

1406 VENICE BLVD.

LOS ANGELES 6, CALIF.

(from page 48)

Mobile and other loaded antennas may be analyzed in the same manner as other verticals. Their feed-point impedance may be as low as five ohms. Therefore, an added series resistance may be required to measure the exact value.

### Parasitic Arrays

The driven element of a parasitic array is adjusted with the aid of the *Antennascope* in the same way as any other dipole. Impedance readings will normally fall between a few ohms and 100 ohms. Do not be surprised if two apparently identical arrays show up considerable differences on the *Antennascope*. Also, it is not unusual to discover more than one null in a close-spaced array. In a 3-element array, for example, there may be partial nulls at the self-resonant frequencies of the reflector and director, as well as at the resonant frequency of the radiator. Careful attention to the standard length formula (7) will eliminate confusion from these multiple nulls.

Normally, the reflector runs 5 per cent longer and the director 4 per cent shorter than the radiator. Varying their lengths seldom increases the gain of the array, but doing so will shift the resonant frequency and the center impedance of the radiator. Changes in their length can only be made intelligently with the aid of a field-strength meter.

### Measuring Standing-Wave Ratios

The actual standing-wave ratio of a feed line can be measured in several ways with an *Antennascope*. If the *Antennascope* shows a complete null with *R1* set to the line impedance and the *Dipper* set to resonant frequency of the antenna, the SWR is 1:1.

When the line is not flat, comparing the line impedance ( $Z_0$ ) with the setting of ( $Z_s$ ) required to null the *Antennascope* will also indicate the SWR, thusly:

$$SWR = Z_0/Z_s \text{ or } Z_s/Z_0 \quad (9)$$

Also the *Antennascope* may be calibrated to read SWR directly. Set *R1* to the impedance of the line upon which measurements are to be made. Adjust coupling to the *Dipper* for full-scale meter deflection with the *Rx* terminals open. Without disturbing any of these adjustments, connect different non-inductive resistors across the *Rx* terminals and note the current on the meter.

A resistance equal to *R1* will, of course, produce zero current. Higher and lower resistances will cause the meter to indicate. Prepare curve of SWR vs. current readings up to about 10 to 1. In the future to read SWR, set *R1* to the predetermined value and determine the line SWR by comparing the meter deflection with the calibration curve.

# You Asked For It!


a complete handbook on the hottest thing in Ham radio

## "SINGLE SIDEBAND TECHNIQUES"


by Jack N. Brown, W3SHY, ex-W4OLL

(the first volume in the CQ TECHNICAL SERIES)

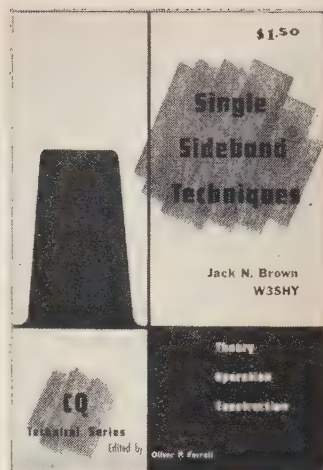to be released in September  
order your copy today and have it mailed  
when it comes off the presses—ONLY \$1.50



## You Continue to Ask For It—

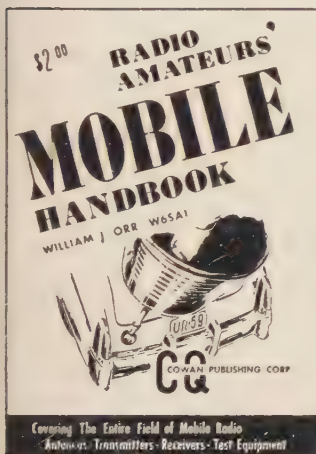

## "Radio Amateurs' MOBILE HANDBOOK"

by William I. Orr, W6SAI

the one book exclusively devoted to the subject of mobile  
installation, construction and operation. ONLY \$2.00

Ask for either book at your jobber or  
radio parts distributor—or use the coupon  
below for prompt service from the publisher.



CQ Magazine  
67 West 44th St., New York 36, N.Y.

CQT-6

Enclose find \$\_\_\_\_\_ for which please send me \_\_\_\_\_ copies of the  
"MOBILE HANDBOOK" @ \$2.00 each.

send me \_\_\_\_\_ copies of "SINGLE SIDEBAND TECHNIQUES" @ \$1.50 each  
as soon as it is printed.

All New York City purchasers please add 3% sales tax to above items.

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



# Go Mobile

## NEW BABCOCK

### MT-5B

#### MOBILE D-X MITTER 6 Band Bandswitching



5" x 8" x 7" deep

**Vibration-Proof, Shock-Proof, Small, Compact**

New exclusive meter, D'Arsonval movement, new crystal oscillator circuit using 6CL6 tube. VFO-XTL crystal switch and VFO connector now on panel. Same professional performance and fine quality as found in Babcock military radio equipment. Constant solid signal, every tube, every part tied down. Lifetime gray Hammertone metal case, easy to install. Examine—compare—buy Babcock!

Price complete with tubes, plugs and instruction book, Ham net. . . . . **\$119.50**

Contact your dealer or write for literature

**BABCOCK RADIO ENGINEERING, INC.**

7942 Woodley Ave., Van Nuys, Calif.

Export, Frazar & Hansen, 301 Clay St., San Francisco, USA

## Ham and Novice Crystals

Write for new low prices and specs.

### TPL-1 RADAR CHASSIS

Contains 6 oil-filled condensers. Transformers, chokes, raft of other parts worth \$20-\$25! Approx. **\$1.79**

24x18" in size and 75 lbs in weight. Fair cond.

### ID-51/TPS-3 DUAL INDICATOR

Great for scope, monitor AND PPI RADAR ON SHIPS. With 12-6SN7, 7-6V6, 3-6AG7, 2-6HG6, 1-5CP1, 1-7BP1 TUBES—worth \$50.00 alone! If you really know what this is, you'll latch on to it! **\$29.95**

### NEW. TREMENDOUS REDUCTION. . . . .

### RA-105 HI VOLTAGE POWER SUPPLY

This is a hot one! 117.5 VAC. Single phase, 60 cyc. 2400 V. output. Filter capable of supplying all NU, bias v and Fil. v of sig. C xmt and rec. **\$13.95**

PARTS ALONE WORTH \$75.00! NEW. . . . .

40 METER COMMAND ARC-S RECEIVER. **\$3.95**

With tubes. Good condition! Look-ee-eel! **\$29.95**

### MBF COLLINS TRANSCEIVER

10 meter, crystal control, 110 V. 60 cyc. **\$29.95**

With tubes like new. ONLY. . . . .

### TUBES!

304 TL. . . . .	\$2.95	5CP1 . . . . .	\$4.95
3C24/24G . . . .	1.00	829B . . . . .	5.95
5BP4 . . . . .	2.95	832A . . . . .	4.95

2 METER or 220 BAND VARIABLE TRANSMITTER. Freq. 95-210 Mc. 30 W. output R.F. contains 2-832, 2-5R4, 2-6C4, 1-6X5, 1-6V6, 3-6AC7, one 931 photo-electric cell, two 24 V. motor blowers, etc. **\$17.95**

### SUMMER GIVE-AWAY! Like new. . . . .

### TG-10 AUTOMATIC KEYS

Photocell operated. Self-contained 25 W. amplifier. 300 head phone capacity. Self-contained power supply. **\$19.95**

Tape rewinding keyer. Like new, less tape. . . . .

### 6 VDC PORTABLE PISTOL GRIP SPOTLIGHT

40,000 beam candle power and spotlight. Plugs into cigarette lighter or bulb socket on car. YOUR AUTO NEEDS THIS. A MUST FOR NIGHT DRIVING & SAFETY! Brand new, original box. **\$3.95**

REDUCED TO

All orders FOB Los Angeles. 25% deposit required. Items subj. to prior sale. WRITE FOR FREE NEW HAM FLYER. DEALER INQUIRIES INVITED.

**COLUMBIA ELECTRONICS SALES**

2251-53 W. Washington Blvd., Los Angeles 18, Cal.

(from page 50)

In common with other resistance-type, bridges, these last two methods of determining line SWR give entirely accurate results only when the antenna is resonant and the line is an integral multiple of a  $\frac{1}{2}$  wave\* at the frequency, because they are not capable of properly evaluating the reactive component introduced by non-resonant operation.

## Other Uses Of The Antennascope

Many additional uses for the *Antennascope* 54 and the *Antennascope Jr.* will suggest themselves to the reader.

\* or of a  $\frac{1}{4}$  wave—Editor.

## TVI FILTER

(from page 16)

plate about 2 inches square and bolting with bolts to the bottom of the can. At the base of the cavity the r-f current density is high. For this reason care should be taken to see that a good electrical connection is made between the center conductor and the bottom of the can.

The connectors for the input and output should be either soldered or bolted into place, depending on the type used. The location is shown in Fig. 2 as about 3 inches up from the bottom of the cavity for the can we used. The height of the center conductor is 6.75 inches, or just high enough so that the end capacity effects are not too great when the top is soldered back on to close up the can. The can should be opened with as clean a job of "can opening" as you can do. The top should be soldered back on when all parts are inserted.

The cavity will work best when connected to the output of the transmitter through a piece of co-ax cable about one-quarter wavelength. At no time should the output of the cavity be left unloaded. The voltages developed due to the high VSWR produced by an open line may damage the connectors.

With the cavity connected the tuning procedure in the transmitter will not change. However, the point of "dip" may change on the final plate circuit dial. This is due to a slight reactance term in the insertion impedance of the cavity.

The best tuning procedure is to dip the final and uncouple it slightly. Then resonate the cavity as indicated by the r-f crystal probe. The transmitter may then be fully loaded and tuned as usual. The results measured on the cavity are shown in Fig. 4. It can be seen we realized as high as 50 db. attenuation at 200 Mc. We did not bother to measure

thing above 400 Mc. or below 40 Mc. since we feel that most of the "junk" coming out of a 2-meter transmitter will fall in that range. The curve speaks for itself giving both the loaded  $Q$  of the cavity from  $Q = f/\Delta f$ ; where  $\Delta f$  is the bandwidth at the 3 db. points, and the attenuation we can expect at any point. For example, if you know a transmitter has an undesirable 72 Mc. response you can easily see that 27 db. attenuation can be expected at this frequency. When we consider the ease of mechanical construction and the low electrical power loss of the cavity, the results in terms of, attenuation of undesirable signals are most gratifying.

## DX NEWS

(from page 31)

with Clipperton, passing WØYXQ. F08AJ also put W6AM on 171 A3 . . . Al, W8PQQ, and Howy, W2AGW, are neck and neck at 243 with F08AJ under their belts . . . W6SYG, W3EVW and W8BHW stand at 242 with Clipperton and W8BHW's EA9DE and CE0AA. W3EVW hits a phone total of 166 with F08AJ, EA9DD and VP8AN . . . W6MX goes to 241 with F08AJ while W6ADP also lands on 241 by coming up to date with F08AJ, EA9DC, VS5ELA, ZC2MAC and CE0AA . . . George, VE4RO, now roosts on 238 thanks to Clipperton while W6DZZ jumps to 235 with OD5AX, 4W1UU, EA9DF, FR7ZA, VK1HM and F08AJ . . . W6GDJ, with F08AJ, makes it 231 . . . El, W7BD, goes to 228 with CE0AA, ST2AR, EA9DE, F08AJ and VP2DA . . . W6TI goes to 221 with F08AJ while W6DLY added F08AJ and VR3A to reach 219 . . . Epsie, W6EPZ, hits 214 with additions of YJ1AB, OD5LX, CE0AA, EA9DF, F08AJ and VR3A . . . W6BUD also adds six to reach 208 . . . W6BUO adds F08AJ, VR3A, FX8AC, VK9OK, EA9DF and VP2GX for 148 . . . WKIA leads the 39 zoners with a modest 239 thanks to Clipperton QSO. This jumped him over W5ASG's 238.

KV4AA went to 236 with F08AJ and Al, W2WZ, jumped to 234 with ZA1KAC, FL8UU and F08AJ . . . W3EPV comes up to date with FB8EB, ZD7A, FB8ZZ, SV0WG, CE0AA, EA9DD, VQ9UU and F08AJ giving him 230 . . . W1BIB adds 15 new ones to give him 223 . . . Howy, W2QHH, tags along, with 223, courtesy of F08AJ . . . Mike, W9FKC, adds EA9DD, VP2GRO, F08AJ, VK9OK and VR3A to reach 216 while W9HUZ reaches 206 with HI6EC and F08AJ . . . Carl, W1ZL, adds F08AJ for No. 205. F08AJ also pushed W3KDP to an even 200 . . . Buck, W4RBQ, came up with Clipperton and JZ0KF to hit 195 while W6GPB goes to 193 with EA9DF, ZB2A, IIBNU/T and F08AJ . . . W9ABA rises to 179 with EA9AP, OD5XX and F08AL . . . W8VLK submits 17, overdue, additions to land on 177 . . . TF3SF nabbed FB8ZZ and FB8BB for 39 zones . . . W6CAE moves to 145 with 32 additions . . . Tom, TI2TG, grabbed F08AJ, and lengthened his lead as No. 1 man in the 38 zone group . . . Bill, WIHA, added ZSSD, VPSAL, MP4BBE and VS9AD to reach 202 while Bob, W0TKX, came up with CE0AA, SV0WA, EA9DD and F08AJ to rest on 184 . . . W4EPA went to 155 with F08AJ and ZC4IP . . . Dixie, W2ZVS, reached 163 with EA9DF while Sam, W3AXT, nabbed VK9OK, ZS7D and FY7YC for a 167 total . . . Jim, W5FXN, rests on 165 with VP2GRO, VR3A and F08AJ while the latter two also helped Miles, W6ZZ, to reach 135.

Lou, W1MCW, ran her phone total to 211 with ZC5VR while Willard, WINWO, was close behind with 206 helped by F08AJ . . . F08AJ also moved TI2TG to 182 on phone . . . KV4BB gets in the act with 35-186 to lead the 38 zoners and then, whoops, adds MP4QAH for 187!

W1FH hooked HK0EV, A3 . . . W8JGU added F08AJ, HI6EC, VK9RM, JZ0KF and MP4BBK . . . W2MOJ nabbed F08AJ, A3, I5LV and MP4BBK . . . TI2TG nabbed 26 HK0 calls!! . . . W9UKG reached 100 with FK8AL and VQ5DZ . . . First W2 for VR3A was W2AGW . . . SM5AQV is up to 70 on 3.5 Mc. with EI2X,

(Continued on next page)



## LOOKING FOR DX? GET A GOTHAM BEAM AND WORK THE WORLD!

Reports tell the story of GOTHAM BEAM performance—you can work more DX in a day off a GOTHAM BEAM than in a year off a wire or dipole. GOTHAM BEAMS are strong, too; easy to assemble and install, no special tools or electronic equipment necessary; full instructions included, matching is automatic; maximum power gain built into the design—AND ALL AT LOW, LOW, PRICES.

## NEW! NEW! NEW! 2-METER BEAM KITS

GOTHAM proudly presents a 6 element Yagi beam for 2 meters at only \$9.95. Contains a 12 foot boom, 1" alum. tubing; 5/8" alum. tubing for elements; Amphenol fittings; all hardware, and instructions. Vertical or horizontal polarization, terrific performance!

And GOTHAM'S new 12 element Yagi for 2 meters at only \$16.95! Contains a 12 foot boom, 1" alum. alloy tubing; 5/8" tubing for elements; all Amphenol fittings; all hardware, and instructions. Vertical or horizontal polarization, multiplies your power by 32!

## 10 M. BEAMS

**S103T - Std. 10m 3-El. T match, \$18.95.** 1—8' Boom, 3/4" Alum. Tubing; 3—6' Center Elements, 3/4" Alum. Tubing; 6—6' End Inserts, 5/8" Alum. Tubing; 1—T Match (4'), Polystyrene Tubing; 1—Beam Mount.

**D103T - DeLuxe 10m 3-El. T match, \$25.95.** 1—8' Boom, 1" Alum. Tubing; 3—6' Center Elements, 1" Alum. Tubing; 6—6' End Inserts, 7/8" Alum. Tubing; 1—T Match (4'), Polystyrene Tubing; 1—Beam Mount.

**S104T - Std. 10m 4-El. T match, \$24.95.** 1—12' Boom, 1" Alum. Tubing; 4—6' Center Elements, 3/4" Alum. Tubing; 8—6' End Inserts, 5/8" Alum. Tubing; 1—T Match (4'), Polystyrene Tubing; 1—Beam Mount.

**D104T - DeLuxe 10m 4-El. T match, \$30.95.** 1—12' Boom, 1" Alum. Tubing; 4—6' Center Elements, 1" Alum. Tubing; 8—6' End Inserts, 7/8" Alum. Tubing; 1—T Match (4'), Polystyrene Tubing; 1—Beam Mount.

## 15 M. BEAMS

**S152T - Std. 15m 2-El. T match, \$22.95.** 1—12' Boom, 1" Alum. Tubing; 2—12' Cen-

ter Elements, 3/4" Alum. Tubing; 2—5' End Inserts, 5/8" Alum. Tubing; 2—7' End Inserts, 5/8" Alum. Tubing; 1—T Match (6'), Polystyrene Tubing; 1—Beam Mount.

**D152T - DeLuxe 15m 2-El. T match, \$39.95.** 1—12' Boom, 1" Alum. Tubing; 3—12' Center Elements, 1" Alum. Tubing; 2—5' End Inserts, 7/8" Alum. Tubing; 2—6' End Inserts, 7/8" Alum. Tubing; 2—7' End Inserts, 7/8" Alum. Tubing; 1—T Match (6'), Polystyrene Tubing; 1—Beam Mount.

## 20 M. BEAMS

**S202N - Std. 20m 2-El. (No T), \$21.95.** 1—12' Boom, 1" Alum. Tubing; 2—12' Center Elements, 1" Alum. Tubing; 4—12' End Inserts, 7/8" Alum. Tubing; 1—Beam Mount.

**S202T - Std. 20m 2-El. T match, \$24.95.** 1—12' Boom, 1" Alum. Tubing; 2—12' Center Elements, 1" Alum. Tubing; 4—12' End Inserts, 7/8" Alum. Tubing; 1—T Match (8'), Polystyrene Tubing; 1—Beam Mount.

**D202N - DeLuxe 20m 2-El. (No T), \$31.95.** 2—12' Booms, 1" Alum. Tubing; 2—12' Center Elements, 1" Alum. Tubing; 4—12' End Inserts, 7/8" Alum. Tubing; 1—Beam Mount.

**D202T - DeLuxe 20m 2-El. T match, \$34.95.** 2—12' Booms, 1" Alum. Tubing; 2—12' Center Elements, 1" Alum. Tubing; 4—12' End Inserts, 7/8" Alum. Tubing; 1—T Match (8'), Polystyrene Tubing; 1—Beam Mount.

**S203N - Std. 20m 3-El. (No T), \$34.95.** 1—12' Boom, 1" Alum. Tubing; 3—12' Center Elements, 1" Alum. Tubing; 6—12' End Inserts, 7/8" Alum. Tubing; 1—Beam Mount.

**S203T - Std. 20m 3-El. T match, \$37.95.** 1—12' Boom, 1" Alum. Tubing; 3—12' Center Elements, 1" Alum. Tubing; 6—12' End Inserts, 7/8" Alum. Tubing; 1—T Match (8'), Polystyrene Tubing; 1—Beam Mount.

**D203N - DeLuxe 20m 3-El. (No T), \$46.95.** 2—12' Booms, 1" Alum. Tubing; 3—12' Center Elements, 1" Alum. Tubing; 6—12' End Inserts, 7/8" Alum. Tubing; 1—Beam Mount.

**D203T - DeLuxe 20m 3-El. T match, \$49.95.** 2—12' Booms, 1" Alum. Tubing; 3—12' Center Elements, 1" Alum. Tubing; 6—12' End Inserts, 7/8" Alum. Tubing; 1—T Match (8'), Polystyrene Tubing; 1—Beam Mount.

**HOW TO ORDER:** Remit by check or money-order. We ship immediately by Railway Express, charges collect; foreign shipment cheapest way. 10-day unconditional money-back guarantee.

**DEALERS & CLUBS: WRITE FOR QUANTITY PRICES!**

Send For Folder on Multi-Band and Pigmy Beams.


**GOTHAM HOBBY**

107 E. 126 Street  
New York 35, N.Y.



# BUY OF A LIFE TIME!

## TRIED AND PROVEN THE WORLD OVER

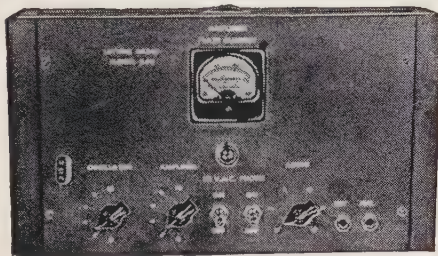

### LETTINE MODEL 240 TRANSMITTER WITH MOBILE CONNECTIONS AND A.C. POWER SUPPLY

This outstanding transmitter has been acclaimed a great performer throughout the world. Excellent for fixed station, portable or mobile operation. Air wound plug-in coils used for greater efficiency—never obsolete—will take any new freq. An outstanding buy, direct from our factory, ready to operate.

**NOVICES!** Save money. Buy only once. The 240 operates in the 80 and 40 meter Novice Bands, as well as the General Class Bands.

The 240 is a 40 to 50 watt Phone-CW rig for any freq. from 1.7 to 30 mc., complete with: (8x14x8) cabinet, A.C. power supply, 40 meter coils and crystal and tubes: 6V6 osc., 807 final, 5U4G rect., 6S37 crystal mike amp., 6N7 phase inverter, 2 616's PP mod. for excellent audio quality. Weight 30 pounds. TVI instructions included. 90 day guarantee. Price \$79.95.

\$25 deposit with order—balance C.O.D.  
80, 20, 10 meter coils \$2.91 per set. 160 meter coils \$3.60. Also for CAP, Broadcast, MARS, Marine, State Guard, Civil Defense.

**LETTINE VKF AND ANTENNA TUNER NOW IN STOCK**

### LETTINE RADIO MFG., CO.

62 BERKELEY STREET VALLEY STREAM, N. Y.

## CRYSTALS!

2 METER CRYSTALS. Ea. 69c

### COMPLETE SET—80 CRYSTALS

Ranging from 370-516 Kc., 54th Harmonic. INCLUDING 500 Kc. & 455 Kc. crystals.

Only . . . . . Per set **\$6.95**

### COMPLETE SET—120 CRYSTALS

Ranging from 370-540 Kc., 72nd Harmonic. INCLUDING 500 Kc. & 455 Kc. crystals.

Only . . . . . Per set **\$9.95**

200 KC. CRYSTAL . . . . . Ea. **\$1.75**  
500 KC. CRYSTAL . . . . . Ea. **.75**  
GENERATOR: 12 V. 35 A. Used cond. . . . . Ea. **3.95**

### \$600 VALUE! SPECIAL! HOT!!

A TRANSCIVER WITH A RAFT OF USES! Makes an ideal 2-Meter transmitter. Only a few of its many parts include: miniature blower, gear reduction motor easily converted to 110 VAC, over 40 miniature tube sockets, 7 panel coaxial fittings, microswitches, & MUCH MORE! Excellent condition. Original cost over **\$9.95**

\$600! IT'S ALL YOURS FOR ONLY . . . . .

### MS-53 INTERCHANGEABLE ANTENNA MAST

New. Per 3 ft. section. . . . . Ea. **97c**

### O-1 THREE-INCH MILLIAMPER METER

270° indication. You just by-pass shunt and add scale. ONLY **\$1.95**  
WITH Shunt By-passed. . . . . **2.49**

### EXTRA!

See Our Ad in April '54 Radio News.  
Loads of Hot Buys. No Change in Prices!

24 V. TRANSFORMER. Dri. 110 @ 2 amps. NEW **1.95**  
400 MICA CAPACITORS. Assorted. Mounted 10 to a strip. All 400. . . . . **1.95**  
ARW-2 REMOTE CONTROL RECEIVER. NEW. . . . . **27.50**

All merchandise sold as is

WRITE FOR QUANTITY DISCOUNTS!

Items subject to prior sale. Send for FREE Catalogue!

**J. J. GLASS ELECTRONICS CO.**  
1624 S. MAIN ST. LOS ANGELES 15, CALIF.

(from preceding page)

AP2K, KZ5DE, VP9BK and 4S7NG . . . W8BHW went to 124 on 21 Mc. with VP1GG, KW6BB, VP3YG, KJ6BA and F08AJ. Lindys phone total for this band is 103. . . . Max, W6ALQ, with new wooden frame beam, nabbed ZC5VS, ZP5AY, EA9DF, ZE3JP, OQ5CP, VP8AJ, YN1AA and others . . . W6YY rec'd A3 QSL's from VK1HM and ZC5VM . . . 160 meter QSO's at W9FIM this season included 15 with ZL3RB, 2 with ZL1WW and one with ZL1BY. Walt runs 150 watts to a 160-meter ground plane antenna, top section loaded, 93 feet up . . . VE3IG has an even 50 on 3.5 with GW3ZV and EA4CH . . . Mickey, W8YIN, nabbed MP4QAH, ZD6BX and F08AJ for new ones . . . Bill, W2SDB, has 79 to show for a year on the air. He has nabbed IT1AGA, TX4CZ, ZD4BQ, 5A2FA, HK4AB and EA9DF . . . W3CGS is up to 178 with such as CR5SP, ST2NW and EA9DE on phone. Harry nabbed 72 countries on 21 Mc. in '53 with 64 cards to show for it. Not a bad average . . . W6ZAT has worked VR3A on 3.5! . . . Bill, W6OHX, only runs from 25 to 40 watts, but that was good enough to drag in such as FK8AO, VR3A, VS6CG, KX6BU, KR6AA and many others.

## Here and There

W5PPI has the log of KF3AB covering the period from Nov. 29, 1953 to Feb. 19, 1954 and will be glad to replace any missing QSL's . . . It appears that the rumor that Russian amateurs might be allowed to contact V stations, after May 1, had no basis in fact. We have heard nothing to indicate that their restrictions have been loosened . . . VQ4DW is now on a six-month leave in England and may be contacted at 28 Kings Ave., Carshaton Beeches, Surrey . . . 4S7XG is due home from Ceylon shortly . . . ZS6ACD is now ZS1ACD . . . TI2TG received his WFJF and WAJAD awards after a six-month wait . . . ZD6RD was heard on 21,257, A3, workie KV4BB . . . G6ZO received visits from ST2AR at W3LYK/Antarctica . . . W1OMY is now K2BIB . . . W3AXT seeks QSL from CM1AR . . . W1WLW/1 w

## Japanese Award

The Japan DX Radio Club (JDXRC) will present a "WJDXRC" Certificate to any amateur station submitting proof of contact with five, or more, JDXRC members. Some active members are: JA's 1AAW, 1AB, 1AF, 1CC, 1CR, 1KF, 2DO, 3IW, 5BQ, 6AO, 7CS, 8AA, 9AB (ex-2WB), 0AA, 0AB, etc. QSO's should date after September 1, 1952. Contact Kiyoshi Mizoguchi, JA1BK, Box 7, Nerima, Tokyo, Japan for further details.

operate from Gilmanton, N.H. each week-end during summer . . . KV4AA was No. 60 for W1TSP . . . ZL visited K2BZT, he now works for BOAC and hopes to get his old call of G3CZT back. He plans 160 and meter operation . . . W2AOS/KG6 now keys from W3E . . . We regret to report the passing of VK5FL . . . GM3EYP, ex-VP8AP, may become a U.S. citizen . . . K6CST is none other than old W4ABY . . . W4OI Sparky, now keys from SV9WA . . . W0KBD sends cards from VP7NB and OE13USA for 100% average. FI2TG reports rumor that VU7BX is active from Di Garcia Island. Location unknown . . . W8VLK received WAA Certif No. 115.

## New Addresses

AB1US (Formosa)—APO 63, c/o P.M. San Francisco, Calif.

EL2P, EL2X—Via W1JOJ (EL2P, c/o P.A.A. Box Harbel, Liberia).

AK0 Expedition—L.C.R.A. Apartado Postal 584, Bogota, Colombia.

VQ4CF—Sailor, Box 5163, Nairobi, Kenya.  
W8DUY—Don Holzapfel, R.F.D. 5, Ashland, Ohio (QTH).

YU1AD—Mirko Voznjak, 152 Baje Sekulica, Belgrade, Yugoslavia.

ZC7DO—Paddy, Box 01, APO MELF 12, GPO, London, England.

Thanks to W2WZ, W6MUR, W6BIL.

## TEST EQUIPMENT

in the

### HAM SHACK

(from page 27)

checking electrolytics. From the time an ordinary electrolytic is manufactured, its days are numbered. Heat and overload increase its mortality rate. However, to offset this disadvantage they carry the widest tolerance of any common condenser. Because they are most suited for audio bypass and filter use they can be considered acceptable with variations as great as minus 25% or plus 200% from their rated values. Even this range can be exceeded with caution. And a word to the new Ham, always keep the electrolytics in low frequency uses. If r.f. is present in the same circuit shunt the electrolytic with a mica or ceramic condenser.

### Checking Paper Capacitors


Though robbed of some of its popularity by the new ceramics, the paper condenser is still used in great quantities. Paper capacitors seldom change much in value. A good "open-intermittent-short" check will usually tell the story except when sorting unmarked lots. The bulk of paper units today are non-inductive, that is, they are constructed in such a manner as to keep the internal inductance of the foil roll and leads to a minimum. This increases their efficiency at the higher frequencies. Unless one is sure that a particular paper condenser is of the noninductive type, its use should be limited to the broadcast, audio and intermediate frequencies. Even for these frequencies they should be used only for bypass and blocking purposes.

In using condensers make sure the breakdown voltage rating is sufficient for the job that they must do. Recently we had occasion to check a code practice oscillator of the usual variety using a battery tube, an interstage transformer and 45 voltage of "B" battery. In this particular case re-occurring peaks of 1200 volts were measured on the plate. While this is not common, don't belittle the voltages which can occur across the common plate to grid coupling capacity. It is a good rule to have the voltage rating of the condenser at least twice the value of the d-c voltage across it and more when practical.

The mica, which is one of the oldest condenser types, and the ceramic, which is one of the later additions to the family of condensers, have two things in common. Their use can be ex-

## PALCO

### Mobile Power Supplies

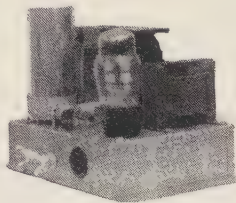


6 V. kit **\$29.50**  
12 V. kit **\$33.50**  
(fob factory)

- 500 VDC 225 Ma.
- No battery drain on standby.
- Instant start and stop—no waiting.
- Communications type vibrator.
- Small, compact, rugged. Shipping wt. 14 lbs.
- Chassis 6"x7". Height 6 3/4", Mtg plate 6x9".
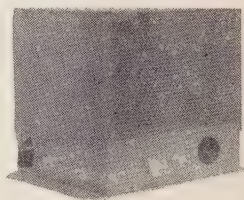
### NEW

- 6 V. input
- Output power switch. Pos #1 500 V 225 Ma. Pos #2 400 V 170 Ma.
- Built in relay for remote control.
- On-off switch for local control.
- 700 Volt filter condensers.
- Extra heavy duty vibrator.
- Complete power supply ready to go.



Model 6A, **\$49.50**  
(fob factory)

Order from

**PALCO ENGINEERING, INC.**

(new location)

**CARMEL, IND.**

### H.V. PLATE TRANSFORMER

Made by Chicago Transformer Co. 3000-0-3000 Volts RMS 300 MA. Primary 115V, 60 Cy. Type FS Full case Primary tapped to reduce voltage to 2500V. RMS. BRAND NEW BOXED IN ORIGINAL CASES. **\$29.96** ea.

A TERRIFIC VALUE AT.....

### MOBILE DYNAMOTORS

Made by Pioneer/Input 6 V. DC. Output 400 Volt @ 17 MA. Mounting bracket attached. Removed from equipment. A checked and guaranteed. This is your chance to get a small rugged Dynamotor at only..... **\$12.96**

### G.E. RELAY CONTROL

(Ideal for Model Controls, Etc.)

Contains a sigma midget 8000 ohm. relay (trips at less than 2 MA.) a high impedance choke, bi-metal strip, neon pilot and many useful parts. The sensitive relay alone is worth much more than the total **\$1.26** ea. 10 for **\$9.96**

Panel Meters NEW GOV'T SURPLUS STANDARD BRANDS 2" METERS	
0-4 Amps RF.....	\$2.95
0-80 ma DC.....	2.95
3" METERS	
0-200 Microamps.....	\$6.96
0-500 Microamps.....	5.96
0-200 Milliamp.....	4.56
0-250 Milliamp.....	4.56
0-150 Volt AC.....	5.95

### MINIATURE METER

1 3/4" Face, Bakelite case.  
0-500 micro amps. Ideal for  
GD Meters, Antennascope,  
Small Equipment.  
Only **\$3.96** ea.  
3 for **\$9.96**

### NATIONAL "S" METER

2", Illuminated Scale. Marked  
in DB 0-1 MA movement.  
BRAND NEW..... **\$2.96**

### OIL CONDENSERS

4 MFD-600VDC	\$ .95
10 MFD-600VDC	1.50
2 MFD-1000VDC	.95
3 MFD-1000VDC	1.25
5 MFD-1000VDC	1.95
12 MFD-1000VDC	2.95
15 MFD-1000VDC	3.50
3 MFD-1500VDC	2.65
5 MFD-1500VDC	2.85
6 MFD-1500VDC	2.95
10 MFD-1500VDC	3.75
15 MFD-1500VDC	4.50
2 MFD-2000VDC	2.25
3 MFD-2000VDC	2.95
4 MFD-2000VDC	3.95
5 MFD-2000VDC	4.50
6 MFD-2000VDC	4.95
10 MFD-2000VDC	6.95
12 MFD-2000VDC	7.95
2 MFD-2500VDC	3.95
4 MFD-2500VDC	5.95
2 MFD-3000VDC	4.95
.5 MFD-4000VDC	1.50
1 MFD-4000VDC	2.75
15 MFD-5000VDC	49.50
.1 MFD-7500VDC	1.75

Min. Order **\$3.00**—25% with Order. F.O.B. N.Y.

**PEAK ELECTRONICS CO.**

66 West Broadway New York 7, N. Y.

Phone WO 2-5439





## Terado Trav-Electric

miniature

**POWER CONVERTERS**  
10 WATTS TO 75 WATTS

CHANGE BATTERY CURRENT TO  
110 VOLTS—60 CYCLE A.C.

**FULLY FILTERED TO OPERATE  
MOBILE EQUIPMENT**

**\$11.95 LIST PRICE TO \$37.95**

**SIZE 2"x2"x3"-TO-4"x5"x6"**

SEE YOUR ELECTRONIC, AUTOMOTIVE,  
OR HARDWARE JOBBER OR DEALER.

## TERADO Company

Creators of Electronic Equipment

1052 Raymond Ave., St. Paul 14, Minn.

IN Canada Write: Atlas Radio Corp., Ltd.

560 King St. West, Toronto 28, Ont.

Export Sales Division: Scheel International, Inc.

4237 N. Lincoln Ave., Chicago 18, Ill. U.S.A.

Cable Address—Harshel

## SPEAKER SALE!

**HEAVY DUTY — GE 6" — PM**

**2.98 oz. Magnet**

MOUNTED IN 8" x 3-3/8" ROUND METAL BAFFLE  
(Used — but fully guaranteed)

FOR—playrooms, porches, music systems, radio shacks,  
intercommunications, P.A. systems, paging systems  
and replacement uses.

Original List

\$11.95

**NOW**

\$1.95 ea.

3 for \$5.00

**Cramer Electronics, Inc.**

811 Boylston Street

Boston 16, Mass.



## MOVING?

**Please Mail Us Your  
Change of Address**

Also be sure to include your old address, and code line from the mailing label. Or, if you prefer, tear off the entire label and send it along with your new address. Duplicate copies cannot be sent.

**CQ MAGAZINE**

67 West 44 Street  
New York 36, N.Y.

tended into the ultra-high frequency ranges, and they can be manufactured in various forms which are very stable. The present popularity of slug tuned circuits depends to a great extent upon the stability of mica and certain types of ceramics when used as the capacitive element in the resonant circuit.

However, for this type of work the (red) silvered mica is much preferred. When the ceramic types are used in resonant circuits, never use the general purpose varieties which

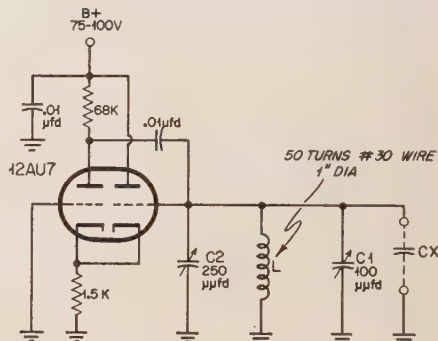


Fig. 7. A simple oscillator circuit for use in checking small value condenser at radio frequencies.

are intended for bypass and blocking only. The temperature coefficient of many of these is so poor that the only tolerance specification which can be given them is a minimum capacity below which they will not fall. This is of little importance, however, in reference to the bypass purposes for which they are intended, and should be taken into consideration when they are checked for capacity.

For those who use fixed condensers in tuned circuits, the small values from 1.0  $\mu\text{fd.}$  to 10  $\mu\text{fd.}$  are very important. The reactance of the very small values is so great at the 60-cycle frequency used in most ordinary bridges, that the accuracy of measurement begins to decrease in this range. For this reason we have found the little gadget diagrammed in Fig. 7 to be very handy around the shack.

### Measuring Very Low Capacities

This tester consists of a stable one-tube oscillator which can be operated from any small power supply and will deliver in the vicinity of 75 to 100 volts at 5 to 10 ma. The operation is as follows. A broadcast receiver is tuned to a local station at the high frequency end of the broadcast band and adjusted to a comfortable level output.

After warming the little tester up, Condenser C1 is set with its plates closed or fully meshed. This condenser is a straight line capacity of circular plate style. This setting should correspond to the zero setting on the dial used

*C1*. After this is done tune *C2* until a beat is heard with the broadcast station. Then carefully zero in the test oscillator until it is at zero beat on the receiver.

If the small value of capacity being tested is now connected at the terminals marked *Cx*, the frequency of the test oscillator will be lowered, producing an audio beat in the receiver. If the system is restored to zero beat by opening *C1*, the amount of capacity removed from the circuit by opening *C1* will equal the amount in *Cx*. In making a scale for *C1* the calibration will be in reverse to those normally used, or, the 100  $\mu\text{fd.}$  point on the scale will occur when the condenser is wide open and the zero  $\mu\text{fd.}$  point will be reached when the condenser is closed. The leads to *Cx* should be as short and rigid as possible although lead capacity will be cancelled out when *C2* is zeroed.

Calibration may be accomplished by testing several small condensers of known value and then plotting a curve. This will be accurate enough for most Ham work. It is surprising what a linear scale even the low priced tuning condensers will give. Of course, *C2* is only for zero setting and can have any style of plate shape.

This method is usable up to values of 1000  $\mu\text{fd.}$  or more until *C1* becomes rather bulky. One advantage of this little tester is that it



Wondering if there is a short or break in your co-ax feedline? Just measure the capacity with the checker and figure the distance from the manufacturer's specifications on  $\mu\text{fd./ft.}$

checks the capacity at radio frequency which is closer to the actual operating conditions. Even higher frequencies can be used if desired by merely changing the coil.

Although much of the material in this portion of our test equipment series has been concerned with developing the basic principals of capacity checking, we hope to have material of interest to the more advanced amateur in the near future. Of course, we're speaking of the impedance bridge which gives a more complete test of inductance, capacity and resistance.

## COMMAND SETS

SLASH/PRICED TO GO!

### RECEIVERS

3-6 MC ATA/ARA. Used. Xlnt.....	\$ 7.95
6-9.1 MC ARC-5. Used. Xlnt.....	5.95
190-550 KC. ATA/ARA. Used. Good Cond.	17.95
R-28 ARC-5. 100-156 MC. With all tubes. Used, good condition.....	19.95
R-4/ARR-2. 234-258 MC. VHF.....	6.95

### TRANSMITTERS

4-5.3 MC. ATA/ARA. Used. Xlnt.....	\$ 6.95
5.3-7 MC. ATA/ARA. Like new.....	5.95
7-9.1 MC. T-22/ARC-5. Extra clean.....	9.95
T-23/ARC-5. 100-156 MC. With two 832 tubes. Used, good condition.....	19.95

BC-456 MODULATOR. Used, good cond.	\$ 1.95
MD-7/ARC-5 MODULATOR, Used, good cond. ....	14.95
C-30/ARC-5 XMTR. CONTROL BOX.....	4.95

### CO-AX SPECIAL!

110 Ft. roll RG-8/U Co-axial Cable with PL-259  
on each end. Brand New. **\$4.50**  
Per roll .....


NOTE: Send full amount with order. Unless otherwise specified, material shipped via RR Express, shipping costs COD. Californians add 3% sales tax. All items subject to prior sale.

## V & H RADIO & ELECTRONICS

Dept. Q-1  
Los Angeles 6, Calif.

2033 W. Venice Blvd.  
Phone: REpublic 0215

## AMAZING NEW VIBROPLEX

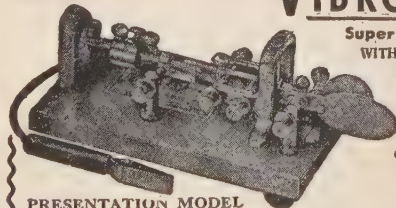

**Super Deluxe**  
WITH ADJUSTABLE  
MAIN SPRING  
AND OTHER  
GREAT  
FEATURES  
24-K  
GOLD-PLATED  
BASE TOP  
**\$29.95**

### PRESENTATION MODEL

Vibroplex presents the first really speed control key. An adjustable main spring permits operator to send slower or faster as desired. No more muddy signals... no sacrifice of signal quality! Suits any hand or any style of sending. Free of arm tension. Sends easily as pressing a button. Praised by operators and beginners alike. Try this new Vibroplex key! You'll be delighted. Other new popular Vibroplex keys from \$12.95 up. At your dealer or

**THE VIBROPLEX CO., INC. 833 Broadway, N. Y. 3, N. Y.**

## 8 WIRE CONTROL CABLE

Two No. 16, Six No. 20 tinned stranded copper, rubber insulated coded leads. Waterproof rubber jacket. Woven tinned copper armor shield overall. Dia. 7/16 inch. Continuous lengths up to 400 ft. Minimum order 100 ft. Shipped Express only, charges collect, F.O.B. **6c ft.**  
Chicago Warehouse. PRICE.....

**TRANS-WORLD RADIO-TELEVISION CORP.**  
6639 S. ABERDEEN ST. CHICAGO 12, ILL.



## EASY TO LEARN CODE

It's easy and pleasant to learn or increase speed the modern way—with an **Instructograph Code Teacher**. Excellent for the beginner or advanced student. A quick, practical and dependable method. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready, no QRM, beats having someone send to you.

### ENDORSED BY THOUSANDS!

The **Instructograph Code Teacher** literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the **Instructograph System**. Write today for full particulars and convenient rental plans.



## INSTRUCTOGRAPH COMPANY

Dept. C., 4701 SHERIDAN RD., CHICAGO 40, ILL.

## GO MOBILE with HARJO!

Compare these Prices—Write for FREE CATALOG!

### REGULATED POWER SUPPLY &

### PULSE GENERATOR HAZELTINE 1017

Complete with 28 tubes and hundreds of extra JAN components, FB for use as lab instrument or for constructing xmttrs, exciters, etc. Shp. wt. 100 lbs. Orig. gov't cost, approx. \$800. Complete with **\$49.50** diagrams. Check this price.

### For Hi-Power Mobile — Hi-Voltage

### FAN BELT GENERATOR

Orig. Gov't Cost, approx. \$180!

Delivers 1000 V. at 500 Ma from your fan belt—makes outputs of 200 to 300 watts possible. Instant hi-power, no machine work needed—ready to install. Complete with pulley, and voltage regulator, hookup diagram and suggested xmttr, tube and circuit combinations.

**\$24.95**

### 701A XMTR. TUBE only \$4.95

A surplus screen grid radar tube which duplicates many of the features of the 4-250 at far less the cost. Send for complete dope sheet. A pair will surprise you!

### DUMONT 3GP1 CATHODE RAY TUBES

**\$1.79 — 3 for \$5**

Complete with schematic for famed Dumont 224A oscilloscope. New, orig. boxes. See Moniscope article —page 15, April issue CQ.

### APS-13 Refer to our old ads ..... \$3.95

### CERAMIC CONDENSORS

Asst. brands. Brand New standard 100 for \$1 postpaid brands. \$10 value!

**MINIMUM ORDER \$3.00**

## Harjo Sales Co.

Dept. OD—4109 Burbank Blvd., Burbank, Calif.

P.O. Box 1187, Magnolia Park Sta.

Cable: Harjo Phone: Rockwell 9-2411

VISIT OUR RETAIL SHOWROOMS

## PROPAGATION

(from page 35)

the equatorial sporadic E during the summer months. The data also clearly indicates that sporadic E occurs in patches. These patches were seldom found occurring simultaneously at points closer together than a few hundred miles. Additional observations made at Stanford by Helliwell, accurately placed the predominant height of the sporadic E layers at 100 kilometers above the earth (62.5 miles) in winter and near 110 kilometers (69 miles) in summer. Sporadic E was also found to peak in occurrence at night, with another peak noticed near noon on the sporadic E occurring during the winter months.

## NOVICE SHACK

(from page 38)

license and want a "General Class" license, do you have to appear before the FCC examiner to take the code test.

The answer to both of these questions is "yes." However, if you live more than 75 miles from a point where the FCC holds amateur license examinations at least five times a year, or can certify by a doctor's certificate your inability to appear at such an examination point, you are eligible to apply for the "Conditional Class" license which grants the same privileges as the "General Class

## HELP WANTED

(to obtain a Novice license)

Johnnie Jones (16), 1012 Madison St., Valparaiso, Ind.

Bob Pence (13), 406 Center St., Valparaiso, Ind.

Francis L. Jacobs, 4 Wilson St., Anson, Me. Box 57. Phone Madison 6-3293.

Richard Bush (15), 1538 N. Volusia, Wichita, Kans.

Russell Canten (32), 56 Brooklyn Ave., Buffalo 8, N. Y.

Carl D. Stier, III (17), 5816 Lafayette Ave., Omaha, Nebr. (Also wants pen pals.)

Jim Le Monds (15), 11212 Milcoann St., Arcadia, Calif., phone FO 04001.

K. J. Farnsworth (35), 3708 South 23rd East Salt Lake City, Utah.

Yvan Deputter, 40 Denison, Granby, Quebec, Canada. Tel. 7650 (Just starting).

Duncan C. Sinclair (13), 402 3rd St., S.W. Moultrie, Ga.

Don Reynolds (13), 5613-16th North East Seattle 5, Wash.

Jack Perkins (16), 423 Bentley Ave., Beverly N.J. (Is waiting for his Novice license. Wants pen pals. Will answer all letters.)

Howard Gomes, 96 Main St., Pawtucket, R. I. Peter Butler (13), 88 South Ave., Whitman, Mass. Phone 1352.

## GET YOUR COMMERCIAL TICKET EASIER WITH...

### RADIO OPERATOR'S LICENSE

### Q AND A MANUAL

(4th Edition)

by Milton Kaufman

Covers Elements 1 through 8.

Complete discussion

of answers to every

technical question in the

F.C.C. Study Guide! Used

by over 50 leading

schools. Only \$6.60 at

jobbers, bookstores

or direct from—



JOHN F. ALLEN

Publisher, Inc.

480 Canal Street, New York 13, N. Y.

license, but is issued by mail. Those in the Armed Services who can show inability to appear at an examination point by presenting a signed statement from the Commanding Officer are also eligible to apply for a "Conditional Class" license.

George, WN3YJG, writes from Philadelphia, "Herb: I have had my ticket for about three months. I have had about 175 contacts in 14 states and Canada. I run 17 watts to a 6L6 on 3740 kc. My antenna is 14 feet long, and the receiver is an S-38C. I am 14 years old and would like to hear from other teen-age amateurs in the Philadelphia area. My address is 914 Napflee Philadelphia 11, Pa."

Ex-Novice Roy, W3WAF, reports on his activities dropping the "N" from his call. "Dear Herb: My DX has been KZ5CI, CO8HB, DL4EN, HH3RC, KP4WA, and CN8FL, all with 20 to 25 watts. HH3RC and CO8HB were in the 7.2-Mc. Novice band. Also, I have worked 43 states. Still need Wyo., Utah, Nev., and Mont. I would like to make a sketch of any WN's in those states. . . . I have worked on

Margaret, WN5AXC in Dallas, Texas. I sure got a big surprise one day, when her dad, W5EJV, called me on the telephone!" (Why did he call? Editor)

Dick, KN2HLA, certainly has not wasted much time. He reports: "I have been on the air for five weeks and three days. So far I have worked 25 states and Canada, with 19 confirmed, all on the 7.2-Mc. band. My best DX is California. My transmitter is a Heath AT-1, the antenna is 67 feet long, end fed, and the receiver is an S-40B. I am 15 years old and am on the air every morning until 10:00 a.m."

Glenn, WN5BWV, writes: "The enclosed photograph is proof positive that I take my amateur radio seriously. New Mexico is one of the states that allow amateurs to purchase call-letter license plates for their cars, but mine is the first Novice call-letter license plate I have seen. . . . I have made over 100 contacts in the few months I have been a Novice. I have worked 16 states, mostly on the 3.7-Mc. band. My transmitter is a TR-75TV, and the receiver is an S-40B. . . . The Novice way of getting into amateur radio is swell for the youngsters as well as some of us middle-age fellows. I think we owe a debt of gratitude to all the clubs and individuals who put in so much effort on this program. I, for one, would like to say thanks for a job well done."

Louise, WN3WRE, comes through with another of her interesting reports from Johnstown, Pa. "Dear Herb: I cannot understand why so many Novices complain that they do not get QSL cards. With about three exceptions, I have had a confirmation for every contact, and I now have 14 states confirmed. Fourteen states! This is a horrible record which I blush to admit when I read the letters saying 'Dear Herb: I got my ticket a month ago and now have thirty states.' I would adore meeting these supermen. . . . However, I do agree with the howls about long CQ's. Point being I get so darned bored waiting for them to quit and sign. Some times, I don't wait. . . . I get some interesting results now that I have some case yakking with my hand instead of with my mouth. I was carrying on a silly conversation with a KN2 one



Russ, WN1ZRF, Sherborn, Mass., "couldn't get out of New England" on 3.7 Mc. He is now on 7177 kc. and has over 100 contacts in fifteen states.

midnight. Two days later, I got a letter from my Mother telling me that I should not flirt with strange men—not even Hams—while Bill was working. Seems W3WET sat and copied our contact and entertained my family with it at breakfast the next day. No privacy."

Dave, WN5PKK, says, "Each month when CQ arrives, the first thing I turn to is the Novice Shack. All the Novices want to get their two cents worth in; so I would like to know how much it would cost a word. . . . Every day, I am hanging around 7180 kc. I run 70 watts and have an SX-71 receiver. I have worked 42 states, WP4, KL7, CO2, VE7, VE8 in a few months. I am trying for WAS. I am 12 years old."

Steve, K2EOF, offers his help to anyone in the New York City seeking a Novice license. His address is: Stephen M. Aug, 175 West 93rd St., New York 25, N. Y. Phone: RIverside 9-5523. He can be reached by phone most evenings.

(Continued on page 60)

## EIMAC ACCESSORIES for the Custom Rig...



- ★ VACUUM CAPACITORS    ★ HR CONNECTORS
- ★ AIR-SYSTEM SOCKETS    ★ FINGER STOCK

*Preformed contact finger stock* is an ideal electrical weather stripping for TVI proofing cabinets as well as being excellent for use with VHF and UHF circuitry. Silver plated, three widths—17/32, 31/32, and 1 7/16 inches.

*HR heat dissipating connectors*, precision machined from dural rod, available in 10 sizes.

*Air system sockets*, designed for Eimac tube types 4-400A, 4-1000A, 4X150A and 4X150D, simplify cooling and assure adequate flow of air to various seals.

*Variable vacuum capacitors* come in three models, are lightweight, compact and have low inductance. Also available are eight types of fixed vacuum capacitors.

- ★ For information  
write our Amateurs'  
Service Bureau.

**EITEL-McCULLOUGH, INC.**  
SAN BRUNO, CALIFORNIA



Export Agents: Frazar & Hansen, 301 Clay Street, San Francisco, California

## MAKE HARVEY RADIO YOUR HEADQUARTERS FOR MOBILE EQUIPMENT

Prompt Service — Immediate Delivery




**HARVEY RADIO CO., INC.**

103 W. 43rd Street, New York 36

Judson 2-1500



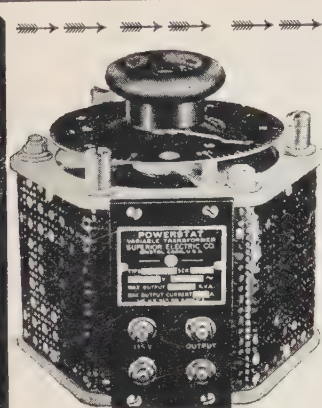

## VARIABLE VOLTAGE TRANS- FORMER

POWERSTAT  
TYPE NO. 1126

NEW  
ORIGINAL  
BOXES

**\$33.95**

Input 115 V. AC, 50/60 cycles. Output voltage 0-135 volts AC. Maximum amps output, 15 amps, 2 KVA. Overall size 8-3/16"x8-1/16". Complete with knob and scale. Send 30% deposit with order. Open accounts to rated firms.

## V & H RADIO & ELECTRONICS

2033 W. VENICE BLVD. LOS ANGELES 6, CALIF.  
Phone: REpublic 0215

## LEARN WITH AMECO COURSES

**BECOME  
A RADIO  
AMATEUR**

Simple, Low Cost, Home-Study Courses prepare you to pass F.C.C. Code and Theory Examinations for Amateur license and Code for Commercial license.

Sold at leading distributors or write for information to

AMERICAN ELECTRONICS CO.  
(Dept. C-7) New York 59, N.Y.

1203 Bryant Ave.

## AN/APR-4 COMPONENTS WANTED

In any condition. NEW HIGH PRICES. Also top prices for: ARC-1, ARC-3, APR-1, APR-5A, etc.; TS-34 and other "TS" and standard Lab Test equipment, especially for the MICROWAVE REGION; ART-13, BC-348, BC-221, LAE, LAF, LAG, and other quality Surplus equipment; also quantity Spares, tubes, plugs and cable.

ENGINEERING ASSOCIATES

434 Patterson Road

Dayton 9, Ohio

## MOBILES! C. D. MEN! CAP!!

IDEAL DYNAMOTOR — CONVERTS EASILY  
TO SUPPLY UNIT DELIVERING

12 VOLT INPUT	OR	6V INPUT
610V at 150 MA		300V at 90 MA
325V at 125 MA		160 at 110 MA

BRAND NEW WITH CONVERSION DATA \$3.75  
Send Check or M.O. Ship. Chgs. C.O.D.

COMMUNICATIONS EQUIPMENT CO.

131 Liberty St. Dept. Q-7 New York 7, N.Y.

## MOBILE... soldering made easy!

With the ORYX-12

Miniature Soldering Instrument

Available in 6, 12, or 24 volts. Light and small—slips in shirt pocket or log book. Feather weight of 1/2 ounce eliminates hand fatigue—puts the heat where you want it without damage to adjacent components. (Made in Great Britain). Ask your dealer or write the manufacturer's U.S. representatives:



Amateur Net \$4.95  
spare bits .39

TELEVISION ACCESSORIES COMPANY

Dept. 42, P.O. Box 6001

Arlington 6, Virginia

(from page 59)

Don, KN2GKK/K2GKK, writes, "I have started a new Ham club in the Jamestown, N. Y., area. We are holding Novice classes in code and theory. Anyone interested please contact me. The address is: Chautaugua La. Amateur Radio Association, Don Macdonald, KN2GKK/K2GKK, 100 West Fairmount Ave., Lakewood, N. Y. My rig runs 25 watts input on 3724 kc. and 7187 kc. and my receiver is a one-tube regenerative. I have worked ten states, and my best DX is 950 miles. I want to QSO with some WN1's. One of my problems is that my address is not yet in the Call Book and neither are the addresses of some of the stations I work; so we cannot exchange QSL cards. Anybody I have worked who has not received a card from me can send his to the address above, and I will answer it."

H. L. McPeak, W2SHT; Jim, W9HCQ; and R. Kuck, W6EBR/2, all took time to point out that there was an error in the formulas for calculating db, which appeared in the May column. The correct formulas are:  $db = 10 \log_{10} W_1/W_2$ , or  $20 \log_{10} E_1/E_2$ . At the moment, I reversed the multipliers for no reason that can think of. Fortunately, the error does not affect any of the figures or conclusions in the discussion of db.

Burt, WN9DIK, tells his story in a very few words. "Herb: I want to thank you for putting my name in the Novice Shack 'help' list a few months ago. At first, I was on 3.7 Mc., but now I am on 7.2 Mc., and I like a lot better. My transmitter is a TR-75 and the receiver is an S-53A. I am now waiting for my General."

Jerry, WN1AES, reports from New Haven, Conn. He has had my license for two months. Although I have



Glenn Howard, WN5BWV, Artesia, New Mexico, submits this picture in proof that he takes amateur radio seriously.

been spending most of my time experimenting with tennas, I have made about 15 contacts on 3.7 Mc. 7.2 Mc. with a Lettine 240 transmitter and an S-38C receiver. I have also done a little 147-Mc. work, thanks to the Yale University Radio Club. . . . I am 12 years old. Two of my friends have Novice licenses and two more are just about ready to take the examination."

I wish to thank, most sincerely, the members of the Soo Radio Club, Sioux Ordnance Depot, Sydney, Nebraska, for honoring me with their "Courtesy Award." I am trying to live up to it. The club also offers a "Certificate of Achievement and Honorary Membership" to any amateur working all members of the club. Earning certificate will be a real achievement for anyone on the side of Nebraska!—Herb.

Jerry, W9DKR, gets the honor of being anchor this month. "Hi Herb: WN9CUT installed a Heath AT-1 in his car, 8:30 p.m., April 28. W9QBD, W9JL and myself helped Jim adjust it. Then he and W9JL took it out for a trial run. I copied them for four minutes when the signal quit. . . . In a little bit, they called for help. The transmitter key had fallen apart; so I had had to put it together in the dark, without a flashlight—to report that they ran out of gas. So W9JL and I took them a gallon of gas and got them back to town. Without radio, it would have been a long wait."

Here's hoping that I receive a letter or a picture you before next month. Incidentally, please address mail to me to 385 Johnson St., Gary 3, Indiana. I go o.k., if it is sent to New York, but there is an unavoidable delay. 73—Herb.

# Here is an opportunity to save \$1.00 on your CQ Subscription!

The more in a group the bigger the savings. 6 men or more in a group save \$1.00 each; 4-man groups save 80c per man. Present CQ subscribers may participate in or form a group. Active subscriptions are automatically extended 1 year. Start a Group today! The informative, useful technical data appearing in future issues of CQ will make this the best investment you ever made. The Special Group Rate offer may be withdrawn at any time—so hurry.



Use the coupon for convenience. Address to:

CQ, the Radio Amateurs' Journal  
67 West 44th St., New York 36, N.Y.

Please enter 1-year subscription orders for the names given below. Our remittance is enclosed.

- ☐ One 1-year subscription
- ☐ Two 1-year subscriptions, each,
- ☐ Three 1-year subscriptions, "
- ☐ Four 1-year subscriptions, "
- ☐ Five 1-year subscriptions, "
- ☐ Six, or more 1 year subscriptions, each
- The preceding rates apply to U.S., U.S. possessions, APO and FPO only. Elsewhere add \$1.00 per year per subscription for Postage.

\$3.00  
2.50  
2.30  
2.20  
2.10  
2.00

(7)	
Name.....	Name.....
Address.....	Address.....
City.....Zone.....State.....	City.....Zone.....State.....
Call (if any)..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>	Call (if any)..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>
<hr/>	
Name.....	Name.....
Address.....	Address.....
City.....Zone.....State.....	City.....Zone.....State.....
Call (if any)..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>	Call (if any)..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>
<hr/>	
Name .....	Name .....
Address.....	Address.....
City.....Zone.....State.....	City.....Zone.....State.....
Call (if any)..... state whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>	Call (if any)..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>



## Classified Ads

Advertising in this section pertains to amateur radio activities. The publishers of CQ do not guarantee any product or service advertised in this section. Please print or typewrite copy. Remittance in full must accompany copy.

RATES: 25c per word per insertion for commercial business organizations.

5c per word per insertion for individuals on a non-commercial basis.

CLOSING DATE: July 25, for the Sept. issue.

WRITE: CQ Magazine, 67 West 44th St., N. Y. 36, N.Y. Attention, Jeanne C. Gillespie.

### Wanted:

NEED BC-348 receiver. W. Richards, 4908 Hampden Lane, Bethesda, Maryland.

WANTED: Complete sets or any parts used with: APR-4, BC-610, BC-614, BC-939, BC-729, ART-13, ATC, DY-12, DY-17, CU-25, loading coil, BC-312, BC-342, BC-348. Cash or trade for new or used equipment. Arrow Appliance Co., 38 Exchange St., Lynn, Massachusetts.

ALL SURPLUS equipment for cash. BC-221, I-56, TS-13, TS-148/AP, TS-263, etc.; and receivers, BC-348, BC-312, BC-342, AR-88, RBL, RAO, RBG; also TCS, BC-610, BC-614, R5A/ARN-7, ART-13, DY-17. We buy or swap technical manuals. Amber Company, 393 Greenwich Street, New York 3, N.Y. BEekman 3-6509.

WE WANT your used gear. Highest trade-in allowance on National, Hallicrafters, RME, Hammarlund, Gonset, Morrow, Johnson, etc. Write or call, C & G Radio Supply Co., 2502-6 Jefferson Ave., BR-3181, Tacoma 2, Wash.

AN/APR-4 RECEIVERS and tuning units urgently needed! Engineering Associates, 434 Patterson Road, Dayton 9, Ohio.

WANTED: AN/ARC-3. Write R. Ritter, 4908 Hampden Lane, Bethesda, Maryland.

JOHNSON VIKING I transmitter. Advise price, condition, final, etc. John Olson, W7TYW, Phillipsburg, Mont.

WANTED: ART-13 ATC, DY-12, DY-17, CU-25, BC-342, BC-312, BC-348, BC-221, TS-173, TS-174, APR-4 and tuning units, RA-20, RA-87, TG-7 teletype, keyboard perforators, TCS and parts, BC-939, BC-614, BC-610, APN-9, ARC-1, ARC-3, 32V, 75A, 310 exciters, ARN-7, manuals. Will buy for cash or trade for new amateur equipment, Johnson, Viking, Ranger, Hammarlund, Hallicrafters, National, Elmac, Gonset, etc. All types electronic equipment taken in trade. Altronics, Boston 1, Massachusetts. Richmond 2-0048, 2-0916.

WANTED: Set of "AA" coils for HRO50T1. Reasonable. Will swap something or purchase. W3GHD, Box 34, Philadelphia, Pennsylvania.

WANTED: BC-348 receivers. Write James S. Spivey Inc., 4908 Hampden Lane, Washington 14, D.C.

### Miscellaneous:

TRANSMITTER HUNTERS: We have a complete line of transmitter hunting equipment which is the product of many years experience of hunting and finding 10-meter hidden transmitters. Postcard brings information. W5NFC-W5QZZ, 2024 Ford St., Austin, Texas.

CRYSTALS? 2-meter? Etch surplus easily, cheaply. Instructions 35c W4ATE, 1001 Merritt, Old Hickory, Tenn.

INCREASE CODE SPEED. New method. Free particulars. D. H. Rogers, Fourth Street, Fanwood, N. J.

REPAIR on all makes of TEST EQUIPMENT, and kit construction, starting September First. Write now for free information. Bigelow Electronics, 135 North Pioneer Road, Beulah, Michigan.

GILFER ASSOCIATES offers new release from England 140-page "Radio Control for Model Ships, Boats and Aircraft." Paper bound—\$1.60, cloth bound \$2.10. Also the experimenters magazine from England, "The Radio Constructor." 6-month trial \$1.25; 12-month subscription \$2.50. Make checks payable Gilfer Associates, at P.O. Box 239, Grand Central Sta., New York 17, N.Y.

10, 15 & 20 METER BEAMS, aluminum tubing, etc. Perforated aluminum sheet for shielding. Radcliff's, Fostoria, Ohio.

Beautiful HANDPAINTED NECKTIES with your handle, call and antenna towers. Henry Schanding, W3RRF, Harrington, Delaware.

### For Sale:

FOR SALE: NC183D National Receiver. Used 6 hours. Perfect condition. \$295 or best offer. F. W. Lindsay, J 1523 West 9th St., Hastings, Nebraska.

DYNAMOTORS: 6 V input 425 output @ 375 m. Limited quantity. \$24.95. R. Mersey, W2TXI, 118 Franklin Ave., Lynbrook, L.I.N.Y.

SELLING OUT: Super-Pro SP-200 w/pwr/spkr/ra \$90; Meissner 150 B wo/exctr \$85; LM-15 w/pwr/bc \$75; 4E27 \$5 (4); UTC S-60 5v 22a 10 kv ins \$5 (4); UTC LS12X line-grid \$10; hundreds other tubes/pair Heavy gear local only, rest FOB. K2BEX, 102 Roosevelt Court, Carle Place, L.I.N.Y.

FREE AUTOMOBILE with purchase of Collins 75, and 32V-3, Selectronic Supplies, Inc., 1320 Madison Ave., Toledo, Ohio. Phone FU-3361.

FOR SALE: RME 45 Calomatic dial model \$100. BC-DM NBFM transmitter unconverted \$25. SCR-274 transmitter units \$15. W2CIT, 3919 William St., Seaford, N.

SURPLUS SPECIALS! RG-8/U cable 100 ft. \$5.95; ft. \$13.25; 500 ft. \$25.00. Coaxial connectors—PL-25 for \$2.25, SO-239 5 for \$2.00. New tubes—807 \$1.65, 81 \$4.25, 812A \$3.50, 813 \$10.50, 866A \$1.48, 304TH \$8.872A \$3.95, 24G \$1.85. Postage extra. Request free literature and visit our new store for thousands of bargains. Want to buy or swap. Selsyns, Synchros, Servo Motors, Ampdynes, RTA-1B Aircraft Radio. Electronic Research, 717 Arch Street, Philadelphia 6, Pa.

FOR SALE: 1951 Oldsmobile—4-door deluxe sedan equipped with complete mobile station, Sonar SRT-transmitter, Morrow 5-BR converter, Sherrick Antenna excellent performance of station and car, price \$1, Gonset Communicator used very little \$125; 2-m mobile antenna new \$4.00; Mallory dual vibrapack motor power supply \$22; Gonset mobile VFO \$10; Gonset Six Converter \$30. Reply to: C. Gallo, W2AWI, Lincoln School of Radio & TV, 1851 Broadway, New York 23, N.Y.

SELL: HRO-50T1, perfect including 21Mc. coils, money order \$230. KW, BC221 VFO, bandswitch except PP 813 final, TVI filter, antenna tuner, cannot pack ship, \$250. W5QLY.

FOR SALE: Complete mobile unit. One Leece-Neville Amp alternator and 100 Amp regular. Elmac 54 H transmitter with dynamic push-to-talk mike. 10-2 Morrow converter with noise limiter. Sky line 20 & M mobile antenna with heavy duty mount. PE-103 d motor with relays, etc. Transmit and receiver with Assortment of coax-cable and fittings. Over \$485 w of equipment. Make me an offer. Phil Summers, W8EL 410 Maple St., Delphos, Ohio.

75A3 less speaker, excellent, \$400. Pentron tape recorder less mike \$40. Ray Megirian, W4WZV/2, 169-63 Ave., Whitestone, New York.

WE ARE NOW IN our ultra modern building with stocks to serve you. Bargains, with new guarantee: \$69.50; S-40 \$69; RME-45 \$99; HRO Senior \$99; L 600 \$99; S-27 \$109; SX-43 \$129; S-76 \$149; SX-71 \$8 SX-42 \$189; HRO-50 \$275; 75A1 \$275; HT-17 \$32 EX Shifter \$69; Globe Trotter \$59.50; Harvey V Sr., \$79; Deluxe \$99; Viking I \$199; Elmac A-154 HT-9 \$199; Globe King \$295. Free trial. Terms final by Leo, W0GFK. Write for catalog and best deal. World Radio Labs., 3415 W. B'way, Council Bluffs, I.

### QSL Cards:

QSLs—New—Beautiful. Samples 10 cents. Graphic Cards, Route 12, Ft. Wayne, Indiana.

QSL's TWO COLOR, \$2.00 hundred. Samples for sale Rosedale Press, Box 164 Asher Station, Little Rock, Ark.

QSL's, SWL's. High quality. Reasonable prices. Sample Write Bob Teachout, W1FSV, Box C124, Rutland, Vermont.

QSLs of DISTINCTION. Three colors and up. Uncle Sam's Box 86, Lynn, Pennsylvania.

QSLs! "America's First Choice!" Samples 10c Te Press, Lakehurst, New Jersey.

QSLs, two colors, three dollars, three days, who Ham's "Super-Speed Specials." Samples dime. W9 Dept. S, 12811 Sacramento, Blue Island, Illinois.

QSLs—"Brownie" W3CJI, 3110 Lehigh, Allentown, Pennsylvania. Samples 10c with catalogue 25c.

QSL samples. Dime, refunded. Gale Press, W1BD, Wford, Connecticut.

QSLs, SWLs, Special! 2-color card \$4.25. Free sample Acme Printers, 707 West 8th, Los Angeles 17, Calif.

QSL's SWL's. Sample free. QSL Press, Passaic, N.J.

QSLs ??? Samples 20c Sackers, W8DED, Holland,



## For Sale:

JOHNSON VIKING II with Viking VFO, commercially  
ired, A1 condition, \$300. Harvey Wells TBS-50D, partly  
-TVI'd \$95. Stancor ST203A on 20 meters with dyna-  
motor power supply, remote control box, connecting  
bles \$60. Sanford Weiss, Tamiment, Tamiment, Penn.

JOHNSON VIKING Ranger Kit Form \$179.50 less tubes;  
ith complete set of tubes \$199.95; also available wired  
nd tested; write for details. We trade and offer terms.  
argest inventory of used Ham equipment in New Eng-  
nd. Write for latest list to W1BFT, Evans Radio,  
ncord, New Hampshire.

OR SALE: Hallcrafters SX-42 in excellent condition.  
K. Hussar, Box 143, Oak Hill, West Virginia.

ELL: Boehme automatic keyer for Morse code \$145.  
ehme Driver unit \$55. Boehme portable automatic ink  
order \$175; SX-42 \$145; HRO Sr. \$125; NC100X \$95;  
king I TVI'd \$185; 32V-2 \$485. Want: Collins 310B,  
C-342 or BC-312, 75A2 or 75A-1. Tom Howard, W1AFN,  
Mt. Vernon St., Boston 8, Mass. Richmond 2-0048.

ELLING OUT: power supplies, speech equipment and  
odulators, walkie-talkie units, one KW generator, trans-  
meters power and modulator some are new, ECO with  
7 final, three transmitters complete phone transmitter  
0 watts input ready to operate only \$175. Send for list.  
5HXC, Box 109, Blackwell, Oklahoma.

OR SALE: All equipment like new: HRO-50, coils  
ABCDEF Xtal. calbr. Viking I and VFO, TCS-14, AC  
d 12 volt DC supply. Remote and cables. Unused PE  
3. New Variac 7.5 amp. B & W grid dipper. Collins  
ES VFO. Send card for complete list of power sup-  
plies, etc. W6HVI, 2207 48th Ave., Oakland, California.

ELL: Like New: 1 S-38-B receiver \$25; 1 Browning  
req. meter model S-4 \$50; 1 Carter dynamotor 6v input  
0 v output @ 170MA. 1 Solar Examiner Cond. checker  
5. 1 clean PE-103-A dynamotor \$20. All FOB. W0JZP,  
06 Sunset St., Albert Lea, Minnesota.

EAL BARGAINS: New and reconditioned Collins, Nal-  
onal, Hallcrafters, Johnson, Elmac, Gonset, Babcock,  
orrow, RME, Millen, Lyco, others. Reconditioned S38  
9; S40A \$69; S76 \$129; NC57 \$69; NC88 \$89; NC125  
29; NC183 \$199; HRO50T1 \$299; HRO60 \$399; HQ-  
9X \$169; SP400X \$249; VHF152A \$39; RME45 \$99;  
nset Tri and \$29; Super-Cerber \$89; Commander xmit-  
r \$89; S40B, SX71, SX28A, SX42, SX62, HFS, HRO5,  
R07, Collins 75A1, 75A2, 32V2, 32V3, Viking II, Har-  
y-Wells Bandmaster transmitters, others. Shipped on  
ial. Easy terms. Satisfaction guaranteed. List free.  
enry Radio, Butler, Missouri.

OR SALE: Collins Exciter 310B1 excellent condition  
00. W0NGM, 509 Idaho Ave., Huron, South Dakota.

TTY, Model 12 complete. W6DOU, 1558 "B" St., Hay-  
ard, California.

ALLORY VP557 Vibropack, 400 vdc—150 MA. Elec-  
onic Laboratories model 2606 vibrapack, 300 vdc-100 MA.  
nset 2-meter mobile converter, Gonset Noise Limiter.  
Baake, W2GJP, 750 Pelhamdale Ave., New Rochelle,  
ew York.

BARGAINS: Stock up with these assortments. 12 rotary  
itches; 40 ceramic condensers, 20 wire wound resistors;  
mica condensers; 20 toggle switches; 10 volume con-  
ols. Your choice of assortments \$1.49; any 3 assort-  
nts \$3.99. Also giant 20-pound assortment of parts  
49. Aviation Accessories, Inc., Box 4178, Forth Worth,  
exas.

OLLINS 32-V3 transmitter, like new, used less than 10  
urs \$600. W5LBD, Box 323, Uvalde, Texas.

ALE: TBS-50-D \$85. W4TVE, Box 8693, Lantana, Fla.

OMLETE STATION including recently built all-band  
0 w. rack and panel transmitter with 813 final and  
onar CFC VFO with NBFM, NC-81X receiver; Astatic  
3 microphone, etc. Sell complete for \$200 or in parts.  
chard Applegate, W8ESJ, 19 Maple St., Berrien  
rings, Michigan.

OVING, MUST SELL. NBFM, 130-watt all-band trans-  
mitter (Sonar VFX-680, 24T55, 1000vct, 230MA. power  
pply, crystal mike). Plus TV52-40LP filter, co-ax,  
rge assortment of tubes, condensers (.5µfd 500v., etc.)  
ble & resistors. \$50 Bob Rodieck, Ft. Totten 59, N.Y.

U-18 2 coils \$10. Shipped collect. Harold Burdick, 619  
outh Adams, Sapulpa, Oklahoma.

LEANING SHACK: Eico 5" scope model 425 new con-  
tion \$45; Sonar VFX 680 NBFM VFO exciter with  
bes and set coils, good condition \$50; Millen 90800 75-  
at exciter with tubes and set coils, good condition \$20;  
C-454 3-6 Mc. Command receiver brand new \$11; BC-  
7A 4-5.3 Mc. Command transmitter, excellent condi-  
ion with spare tubes \$12.50. Postage extra. George  
cobs, W2PAJ, 144-40 72nd Avenue, Flushing 67, N.Y.

## Hamfest Announcements:

Remember Blossomland Amateur Radio Association's  
Hamfest Picnic, JULY 25 at Warren Dunes State Park,  
15 miles south of St. Joseph, MICHIGAN on U.S. 12.  
Ten-meter transmitter hunt. Bring gear for swap  
& shop. Registration fee \$1.00 in advance or \$1.25 at park.  
Advance registration through Al Carpenter, WN8ORM,  
Secy-Treas., St. Joseph, Mich.

The annual IRCC "Hoosier Hamfest" will be held on  
Sunday, JULY 18, at TPA Park, Frankfort, INDIANA.  
Registration begins at 10:00 a.m. with activities con-  
tinuing throughout the day. Wanta sell that surplus Ham  
gear? Bring it along. Prizes-awards-games-entertainment  
for all. Don't miss it!

WYOMING Hamfest JULY 24-25 at South Fork Inn.  
Watch for mobiles on Highway 16 west of Buffalo,  
Wyoming. Call any Wyo. Ham for info. W7QPP.

Augusta and Camp Gordon Radio Clubs will hold their  
Second Joint Hamfest on JULY 24 & 25 at Lake Olm-  
stead near Augusta, GEORGIA. Prizes, food, good cheer  
and all the trimmings. Contact O.K. Mixon, W4DJF,  
Masonic Building, Augusta, Georgia; or K4WAR, Camp  
Gordon, Georgia, for reservations. Y'all come!

South Hills Brass Pounders and Modulators 16th An-  
nual Hamfest, Spreading Oaks Grove, South Park,  
Pittsburgh, PENNSYLVANIA. Sunday, AUGUST 2, 1954  
— Noon till ??? Prizes-refreshments-games. For further  
information contact W3LDB, 4949 Roberta Drive, Pitts-  
burgh 36, Pennsylvania or phone WI 1-7025.

The 20th Annual Picnic and Air Mobile Meet of Ham-  
festers Radio Club will be held on the second Sunday of  
August, AUGUST 8, at Mance Park, ¼ mile east of  
Route 45 and ¼ mile south of Route 66 (Stinson Air-  
port). Food, ice cream and beverages available. Games  
for the kiddies. Hammo and Hamfesters style prize table.  
Donations are \$1 in advance, \$1.25 at the gate. Tickets  
from John J. Ruth, W9GVO, 4460 Oakenwald Ave.,  
Chicago 15, ILLINOIS.

## Instruction:

PORT ARTHUR COLLEGE, Port Arthur, Texas, pro-  
vides training in radio, radar & television necessary to  
pass FCC exams for phone and tel. licenses, 12-14 months.  
Start any level, low tuition with board & room at cost  
in dorm. Advanced students on-the-job KPAC (500-watt  
station) training. Approved for Veterans. Write "Regis-  
trar" for catalog and info. New courses start every  
5 weeks.

## Trading Corner:

SWAP: BC221, calibration perfect, cabinet slightly  
scratched, for Hallcrafters S-72 portable. W5QLY.

TRADE OR SELL: Model 12 teletype with synchronous  
motor, table, cover, stand and polar relay. Tape per-  
forator, distributor, and tape transmitter with three  
polar relays. All converted, wired and ready for opera-  
tion. Excellent condition. W4EBH, 328 West Whitlock  
Ave., Winchester, Virginia.

FOR SALE: Television set 7" \$30, suitable for monitor.  
Have couple larger. Want TV camera equipment. W4AP1,  
1420 South Randolph, Arlington 4, Virginia.

SELL OR TRADE: LM12 freq. meter and AC supply \$45.  
New PA107 UTC transformer \$50. Astatic KC mic and  
push-to-talk Stand \$25. Precision E-200-C Signal Gen-  
erator \$30. Model 203 Clough Brengle AC, resistance,  
capacitance, turns ratio bridge \$15. Pair of 813's \$15  
new surplus. Rider manual VII thru XIX \$50. A. McMul-  
len, 2800 Montclair Dr., N.E., Albuquerque, New Mexico.

FOR SALE OR TRADE: Transformers, coils, meters,  
etc.—too much to list here. Want mobile gear (only fac-  
tory built) or photographic equipment, such as camera  
or accessories, darkroom gear, etc. Send self-addressed  
stamped envelope for list. I. E. Aston, R.D. #3, Lan-  
caster, Pennsylvania. W3FMZ.

FOR SALE OR TRADE for 16 mm or 35 mm camera  
and equipment. T-23/ARC-5 new WO/tubes or crystals  
\$10; RT-19/ARC-4 two-meter transceiver, excellent, with  
tubes, xtals, and conversion data \$12; BC433G receiver,  
excellent, tubes, instruction book, control head, BX22E  
relay \$15; BC-453 Q5er excellent \$8; BC-779B Ham-  
marlund Super Pro (Army) like new \$100; 274N trans-  
mitters—5.3-7Mc and 3-4 Mc. complete with tubes and  
crystals \$5. each; transformer 3200 V CT 350MA, Navy  
rating, new \$12; 2-813 tubes, new, 7¢ each; 4-304LT,  
new \$1.50 each; 5-807, new, \$1.00 each. Write for list  
of power supplies and other parts. Carlos O. Love, 11009  
Tascosa Drive, Dallas 28, Texas.





### GOLD PLATED CRYSTALS

3 FOR \$1.00

TEN FOR  
\$3.00

#### ALL FUNDAMENTAL FREQUENCIES

5910	6350	6370	6470
6610	6670	6690	7350
7380	7390	7450	7580

Excellent Multipliers.

### REPAIR PARTS For BC 348

#### MODELS H, K, L, R, ONLY


Main Tuning Capacitor	\$4.50	Dual Volume Control	\$2.75
1st I-F Transf. Assy.	2.00	Main Tuning Cond. Knob	.50
2nd I-F Transf. Assy.	2.00	Band #1 Coils (set of 6)	3.00
3rd I-F Transf. Assy.	2.00	Band #2 Coils (set of 4)	2.00
4th I-F Transf. Assy.	2.00	Band #3 Coils (set of 4)	2.00
Crystal Filter Assy.	6.50	Band #4 Coils (set of 4)	2.00
C. W. Oscillator Assy.	2.00	Band #5 Coils (set of 4)	2.00
915 kc Crystal Mounted	2.75	Band #6 Coils (set of 4)	2.00

### DYNAMIC

#### HEADSET and MIKE

Dynamic mike and headset combination. A high quality, efficient unit, used in B-19 tank Xmts. Mike & phones complete, new

\$2.75

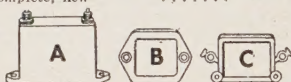

### TRANSMITTING MICA CAPACITORS

MFD	DCWV	Style	Price	MFD	DCWV	Style	Price
.00003	2000	A	.39	.00075	5000	A	\$1.79
.00003	3000	A	.39	.0008	5000	A	1.79
.00005	3000	A	.39	.001	4500	A	1.79
.00009	3000	A	.39	.002	500	C	.19
.0001	3000	A	.39	.002	3500	A	1.29
.0002	3000	A	.39	.003	2000	A	.29
.00035	2500	B	.29	.003	3000	A	.39
.00036	5000	A	1.79	.004	2000	A	.29
.000375	5000	A	1.79	.006	1200	C	.19
.0004	2500	B	.29	.006	2500	A	.39
.0004	3000	A	.39	.01	600	C	.19
.0005	3000	A	.39	.01	1200	C	.29
.00056	5000	A	1.79	.015	1500	A	2.45
.0006	2500	A	.39	.02	600	C	.19
.0007	3000	A	.39	.025	1250	A	1.10
.00075	2500	A	.39	.025	2500	A	1.79

### U.H.F. SPLIT-STATOR

#### VARIABLE CAPACITOR

17 Plates per section. Cap. per section 4.5 mmfd. min. and 35 mmfd. max. Air gap .030. Size 3 7/8x1 1/2x1 in.


2 for \$1.00



### HIGH-PASS FILTER CAPACITOR

This is a low inductance unit for TVI and other interference filtering in low voltage circuits. Rated at .5 mfd., 200 Volts D.C.

2 for \$1.00

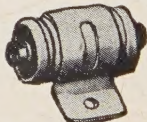

### BRUTE PLATE TRANSFORMER

#### 1500 VOLTS AT 600 MA.

This transformer used with 866's in a bridge rectifier will put out 1500 volts D.C. at 600 MA. Will handle both R.F. final and modulator for more than a half-gallon input. Primary 117 volts 60 cy., test voltage 5500 RMS. Mfd. by Raytheon. Hermetically sealed, oil filled, with cooling fins. Size: 12 1/2x10x10 in. Shipping wgt. 150 lbs. Quantity limited.

Only \$19.50




### TRIPLE FILTER CHOKE

A three section choke for use in power supplies where very low ripple, pure D.C. is wanted, such as for V.F.O.'s, high-gain speech amplifiers, etc. Terminals 1-2 = 3H at 275 MA; Terminals 2-3 = 17H at 125 MA; Terminals 3-4 = 17H at 125 MA. Mfd. by Raytheon. Size 8x7 1/2x3 3/4 in. Weight 23 1/2 lbs.

Test Voltage 1750 RMS.

MINIMUM ORDER  
\$3.00 No C.O.D.'s

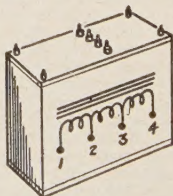

# ELECTRONICRAFT

INC.

27 MILBURN STREET

BRONXVILLE 8, N. Y.

## CQ Ad Index

Abernathy Electronics, Inc. ....  
Allied Radio Corp. ....  
American Electronics Co. ....  
American Television & Radio Co. ....  
Arrow Sales, Inc. ....

Babcock Radio Engineering, Inc. ....  
Barker & Williamson ....  
Bud Radio, Inc. ....

Centralab ....  
Collins Radio Company ....  
Columbia Electronics Sales ....  
Communications Equipment Co. ....  
Cramer Electronics, Inc. ....

Eitel-McCullough, Inc. ....  
Electronicraft, Inc. ....  
Engineering Associates ....

General Electric Company ....  
Glass, J. J. Co. ....  
Gonset Company ....  
Gotham Hobby Corp. ....

Hallcrafters Co. ....  
Harjo Sales Company ....  
Harvey Radio Company ....  
Heath Company ....  
Henry Radio Stores ....  
Hughes Research & Development Labs ....

Instructograph Company ....

K & L Radio Parts Co. ....

Lettine Radio Manufacturing Co. ....

Millen, James Mfg. Co., Inc. ....  
Mosley Electronics ....

National Company, Inc. ....

Palco Engineering, Inc. ....  
Peak Electronics Co. ....  
Petersen Radio Co., Inc. ....

Radio Apparatus Corporation ....  
RCA Tube Dept. ....  
Rider, John F. Publisher ....

Sherrick Products ....

Television Accessories Co. ....  
Terado Company ....  
Trans-World Radio-TV Corp. ....

U. S. Crystals, Inc. ....

Vaaro Electronic Engineering Co. ....  
V & H Radio Supply Co. ....  
Vibroplex Co., Inc. ....

World Radio Laboratories, Inc. ....

### DESIGNED BY "BILL" SCHERER

CONVERTER-ETTES. Highly sensitive and stable converter-prescaler for any one band. Broadcast is used to tune amateur bands. Chassis size 4"x2 1/2". For either 6 or 12 volts. Complete kit with tubes. TWIN NOISE SQUELCHER. Most effective noise available. Does not distort audio. Variable squelch background hash. Chassis size 2 3/4"x2 1/4"x1 5/8". For 6 or 12 volts. Complete kit with tubes \$10.00. Available direct, or at your favorite supplier

## SHERRICK PRODUCTS

86-11 SANCHO  
HOLLIS 23, N.



# blushing with PRIDE

The real test of a receiver, is the test of use. As the old expression goes "You've got to 'winter' it and 'summer it'" before you know how good it is. Part of the guarantee card shipped with each of our receivers is returned to us. On it is space for the owner's comments. As these cards pour in by the thousands, the enthusiastic comments we read never fail to give us a warm glow of pride. Here is a small sampling of the cards we've received commenting on the NC-98. No wonder this superb receiver is blushing.

## THE NEW NC-98

CRYSTAL FILTER • S-METER • 550 KCS. TO 40 MCS. RANGE • CALIBRATED AMATEUR BANDSPREAD OR CALIBRATED SWL BANDSPREAD (FOR SW LISTENING) • NEW MINIATURE TUBES • AN RF STAGE • ACCESSORY SOCKET • TWO I F STAGES • EDGE-LIGHTED LUCITE DIAL SCALES • NOISE LIMITER • SEPARATE HF OSC. • 3. POSIT. SEL. • ANT. TRIM. • PHASING CONTROL • SENSITIVITY CONTROL.

Unmatched Value at \$149.95




tuned to tomorrow

# National

THE NATIONAL ELECTRONIC COMPANY, INC. 41 Sherman St. Malden, Mass.



GOING STRONG—

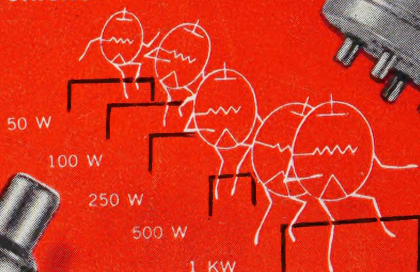

— SINCE EARLY CW DAYS

# RCA

## for those prefer triodes

Known the world over for their conservative ratings, large reserve of emission, and high power output at reasonable plate voltage, RCA power triodes continue to remain the first choice of the transmitter man who prefers triodes.

RCA has a modern line of power triodes to meet every power input requirement—'phone and CW. Check the facts in the charts below—and take your choice.

For R.F. Amplifier Service		Max. Amateur Ratings, Class C Telephony		
Type No.	DC Plate Input (Watts)	DC Plate Volts	Plate Dissip. (Watts)	Max. Freq.* (Mc)
RCA-810	750	2500	175	30
RCA-811-A	260	1500	65	30
RCA-812-A	260	1500	65	30
RCA-833-A	1000	3300	350	30
RCA-8000	750	2500	175	30
RCA-8005	300	1500	85	60

\*for Max. Plate Input and Voltage

For Class B Modulator Service (2 tubes)				Typical
Type No.	DC Plate Volts	Max.-Sig. DC Plate Cur. (Ma)	DC Grid Volts (Max. Rating)	
RCA-805	1250	400	—60	0
RCA-810	2250	450	—60	0
RCA-811-A	1250	350	—60	0
RCA-812-A	1500	310	—60	0
RCA-8000	2250	450	—130	0
RCA-8005	1500	330	—67.5	0

RCA Power Triodes—as well as ALL types of RCA tubes—are readily available through your neighborhood RCA Tube Distributor. For technical information, write RCA, Commercial Engineering, Section G15 M, Harrison, N. J.



**RADIO CORPORATION of AMERICA**  
ELECTRON TUBES  
HARRISON, N. J.